




ON Semiconductor®

Modeling the Control Voltage to Duty Ratio Block
Using a Voltage Mode Stage to Model a CCM
Current Mode Buck


Christophe Basso – IEEE Senior Member

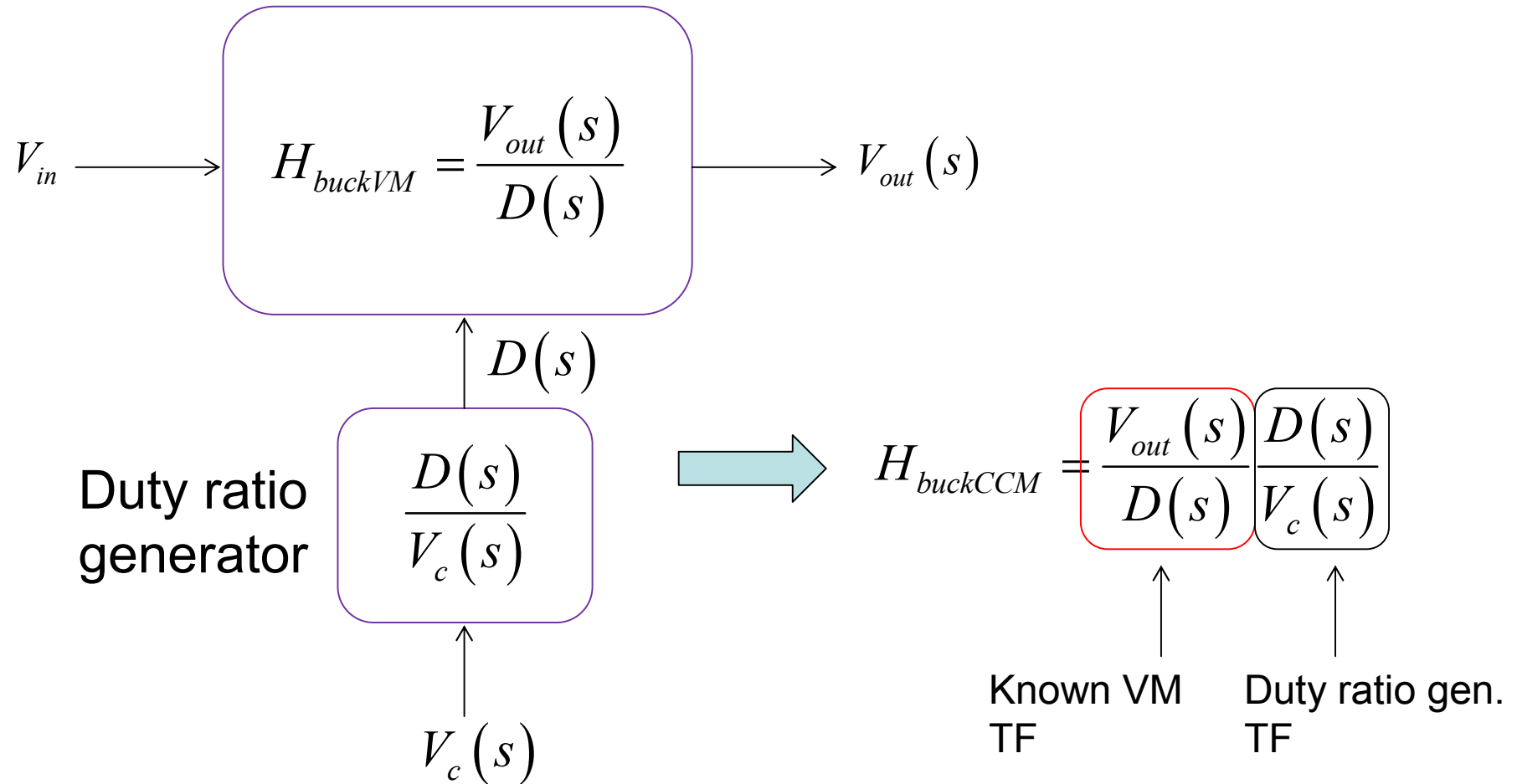Modeling current mode converters with an added generator:
 Keep the VM transfer function $V_{out}(f)/D(f)$
 → Model only the extra generator $D(f)/V_c(f)$



Terminal c current in the PWM switch model, CCM operation

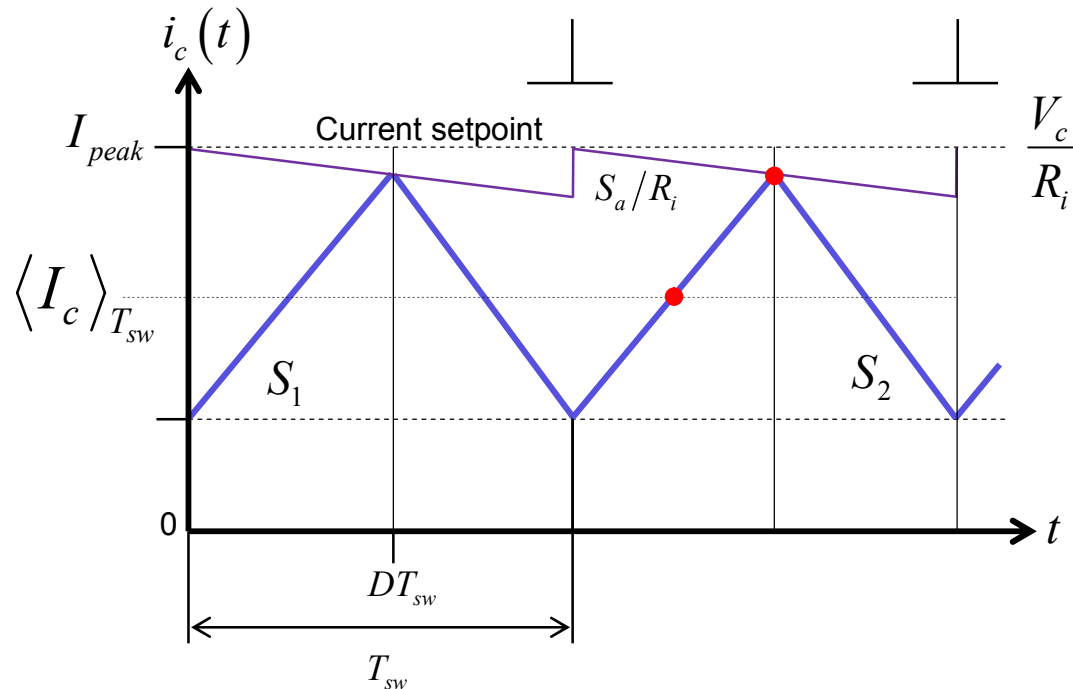We can extract the duty ratio definition from the average current in terminal c



$$I_c = \frac{V_c}{R_i} - \frac{S_a}{R_i} DT_{sw} - \frac{V_{ac}}{2L} DT_{sw} \quad \Rightarrow \quad D = \frac{F_{sw} (V_c - R_i I_c)}{S_a + \frac{R_i V_{ac}}{2L}}$$

Then extract the small-signal coefficients for all variables

$$\hat{d} = \frac{\partial \left(\frac{F_{sw} (V_c - R_i I_c)}{S_a + \frac{R_i V_{ac}}{2L}} \right)}{\partial V_c} \hat{v}_c + \frac{\partial \left(\frac{F_{sw} (V_c - R_i I_c)}{S_a + \frac{R_i V_{ac}}{2L}} \right)}{\partial I_c} \hat{i}_c + \frac{\partial \left(\frac{F_{sw} (V_c - R_i I_c)}{S_a + \frac{R_i V_{ac}}{2L}} \right)}{\partial V_{ac}} \hat{v}_{ac}$$

$$\hat{d} = k_c \hat{v}_c + k_{ic} \hat{i}_c + k_{ac} \hat{v}_{ac}$$

Must express these variables

$$k_c = \frac{F_{sw}}{S_a + \frac{R_i V_{ac}}{2L}} \quad k_{ic} = -\frac{F_{sw} R_i}{S_a + \frac{R_i V_{ac}}{2L}} \quad k_{ac} = -\frac{F_{sw} R_i (V_c - I_c R_i)}{2L \left(S_a + \frac{R_i V_{ac}}{2L} \right)^2}$$

For a buck $I_c = \frac{V_{out}}{R_L}$ $V_{ac} = V_{in} - V_{out}$



$$V_{in} := 15V \quad V_{out} := 5.03V \quad C_{out} := 100\mu F \quad r_C := 0.1\Omega \quad L_1 := 100\mu H \quad R_L := 1\Omega$$

$$V_{ac} := V_{in} - V_{out} = 9.97V \quad I_c := \frac{V_{out}}{R_L} = 5.03A \quad D := \frac{V_{out}}{V_{in}} = 0.335$$

$$V_c := 1.3V \quad F_{sw} := 100kHz \quad S_a := 0 \quad R_i := 0.25\Omega$$

$$k_c := \frac{F_{sw}}{S_a + \frac{R_i \cdot V_{ac}}{2 \cdot L_1}} = 8.024 \frac{1}{V} \quad k_{ic} := \frac{F_{sw} \cdot R_i}{S_a + \frac{R_i \cdot V_{ac}}{2 \cdot L_1}} = 2.006 \frac{1}{A} \quad k_{ac} := \frac{F_{sw} \cdot R_i \cdot (V_c - I_c \cdot R_i)}{2 \cdot L_1 \cdot \left(S_a + \frac{R_i \cdot V_{ac}}{2 \cdot L_1} \right)^2} = 0.034 \frac{1}{V}$$

$$I_c(s) = \frac{V_{(c)}(s) - I_c(s)Z_{eq}(s)}{sL} \quad \text{For a buck} \quad V_{(c)}(s) = V_{in}D(s) + \cancel{V_{in}(s)D_0}$$

$$I_c(s) = \frac{V_{in}D(s) - I_c(s)Z_{eq}(s)}{sL} \longrightarrow I_c(s)(sL + Z_{eq}(s)) = V_{in}D(s)$$


$$I_c(s) = \frac{V_{in}D(s)}{sL + Z_{eq}(s)} \quad V_{ac}(s) = \cancel{V_{(a)}(s)} - V_{(c)}(s) = -V_{in}D(s)$$



$$D(s) = k_c V_c(s) - k_{ic} \frac{V_{in} D(s)}{sL + Z_{eq}(s)} + k_{ac} D(s) V_{in}$$

$$D(s) \left[1 + k_{ic} \frac{V_{in}}{sL + Z_{eq}(s)} - k_{ac} V_{in} \right] = k_c V_c(s)$$
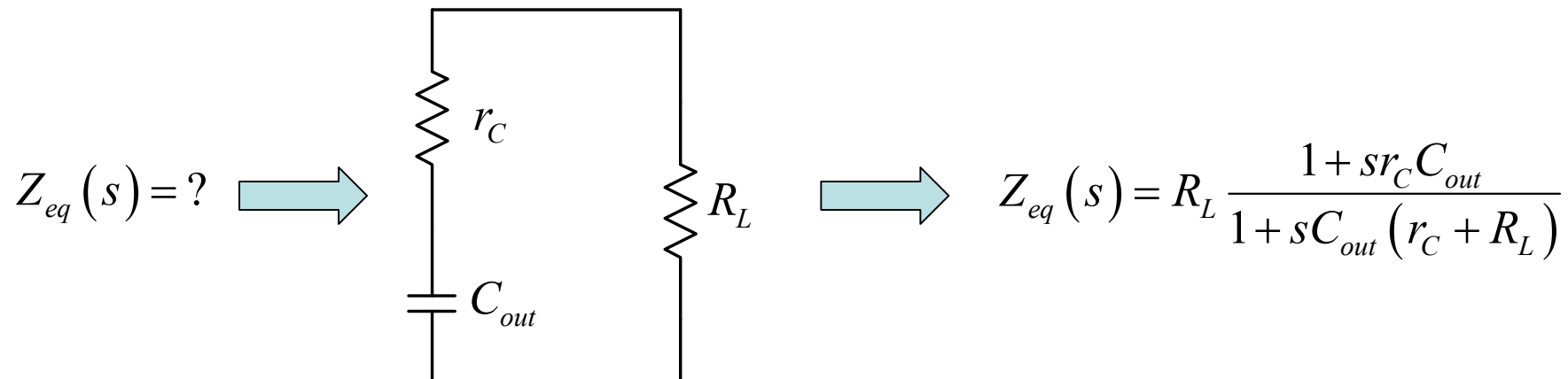
$$H(s) = \frac{D(s)}{V_c(s)} = \frac{k_c}{1 + k_{ic} \frac{V_{in}}{sL + Z_{eq}(s)} - k_{ac} V_{in}}$$



Develop $H(s)$, replace and rearrange...

Same location as LC filter poles

$$H(s) = \frac{R_L k_c}{(R_L + V_{in} k_{ic} - R_L V_{in} k_{ac})} \frac{1 + s \left(\frac{L + C_{out} R_L r_c}{R_L} \right) + s^2 LC_{out} \left(\frac{R_L + r_c}{R_L} \right)}{1 + s \left(\frac{L + C_{out} R_L r_c - LV_{in} k_{ac} + C_{out} R_L V_{in} k_{ic} + C_{out} V_{in} k_{ic} r_c - C_{out} R_L V_{in} k_{ac} r_c}{R_L + V_{in} k_{ic} - R_L V_{in} k_{ac}} \right) + s^2 \left(\frac{C_{out} LR_L + C_{out} Lr_c - C_{out} LR_L V_{in} k_{ac} - C_{out} LV_{in} k_{ac} r_c}{R_L + V_{in} k_{ic} - R_L V_{in} k_{ac}} \right)}$$

$$H(s) = H_0 \frac{1 + a_1 s + a_2 s^2}{1 + b_1 s + b_2 s^2} \quad a_1 = \frac{L + C_{out} R_L r_c}{R_L} \quad a_2 = LC_{out} \left(\frac{R_L + r_c}{R_L} \right)$$

$$b_1 = \frac{L + C_{out} R_L r_c - LV_{in} k_{ac} + C_{out} R_L V_{in} k_{ic} + C_{out} V_{in} k_{ic} r_c - C_{out} R_L V_{in} k_{ac} r_c}{R_L + V_{in} k_{ic} - R_L V_{in} k_{ac}}$$

$$b_2 = \frac{C_{out} LR_L + C_{out} Lr_c - C_{out} LR_L V_{in} k_{ac} - C_{out} LV_{in} k_{ac} r_c}{R_L + V_{in} k_{ic} - R_L V_{in} k_{ac}}$$

$$H_0 = \frac{R_L k_c}{R_L + V_{in} k_{ic} - R_L V_{in} k_{ac}} \quad Q_b = \frac{1}{b_1 \omega_0} = \frac{\sqrt{b_2}}{b_1} \quad \omega_0 = \frac{1}{\sqrt{a_2}}$$




$$Q := \frac{\sqrt{\frac{C_{out} \cdot L_1 \cdot R_L + C_{out} \cdot L_1 \cdot r_C - C_{out} \cdot L_1 \cdot R_L \cdot V_{in} \cdot k_{ac} - C_{out} \cdot L_1 \cdot V_{in} \cdot k_{ac} \cdot r_C}{R_L + V_{in} \cdot k_{ic} - R_L \cdot V_{in} \cdot k_{ac}}}}{L_1 + C_{out} \cdot R_L \cdot r_C - L_1 \cdot V_{in} \cdot k_{ac} + C_{out} \cdot R_L \cdot V_{in} \cdot k_{ic} + C_{out} \cdot V_{in} \cdot k_{ic} \cdot r_C - C_{out} \cdot R_L \cdot V_{in} \cdot k_{ac} \cdot r_C} = 0.12$$

Low- Q approximation holds


$$\omega_0 := \frac{1}{\sqrt{\frac{C_{out} \cdot L_1 \cdot R_L + C_{out} \cdot L_1 \cdot r_C - C_{out} \cdot L_1 \cdot R_L \cdot V_{in} \cdot k_{ac} - C_{out} \cdot L_1 \cdot V_{in} \cdot k_{ac} \cdot r_C}{R_L + V_{in} \cdot k_{ic} - R_L \cdot V_{in} \cdot k_{ac}}}} = 7.556 \times 10^4 \frac{1}{s}$$

$$\Rightarrow D(s) = 1 + b_1 s + b_2 s^2 = 1 + \frac{s}{\omega_0 Q} + \left(\frac{s}{\omega_0}\right)^2 \approx \left(1 + \frac{s}{\omega_{p_1}}\right) \left(1 + \frac{s}{\omega_{p_2}}\right)$$
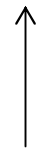
$$f_{p_1} = \frac{\omega_0 Q}{2\pi} = 1.44 \text{ kHz} \quad f_{p_2} = \frac{\omega_0}{Q 2\pi} = 100 \text{ kHz}$$



First pole

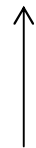

Second pole



The final plant transfer function of the CCM-operated buck is:

$$H_{buck}(s) = \frac{V_{out}(s)}{D(s)} \frac{D(s)}{V_c(s)}$$

↑
↑
 Voltage mode Duty ratio
 Buck TF Factory TF


$$H_{buck}(s) = V_{in} \frac{1 + sr_C C_{out}}{1 + \frac{s}{\omega_1 Q_1} + \left(\frac{s^2}{\omega_1^2}\right)} H_0 \frac{1 + \frac{s}{\omega_1 Q_1} + \left(\frac{s}{\omega_1}\right)^2}{\left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + \frac{s}{\omega_{p2}}\right)}$$

➔


$$H_{buck}(s) \approx V_{in} H_0 \frac{1 + sr_C C_{out}}{\left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + \frac{s}{\omega_{p2}}\right)}$$



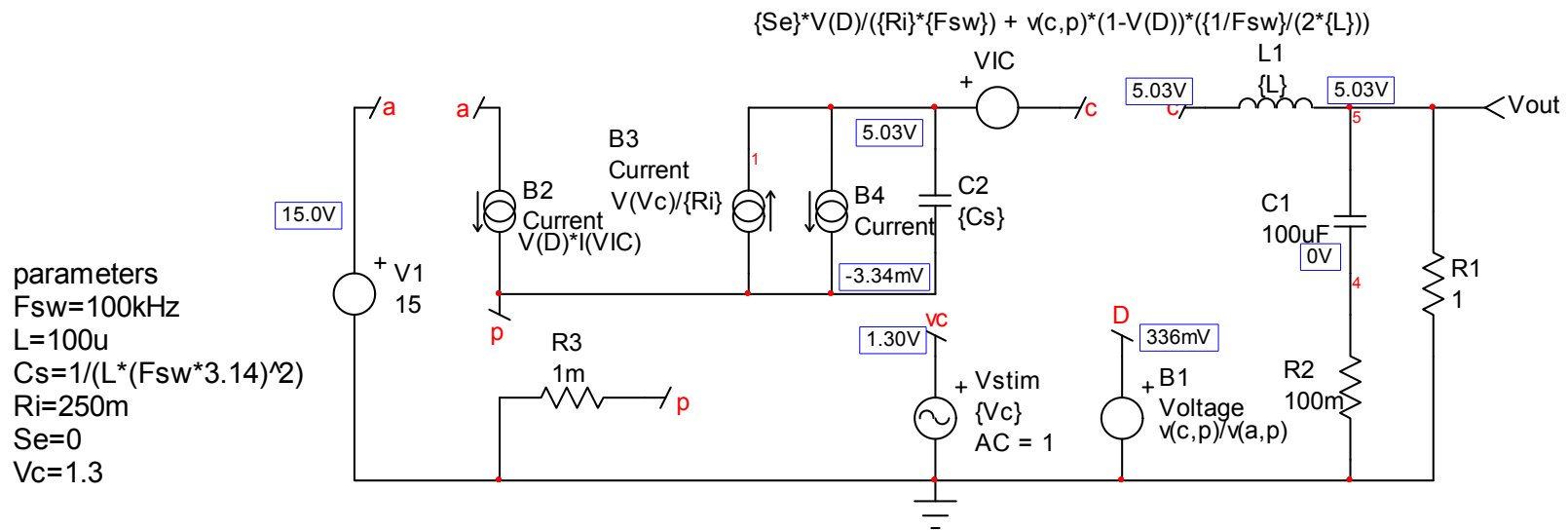Original large-signal CCM CM PWM switch model in a CCM buck converter



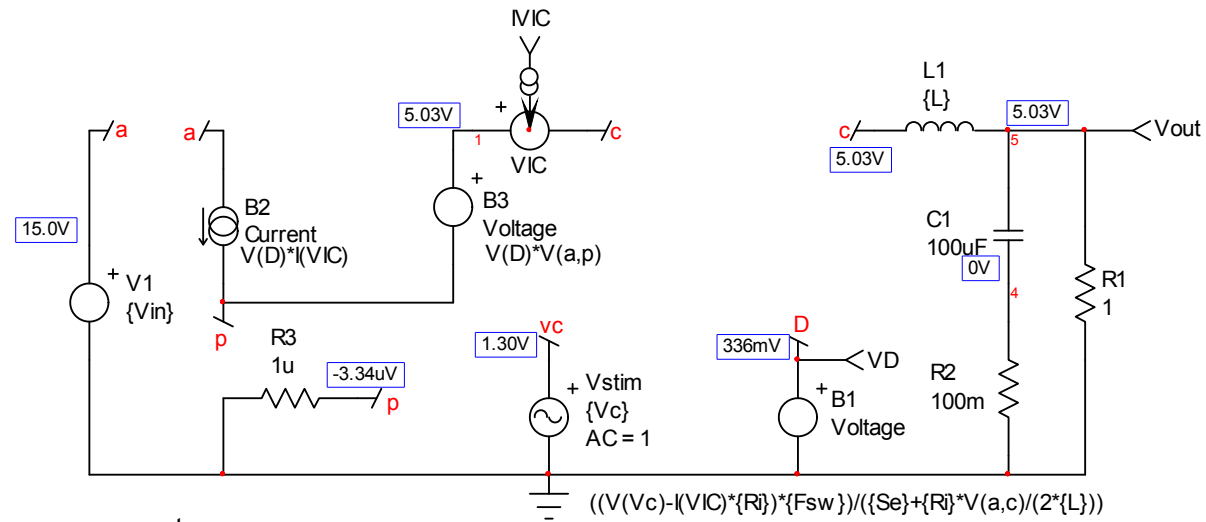
Simulation test model with duty ratio factory CCM buck converter



parameters

- Vin=15
- Vout=5.03
- Fsw=100kHz
- L=100u
- Ri=250m
- Se=0
- Vc=1.3
- RL=1
- Vac=Vin-Vout
- Ic=Vout/RL

Large-signal duty ratio generator

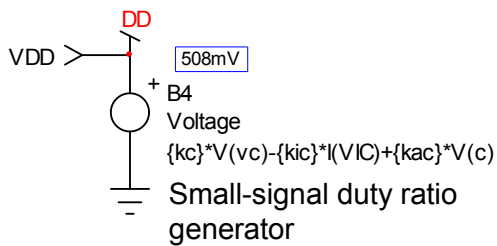

Small-signal duty ratio generator

$$k_c = F_{sw} / (S_e + R_i * V_{ac} / (2 * L))$$


$$k_{ic} = (F_{sw} * R_i) / (S_e + R_i * V_{ac} / (2 * L))$$

$$k_{acc} = F_{sw} * R_i * (V_c - I_c * R_i)$$


$$k_{ac} = (F_{sw} * R_i) * (V_c - I_c * R_i) / (2 * L * (S_e + R_i * V_{ac} / (2 * L))^2)$$




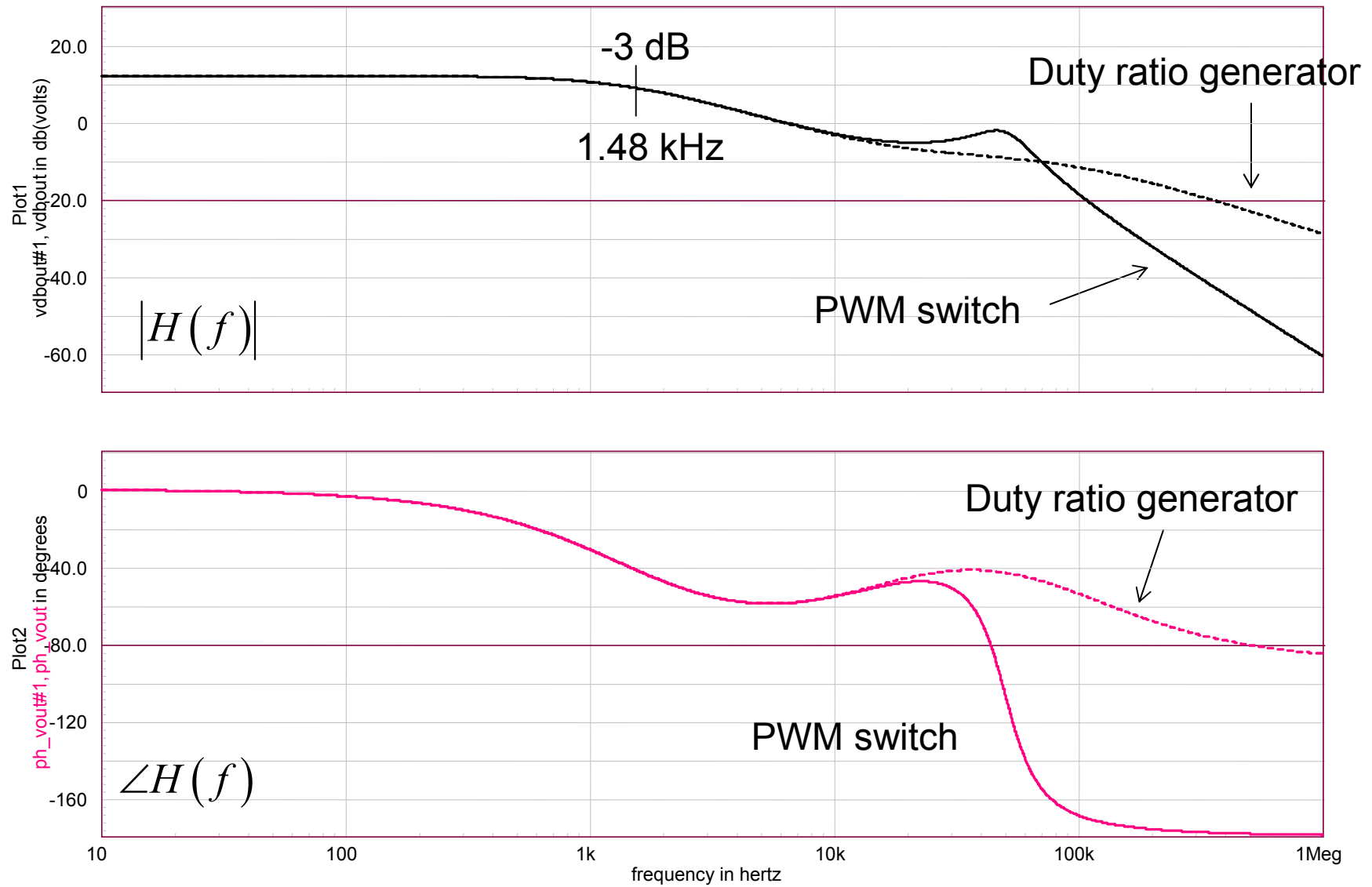Power stage response alone – hi-freq. response differs because of sub-harmonic poles




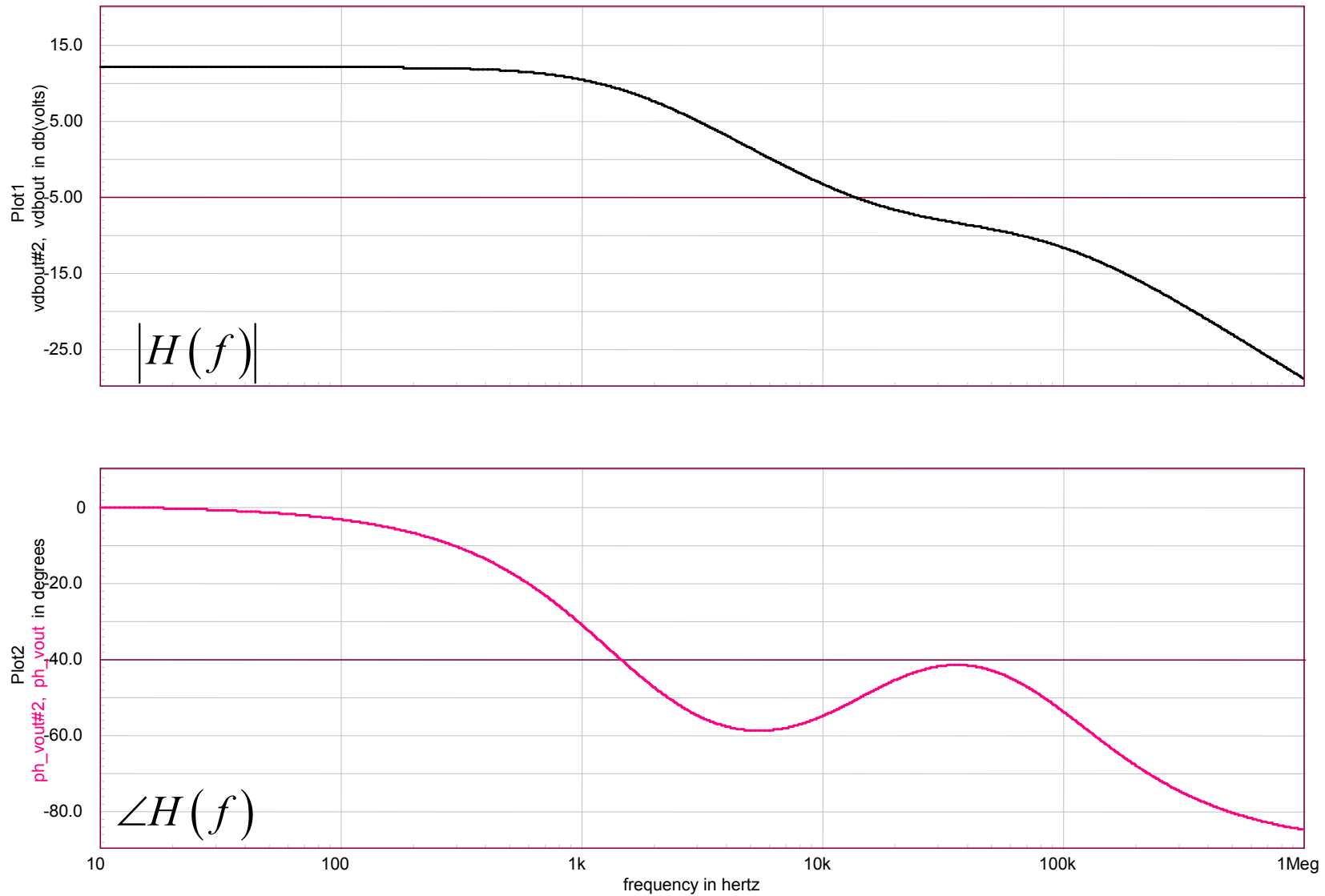
PWM switch without CS cap. versus duty ratio generator: no difference



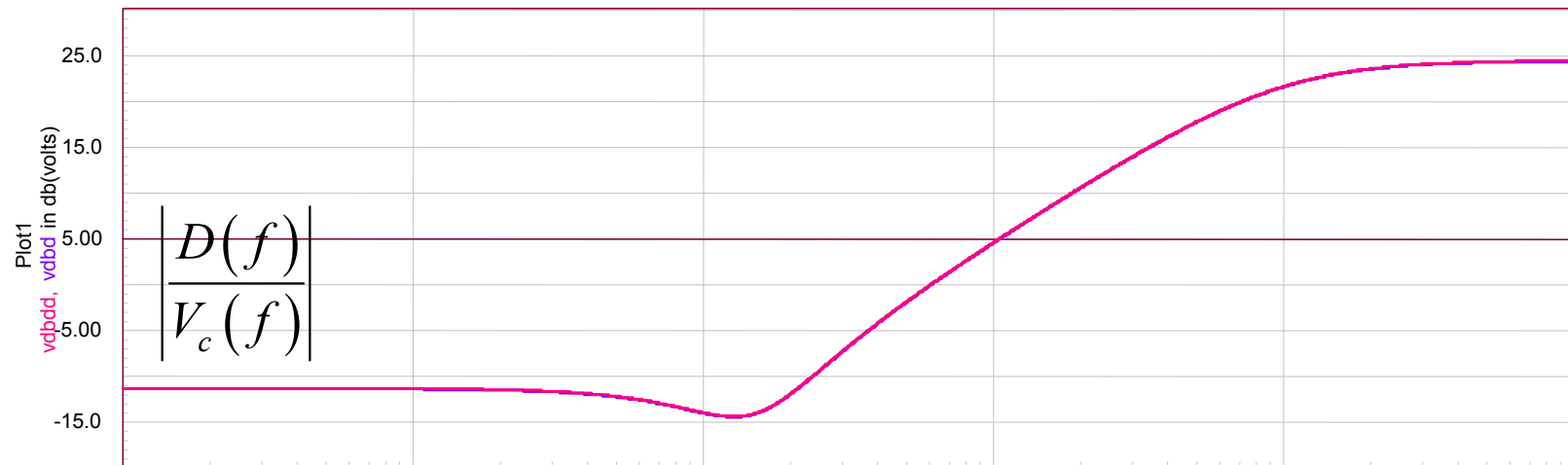


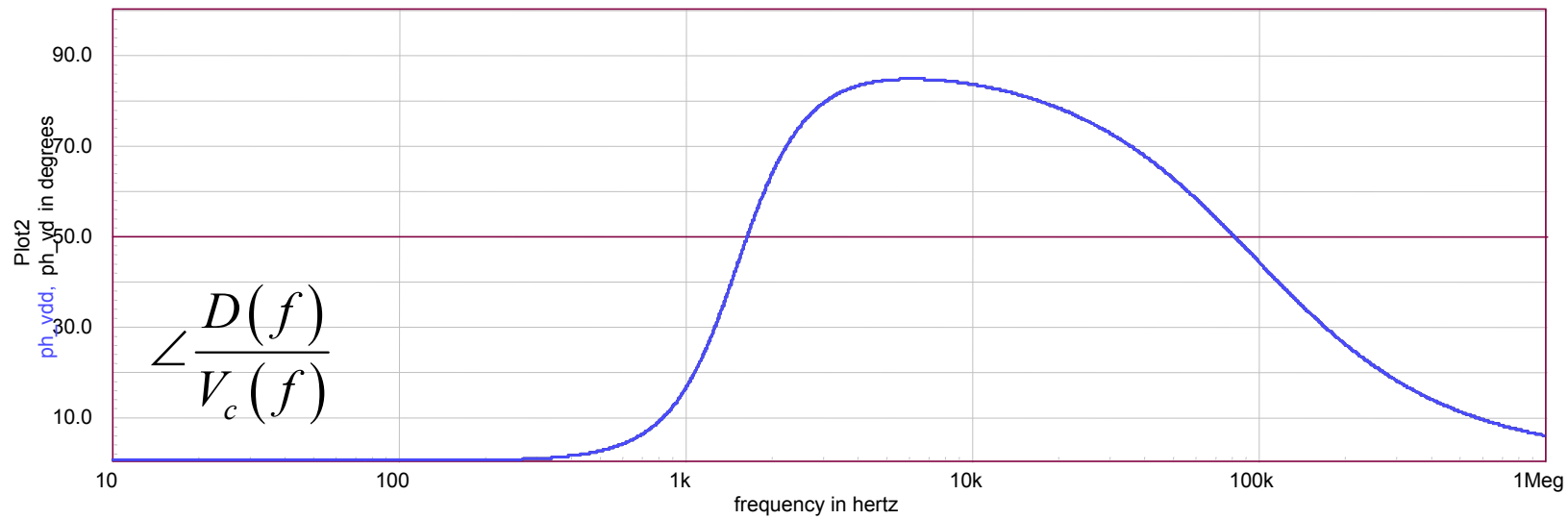Large and linearized response of the V_c to D generator



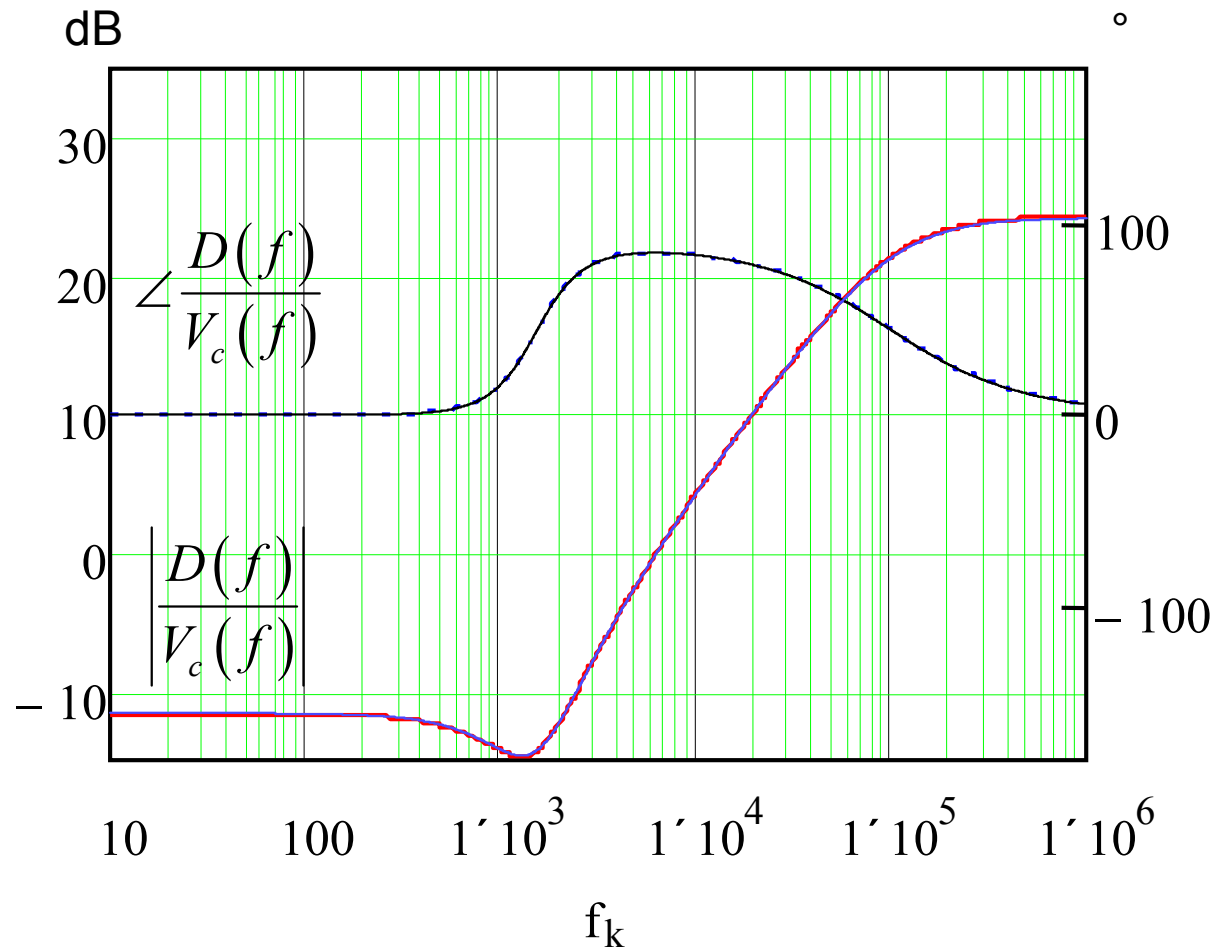

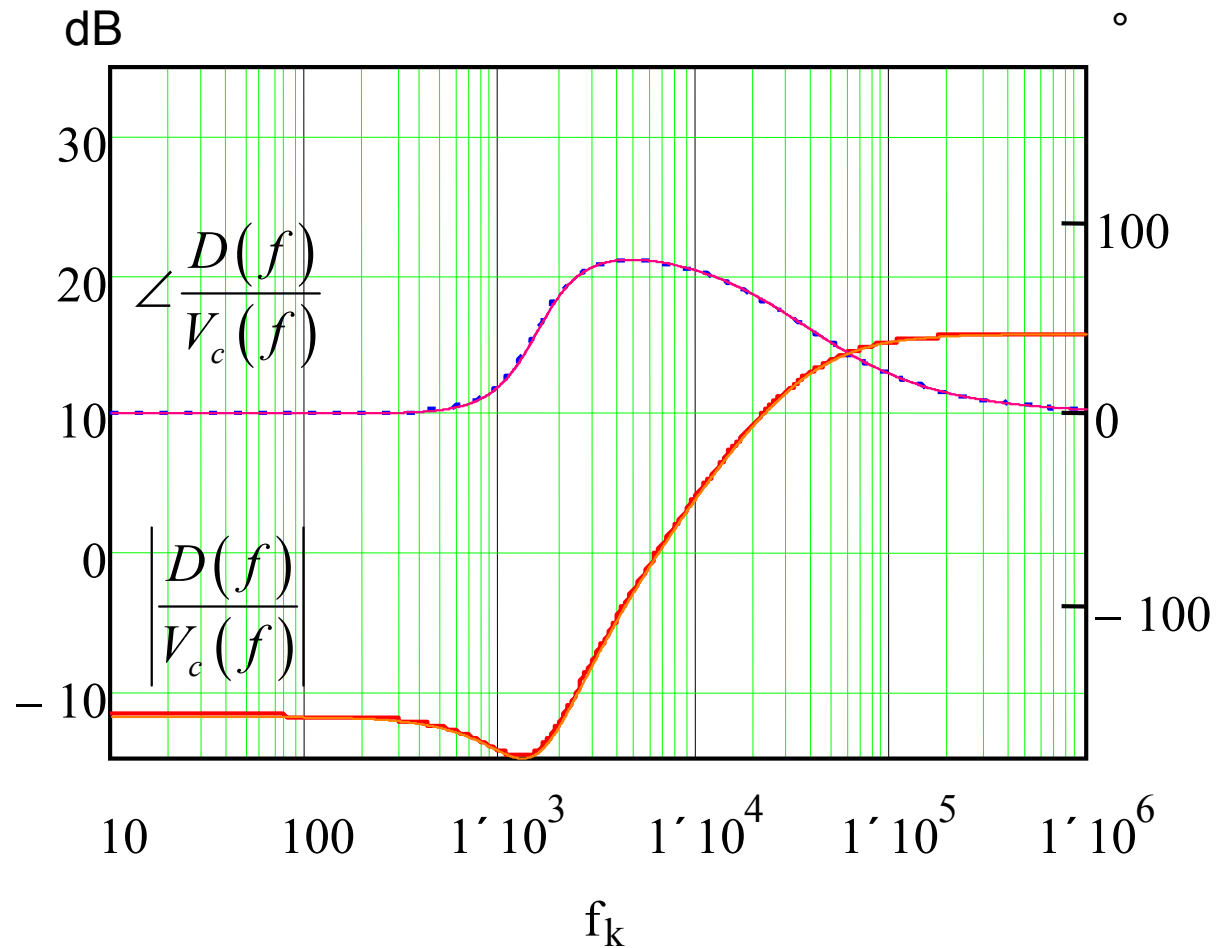
Ac response of duty ratio generator, SPICE versus Mathcad, $S_a = 0$



Ac response of duty ratio generator, SPICE versus Mathcad, $S_a = 10$ kV/s



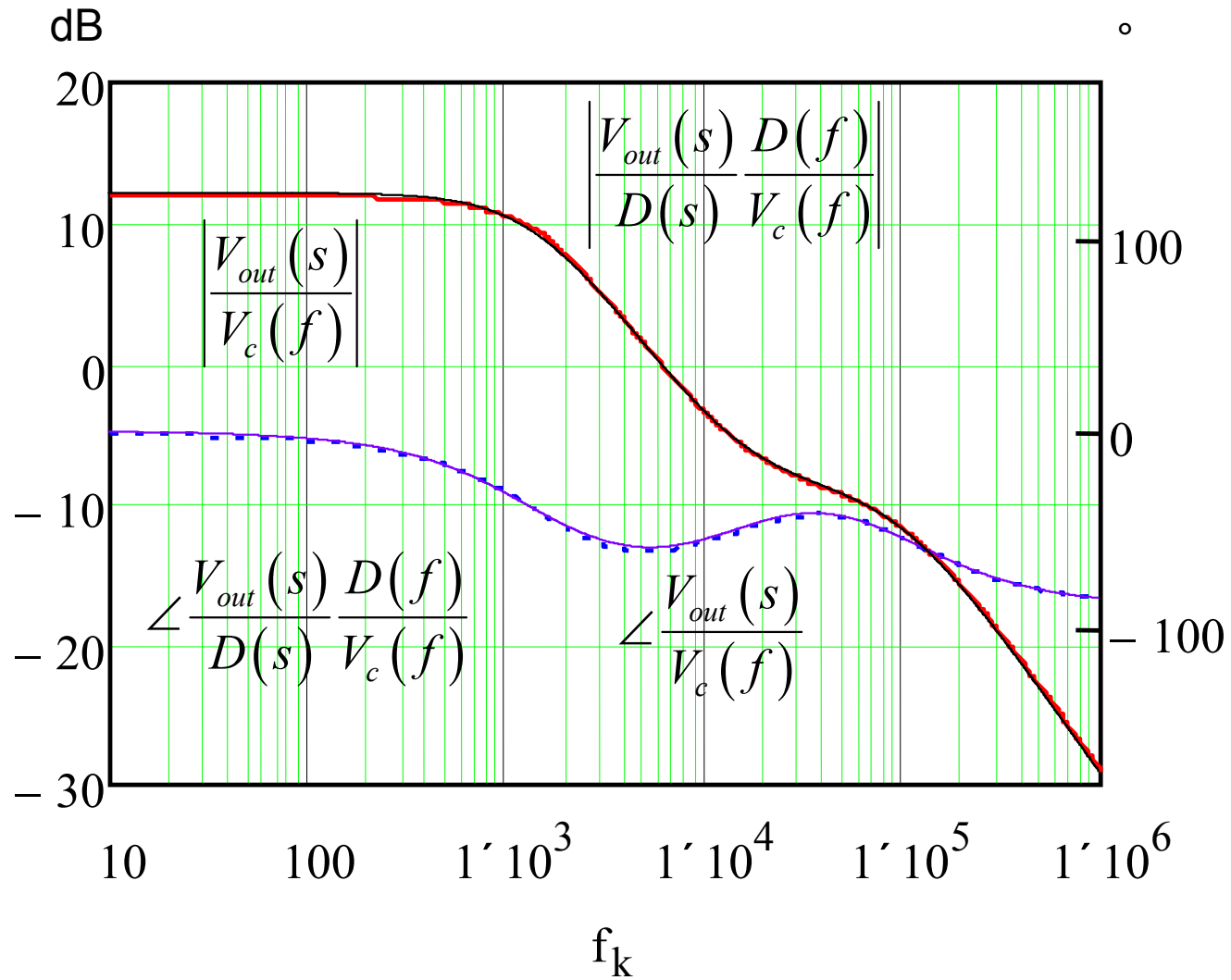Power stage CCM Buck CM final response of cascaded blocks versus large-signal model – $S_a = 0$



Power stage CCM Buck CM final response of cascaded blocks versus large-signal model – $S_a = 10 \text{ kV/s}$

