
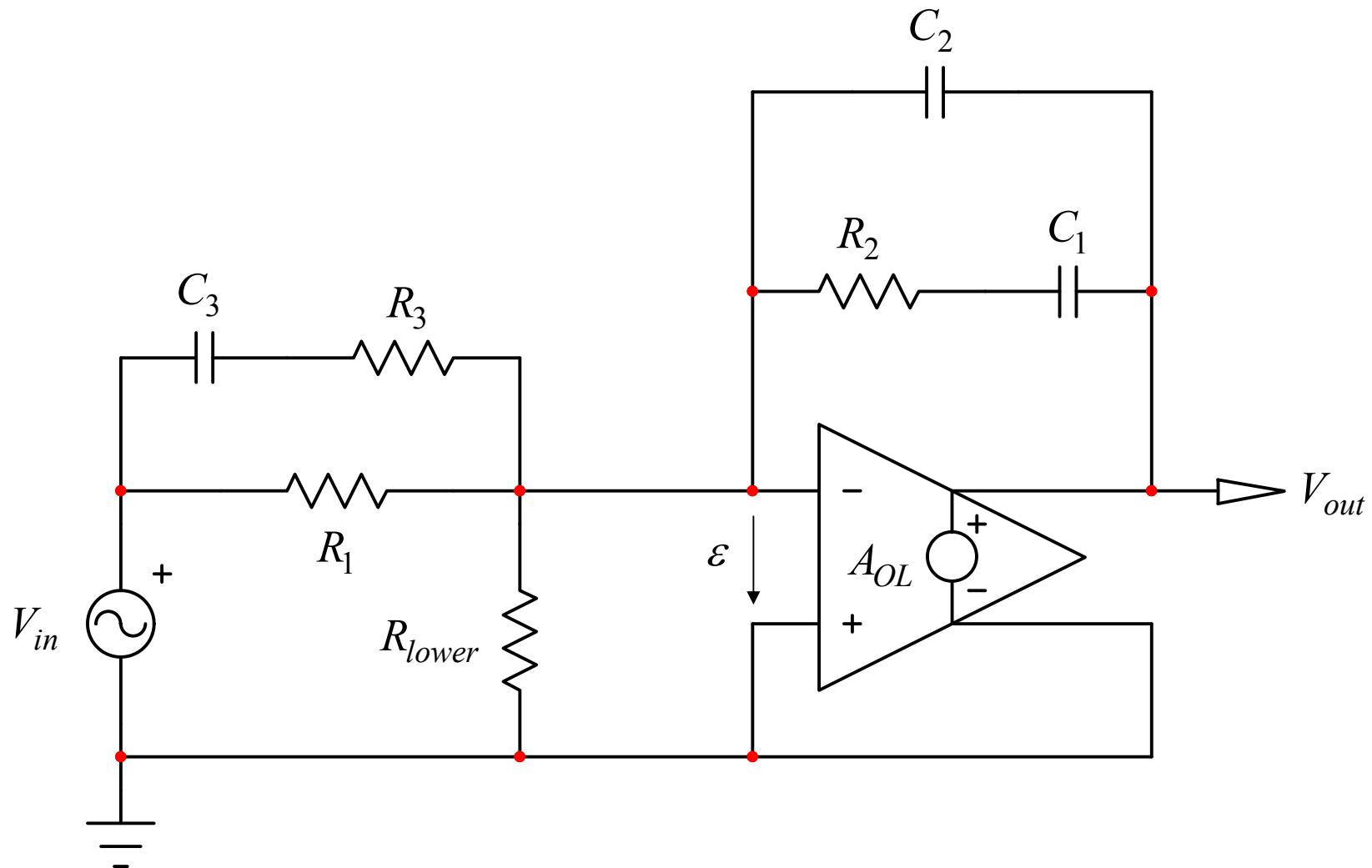


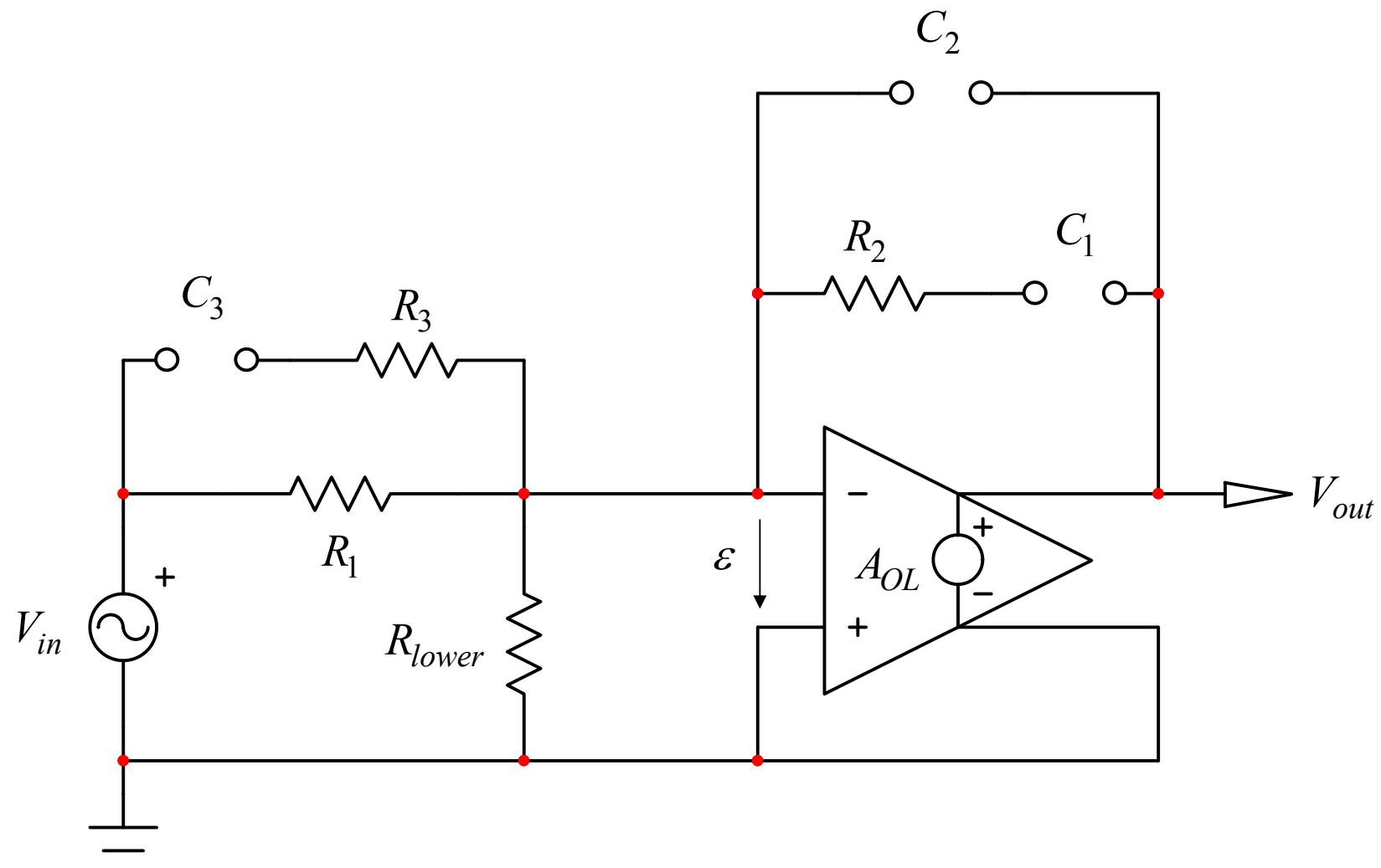FACTs applied to a type 3 compensator – Christophe Basso – August 2017




Dc gain, $s = 0$, open all the caps:




$$H_0 = -\frac{R_{lower}}{R_{lower} + R_1} A_{OL}$$

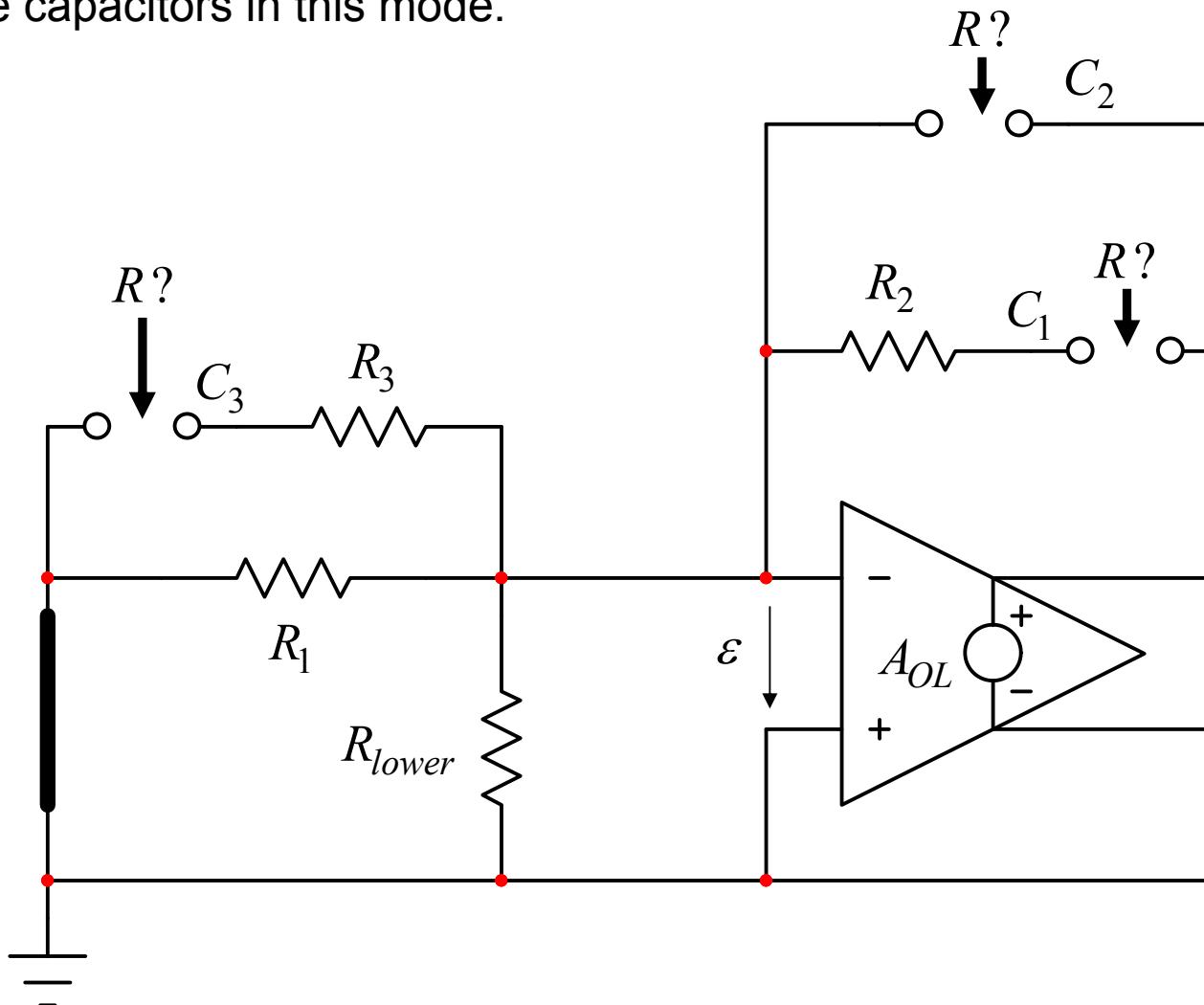
Reduce the excitation (V_{in}) to 0 V and determine the resistances seen from the capacitors in this mode.


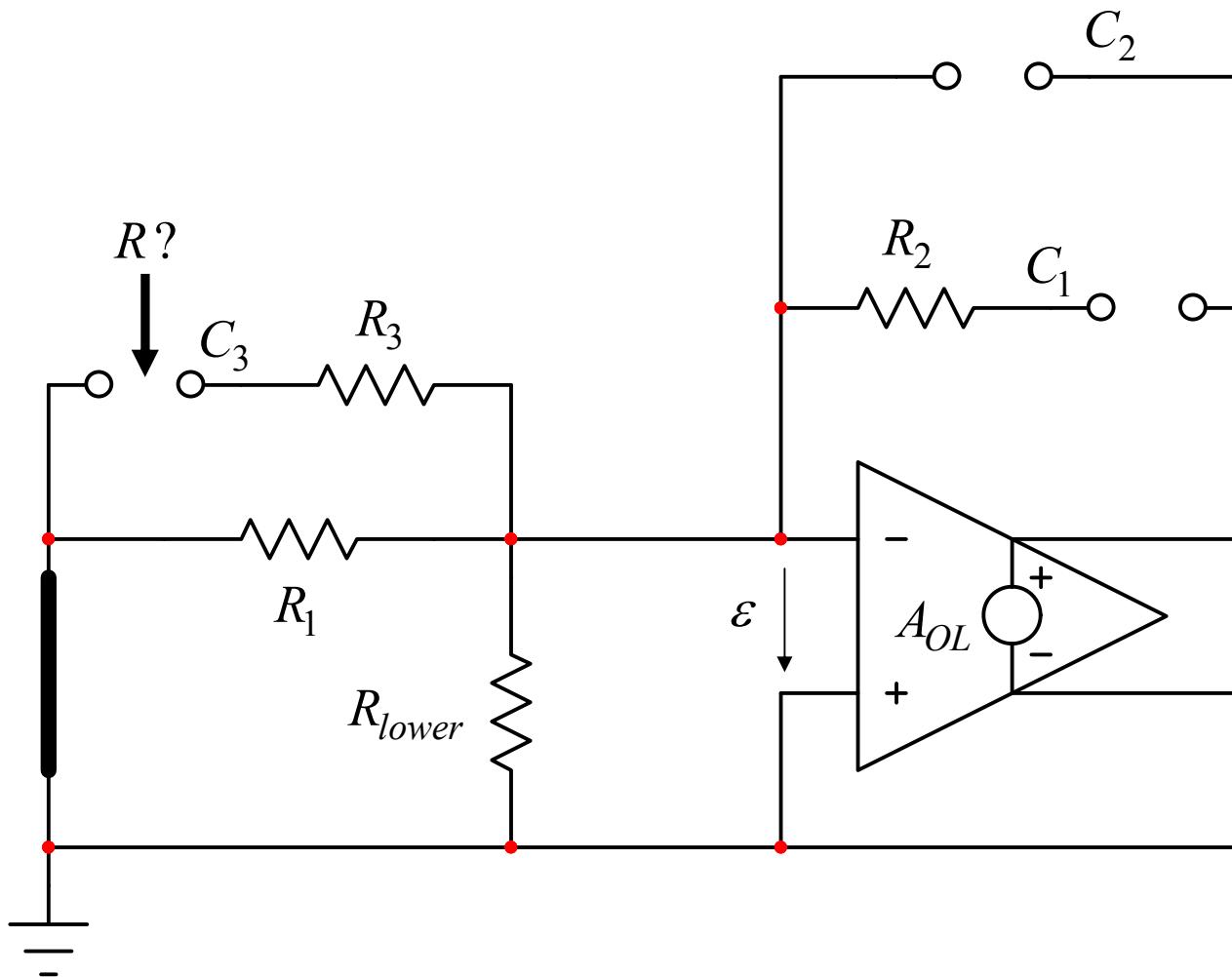
$$\tau_3 = C_3 (R_3 + R_1 \parallel R_{lower})$$




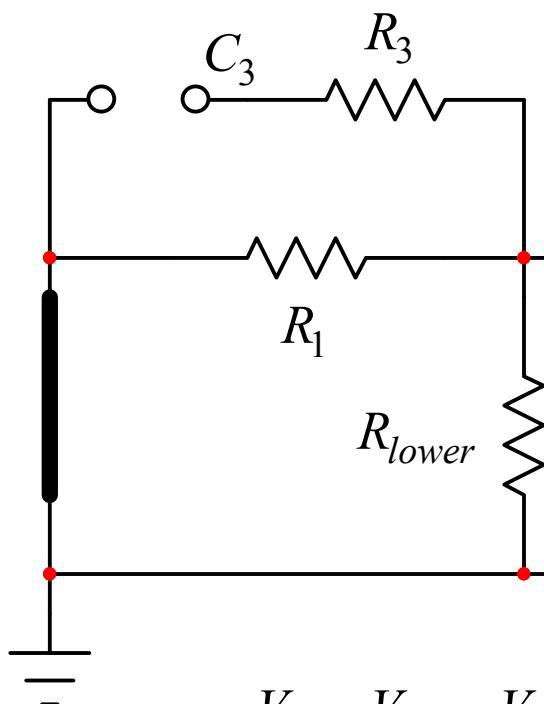
$$\tau_2 = C_2 \left(R_1 \parallel R_{lower} \right) (1 + A_{OL})$$



$$V_T = V_{(b)} - V_{(a)} = \varepsilon A_{OL} - (-\varepsilon) = \varepsilon (1 + A_{OL})$$
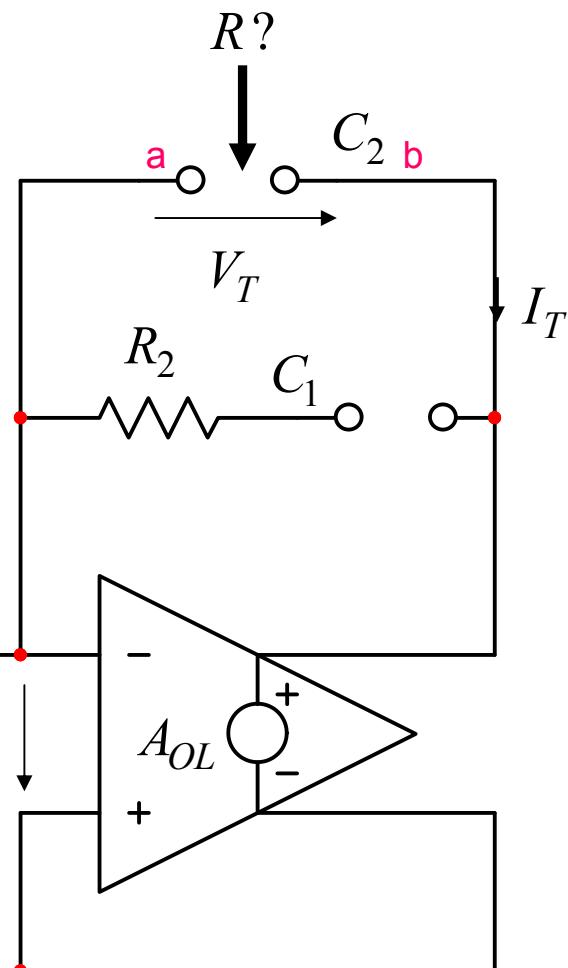
$$\varepsilon = I_T (R_1 \parallel R_{lower})$$



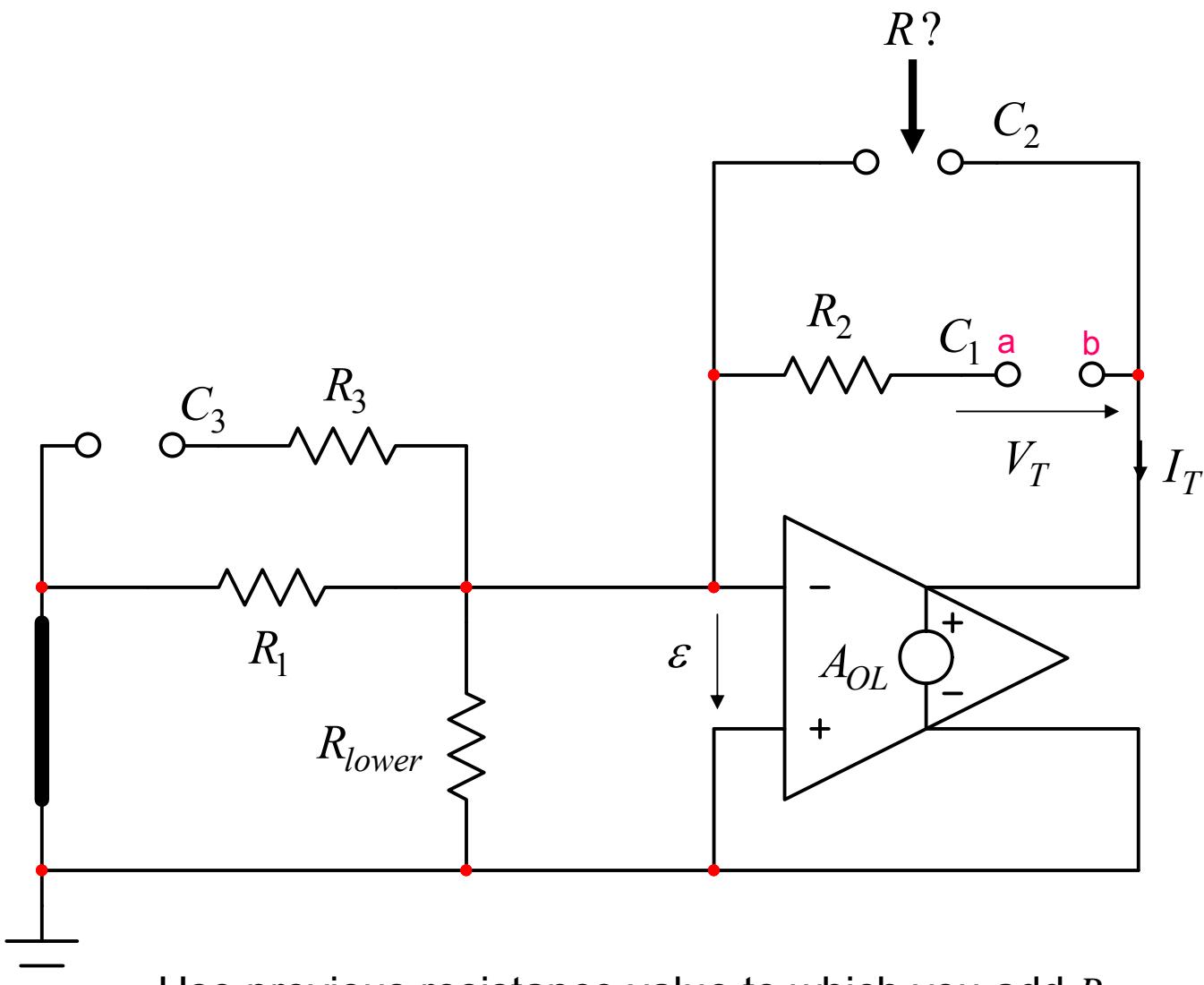

Use previous resistance value to which you add R_2



$$\tau_1 = C_1 \left[(R_1 \parallel R_{lower}) (1 + A_{OL}) + R_2 \right]$$

You can form b_1 for the denominator

$$b_1 = \tau_1 + \tau_2 + \tau_3$$

$$= C_1 \left[(R_1 \parallel R_{lower}) (1 + A_{OL}) + R_2 \right] + C_2 (R_1 \parallel R_{lower}) (1 + A_{OL}) + C_3 (R_3 + R_1 \parallel R_{lower})$$
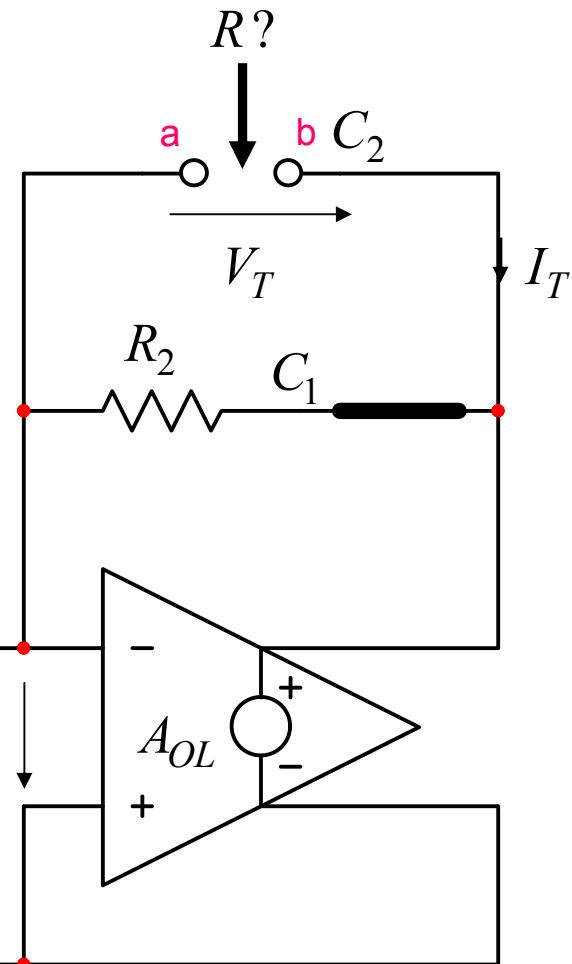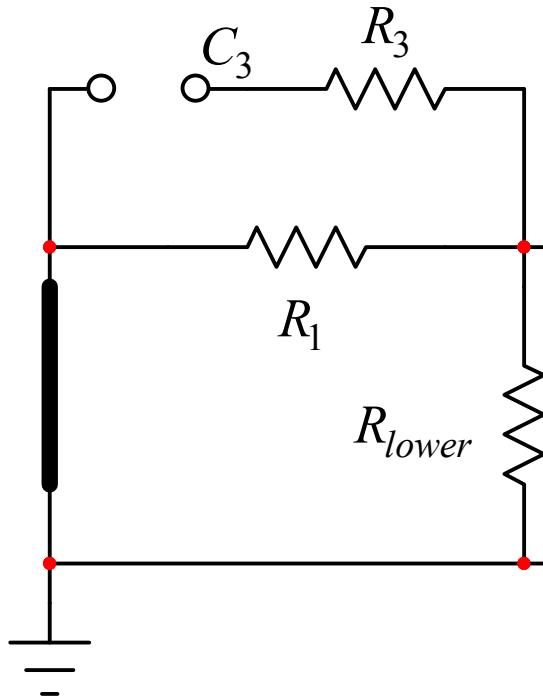
$$b_2 = \tau_1 \tau_2^1 + \tau_1 \tau_3^1 + \tau_2 \tau_3^2 = \tau_1 \tau_2^1 + \tau_1 \tau_3^1 + \tau_3 \tau_2^3$$





$\tau_2^1 \leftarrow$ short
 $\tau_2 \leftarrow R?$

$$V_T = V_{(b)} - V_{(a)} = \varepsilon A_{OL} - (-\varepsilon) = \varepsilon (1 + A_{OL})$$

$$\varepsilon = \left(I_T - \frac{V_T}{R_2} \right) (R_1 \parallel R_{lower})$$

$$\tau_2^1 = C_2 \left[\frac{R_2 (R_1 \parallel R_{lower}) (1 + A_{OL})}{R_2 + (R_1 \parallel R_{lower}) (1 + A_{OL})} \right]$$
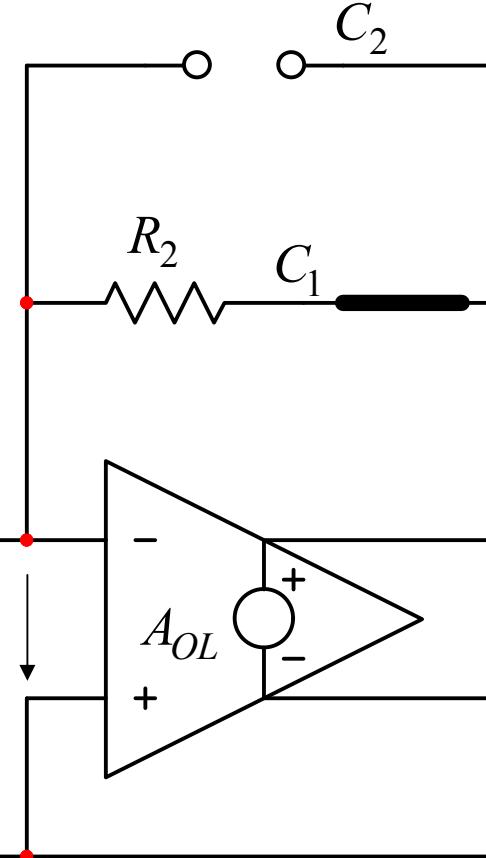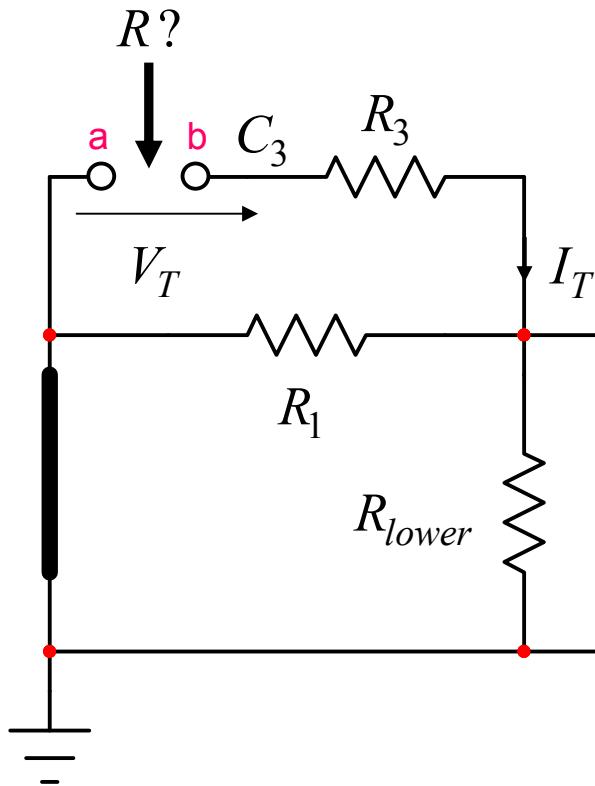
$$\tau_3^1 = C_3 \left[\frac{R_2 (R_1 \parallel R_{lower})}{R_2 + (R_1 \parallel R_{lower}) (1 + A_{OL})} + R_3 \right]$$




$\tau_3^1 \leftarrow$ short
 $\tau_3^1 \leftarrow R?$

In this configuration, IT crosses the op amp but not R_1 and R_{lower} .


$$V_T = V_{(b)} - V_{(a)} = V_{(b)}$$


$$\tau_3^2 = C_3 R_3$$

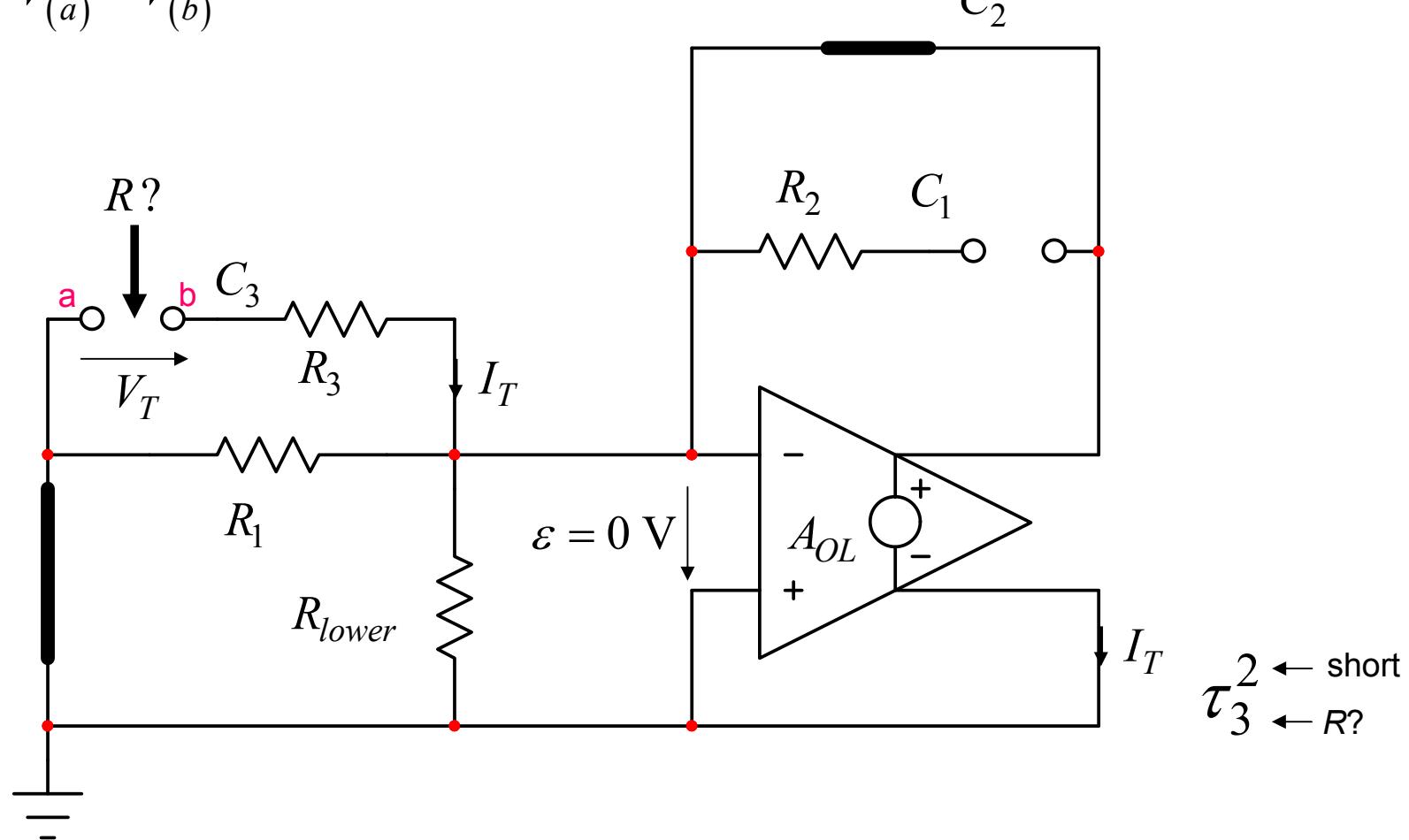

$$b_3 = \tau_1 \tau_2^1 \tau_3^{12}$$

$$\tau_3^{12} = C_3 R_3$$

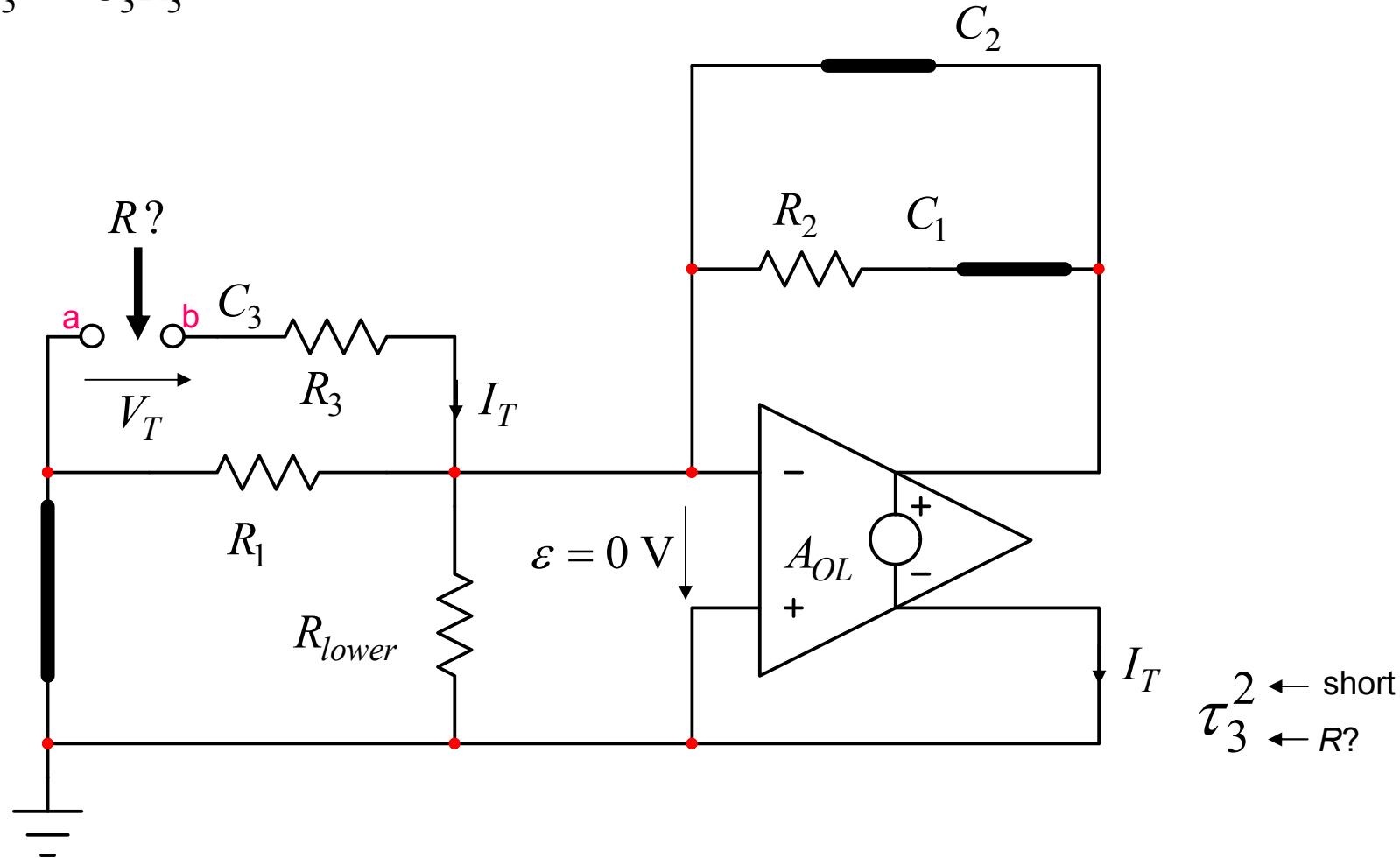

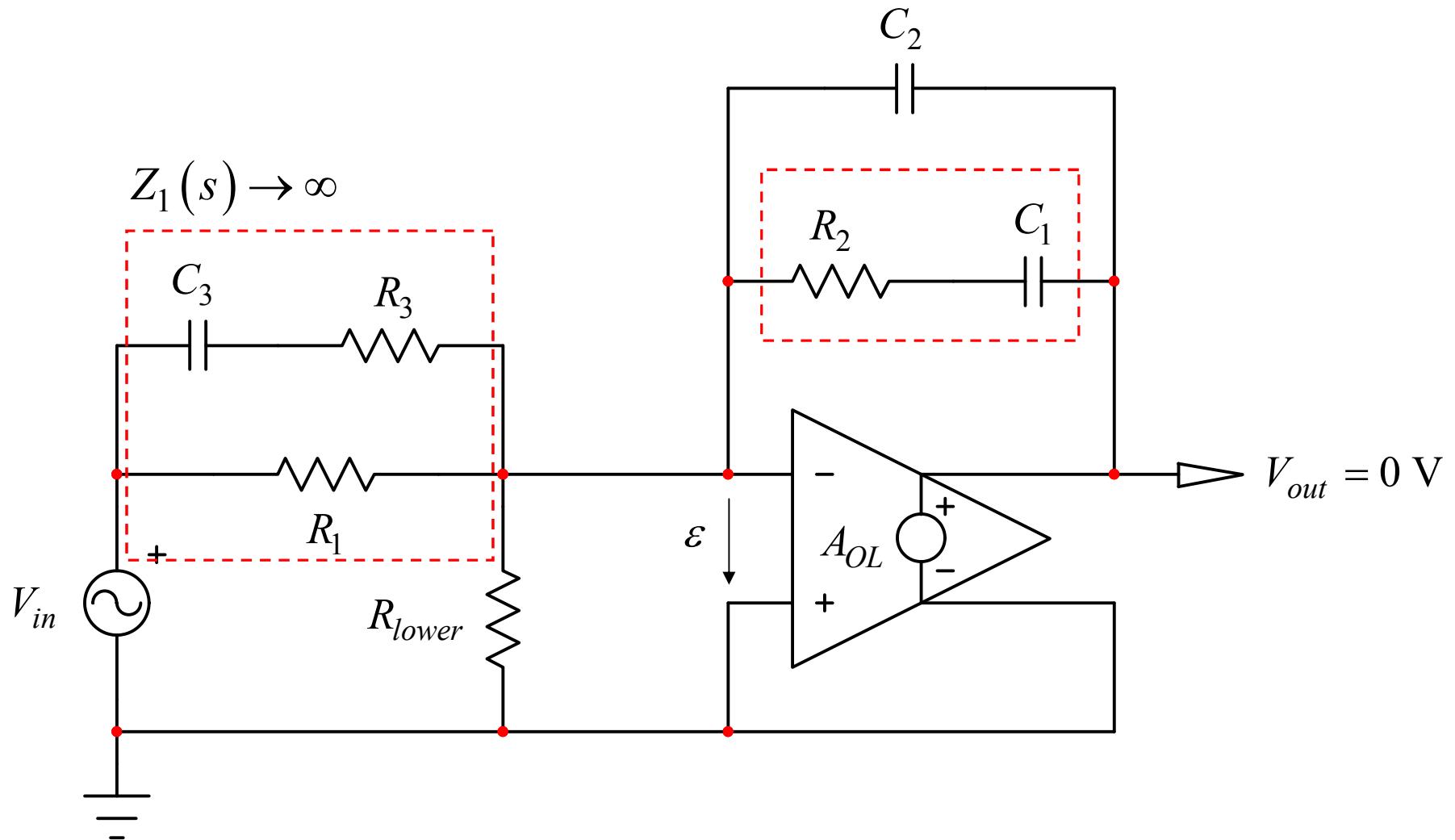

$$\left. \begin{array}{l}
 Z_1(s) \rightarrow \infty \\
 \frac{N(s)}{D(s)} \rightarrow \infty \\
 D(s) = 0
 \end{array} \right\} \quad D(s) = 1 + sC_3(R_3 + R_1) \quad \downarrow \quad Z_2(s) = 0 \rightarrow R_2 + \frac{1}{sC_1} = 0 \quad \downarrow \quad \omega_{z_1} = \frac{1}{C_3(R_3 + R_1)} \quad \omega_{z_2} = \frac{1}{C_1R_2}$$

The final expressions is thus:



$$H(s) = H_0 \frac{\left(1 + \frac{s}{\omega_{z_1}}\right)\left(1 + \frac{s}{\omega_{z_2}}\right)}{1 + b_1 s + b_2 s^2 + b_3 s^3}$$

$$H_0 = -\frac{R_{lower}}{R_{lower} + R_1} A_{OL}$$



$$\omega_{z_2} = \frac{1}{C_1 R_2} \quad \omega_{z_1} = \frac{1}{C_3 (R_3 + R_1)}$$

The simplified expressions is:
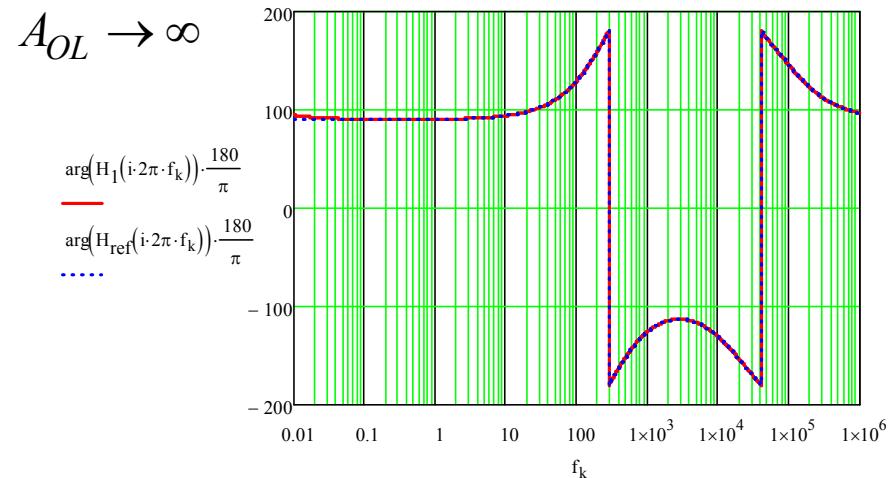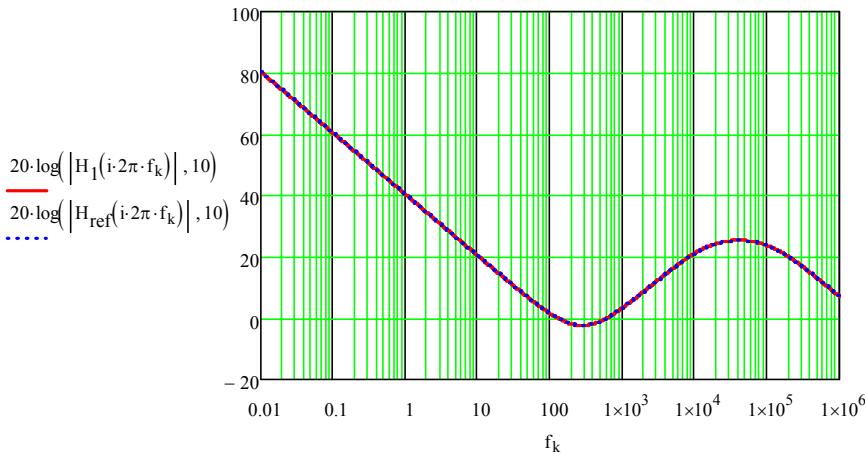
$$H(s) = -\frac{R_2 C_1}{R_1 (C_1 + C_2)} \frac{1 + \frac{1}{s R_2 C_1}}{1 + s R_2 \frac{C_1 C_2}{C_1 + C_2}} \frac{1 + s C_3 (R_1 + R_3)}{1 + s R_3 C_3}$$



$$A_{OL} = 60 \text{ dB}$$

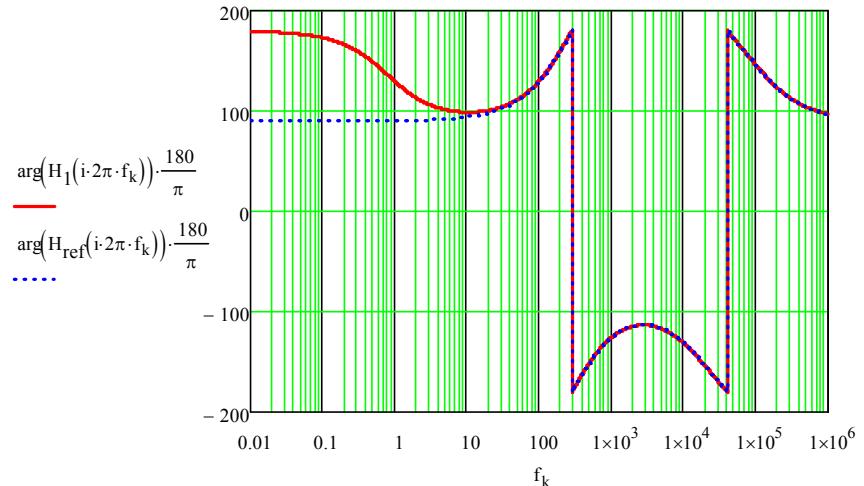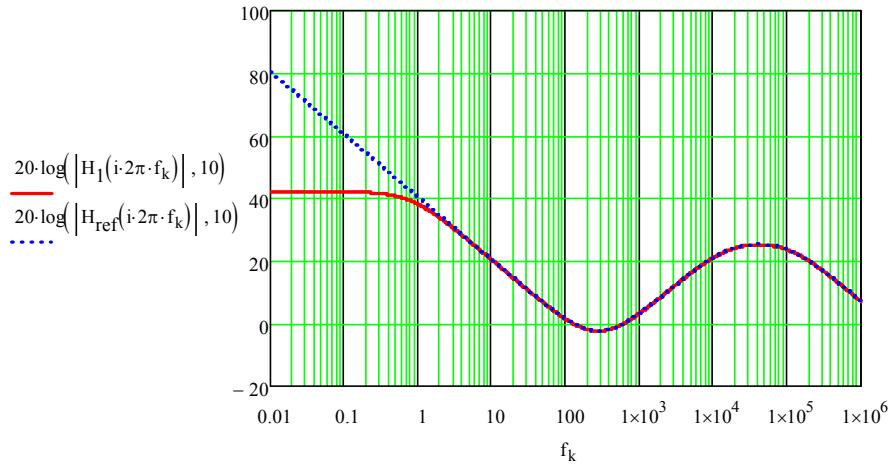

Considering the open-loop gain helps figuring out the role of the resistive network which, in the simplified analysis, does not play a role.

$$H(s) = H_0 \frac{\left(1 + \frac{s}{\omega_{z_1}}\right)\left(1 + \frac{s}{\omega_{z_2}}\right)}{1 + b_1 s + b_2 s^2 + b_3 s^3} \approx -\frac{\frac{R_{lower}}{R_{lower} + R_1} A_{OL}}{b_1 \omega_{z_1}} \frac{\left(1 + \frac{\omega_{z_1}}{s}\right)\left(1 + \frac{s}{\omega_{z_2}}\right)}{\left(1 + \frac{s}{Q\omega_0}\right)\left(1 + \frac{sQ}{\omega_o}\right)}$$

$$Q = \frac{\sqrt{b_1 b_3}}{b_2}$$

$$\omega_o = \sqrt{\frac{b_1}{b_3}}$$