

# ON Semiconductor

## The “PWM Switch” in mode transitioning SPICE models

*PCIM Germany 2005*

*Christophe Basso - Application Manager*



ON Semiconductor™

### *Agenda*

- ❑ Why average simulations?
- ❑ What techniques already exist?
- ❑ The PWM Switch concept
- ❑ The voltage-mode case
- ❑ The current-mode case
- ❑ Checking *averaged* model's validity
- ❑ Conclusion





## The “PWM Switch” in mode transitioning SPICE models

---
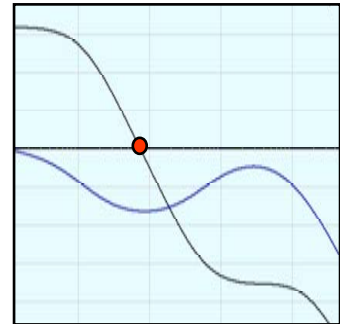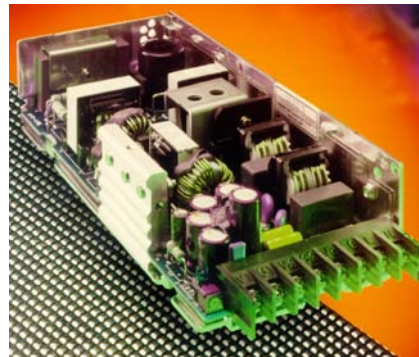
### Why average simulations?


- Unveil open-loop ac response for stabilization purposes
- Helps to assess impact of stray elements variations on stability
- Can predict transient response with large-signal models
- Simulation time is quick as frequency component fades away




# The “PWM Switch” in mode transitioning SPICE models
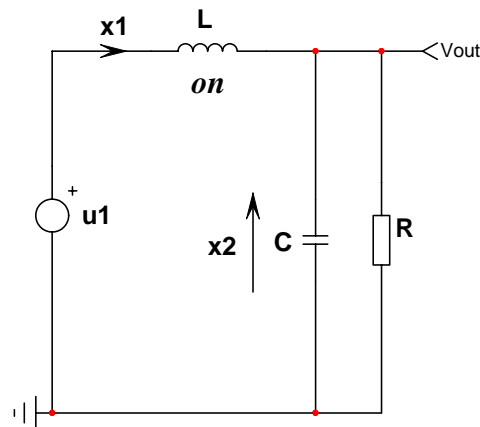
## What techniques already exist?

- ❑ **State-Space Averaging (SSA)**
- ❑ Introduced by Slobodan Čuk in the 80'
- ❑ Long and painful process
- ❑ **Fails** to predict sub-harmonic oscillations


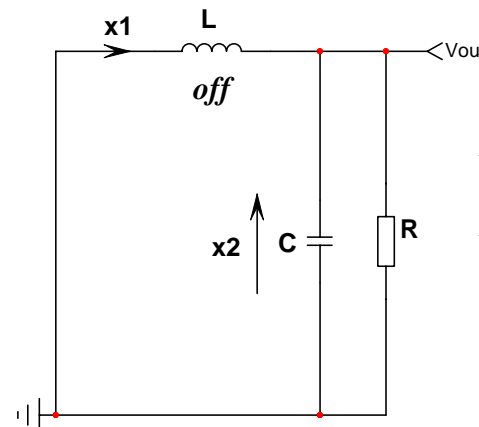
$$\frac{dx1}{dt} = -\frac{1}{L}x2 + \frac{1}{L}u$$
$$\frac{dx2}{dt} = \frac{1}{Cout}x1 - \frac{1}{Rload.Cout}x2$$



$$\frac{dx1}{dt} = -\frac{1}{L}x2$$
$$\frac{dx2}{dt} = \frac{1}{Cout}x1 - \frac{1}{Rload.Cout}x2$$

➡ Apply smoothing process ➡ Linearize





Pffff!



## The “PWM Switch” in mode transitioning SPICE models
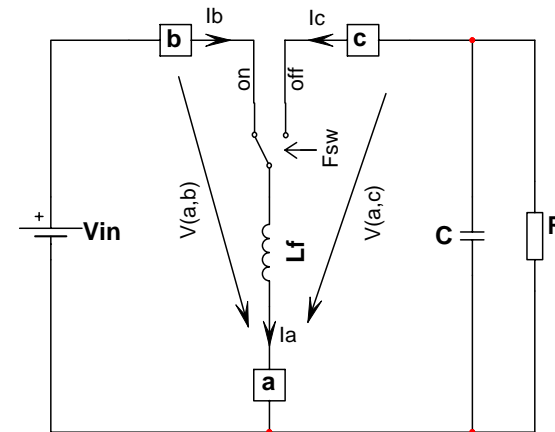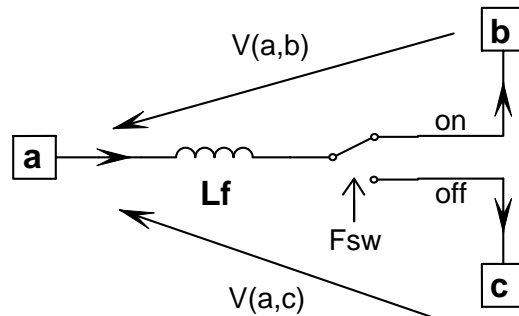
### What techniques already exist?


- ❑ The **GSIM** concept
- ❑ Introduced by Sam Ben-Yaakov in the 90'
- ❑ Easy to derive but not fully invariant (dual inductors converters?)
- ❑ Fully **auto-toggling** mode models
- ❑ **Fails** to predict sub-harmonic oscillations



## The “PWM Switch” in mode transitioning SPICE models
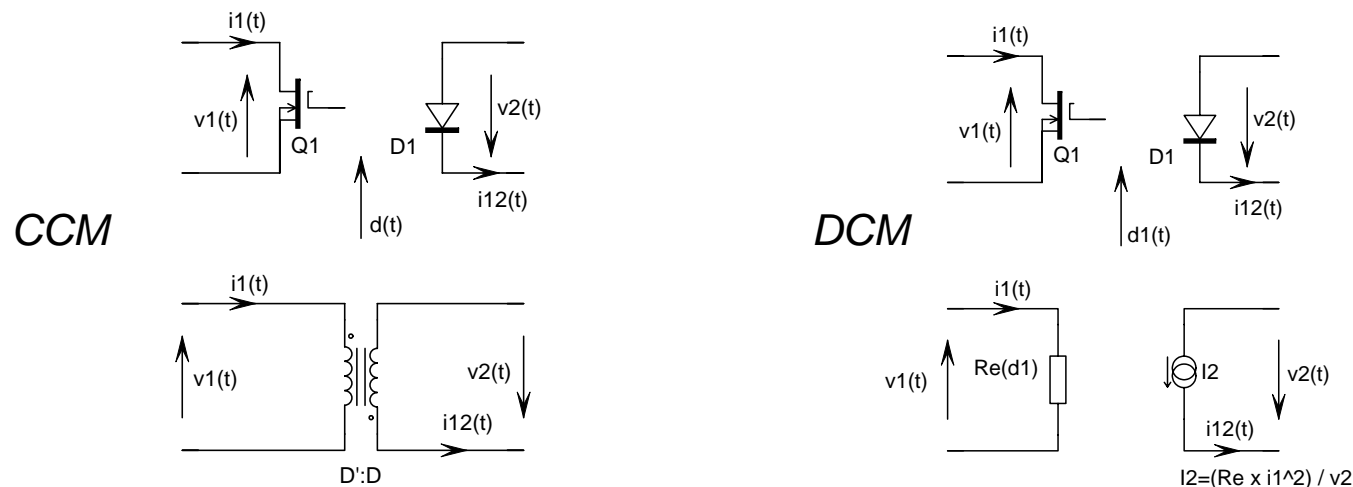
### What techniques already exist?


- ❑ The **CoPEC** model
- ❑ Introduced by the Colorado Power Electronic Center in the 90'
- ❑ Easy to derive and fully invariant
- ❑ Fully **auto-toggling** mode models
- ❑ **Fails** to predict sub-harmonic oscillations



## The “PWM Switch” in mode transitioning SPICE models
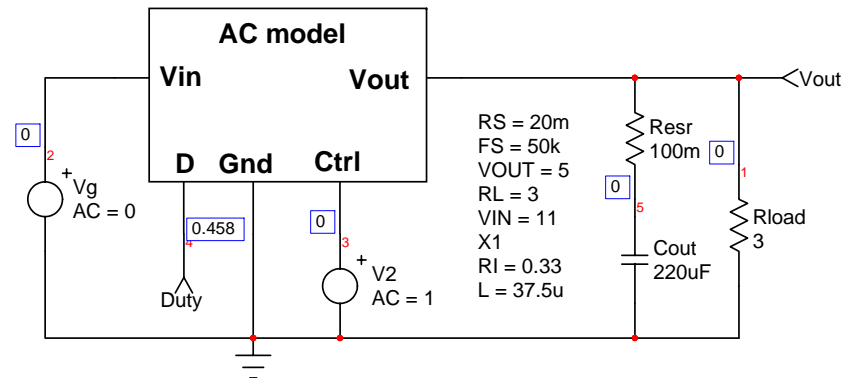
### What techniques already exist?



- The **Ridley** models
- Introduced by Raymond Ridley from VPEC in the 90'
- Use z-transform method
- No** *auto-toggling* mode models
- Can only work in ac
- Can** predict sub-harmonic oscillations in CCM



## The “PWM Switch” in mode transitioning SPICE models
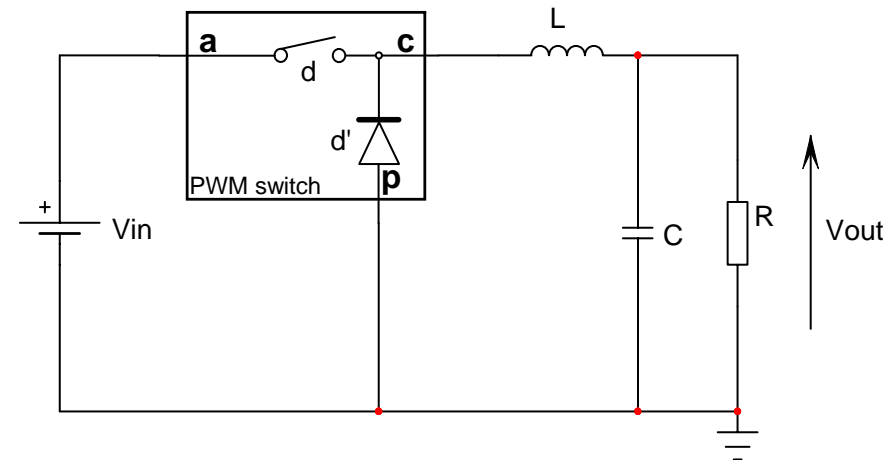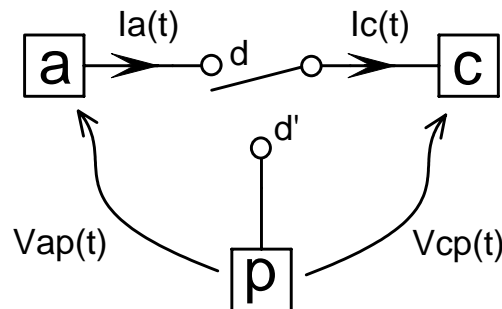
### What techniques already exist?


- ❑ The **PWM Switch**
- ❑ Introduced by Vatché Vorpérian in the mid-80'
- ❑ Easy to derive and fully invariant
- ❑ **No** auto-toggling mode models
- ❑ **Can** predict sub-harmonic oscillations in CCM
- ❑ DCM model was never published!






# The “PWM Switch” in mode transitioning SPICE models

## The PWM Switch concept

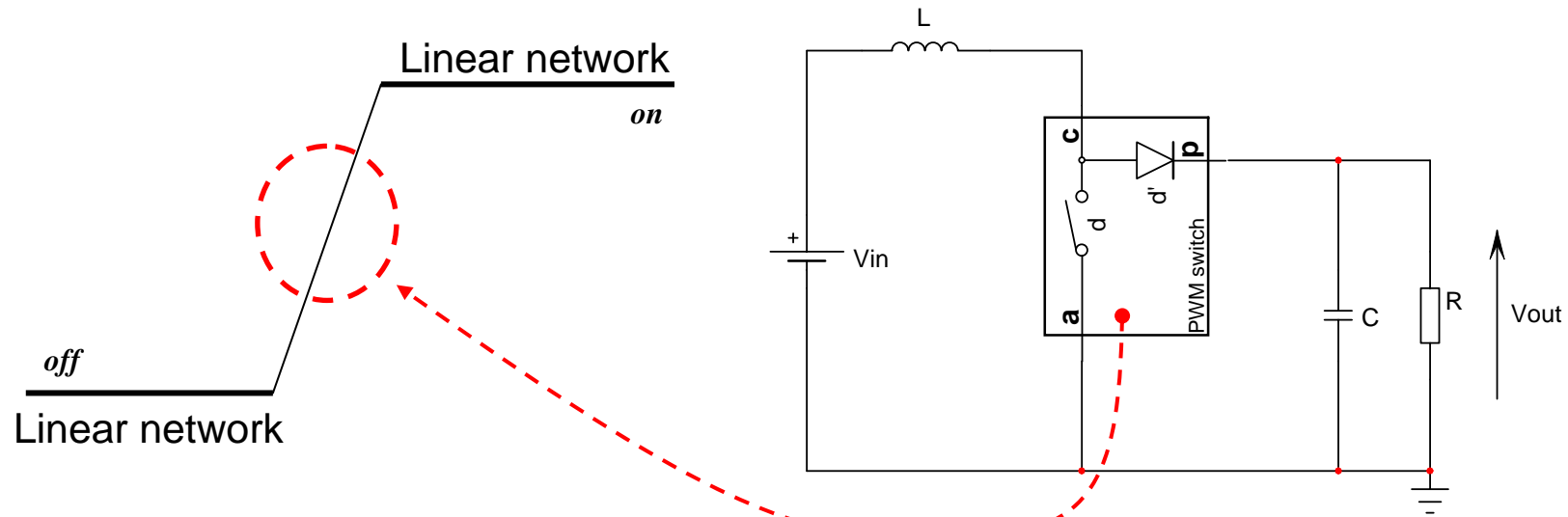



What do you plead?

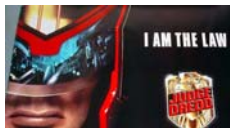diode + transistor = guilty for non-linearity!



# The “PWM Switch” in mode transitioning SPICE models

## The PWM Switch concept

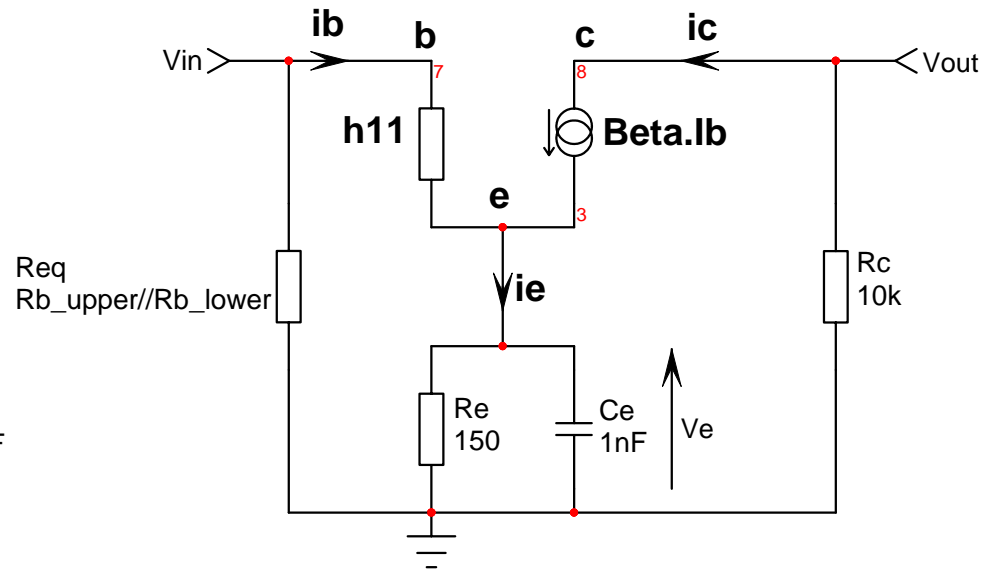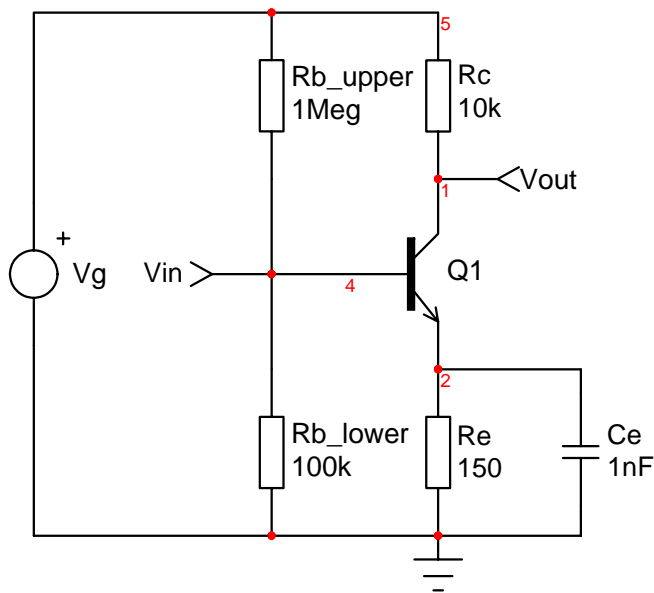

Replace  $Q_1$  by its small-signal model







Remember the *bipolars*  
Ebers-Moll model...





# The “PWM Switch” in mode transitioning SPICE models

## An invariant association

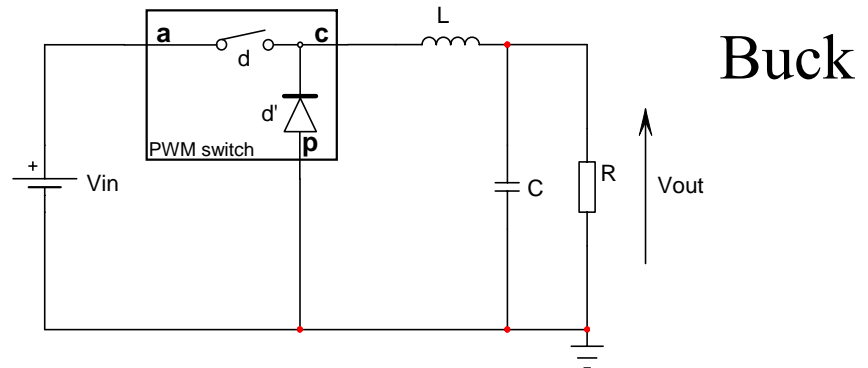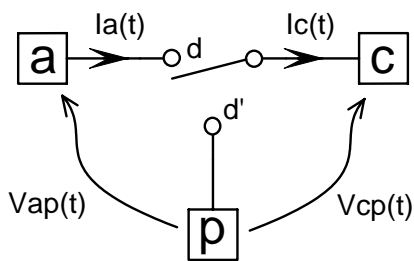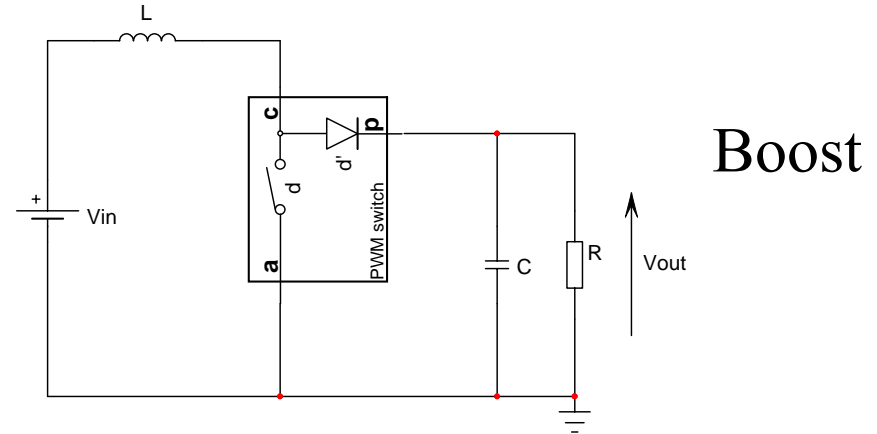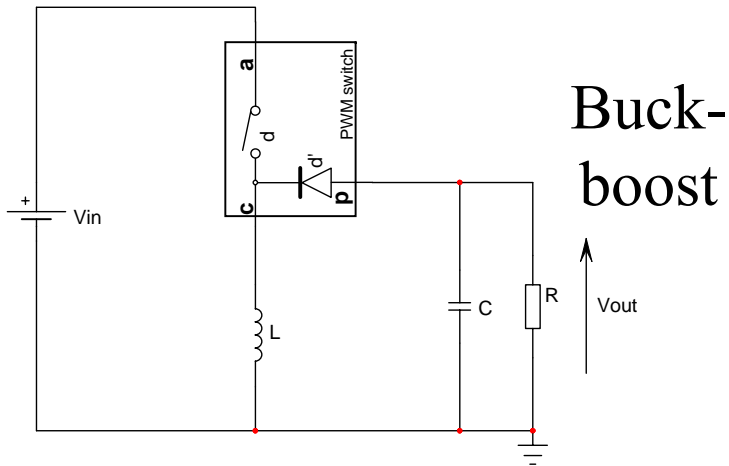


# The “PWM Switch” in mode transitioning SPICE models

## Observe waveforms and *average* them

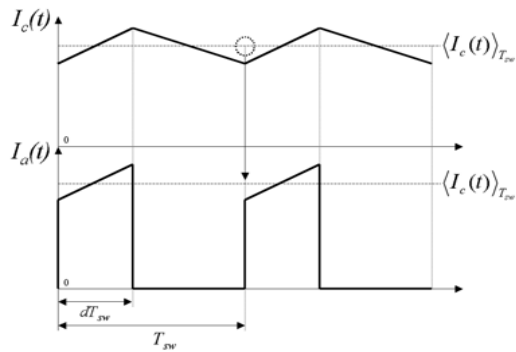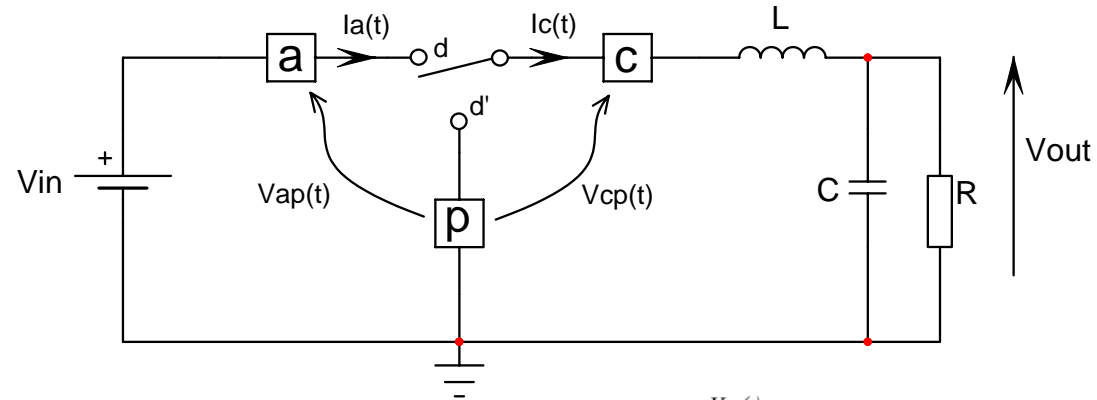
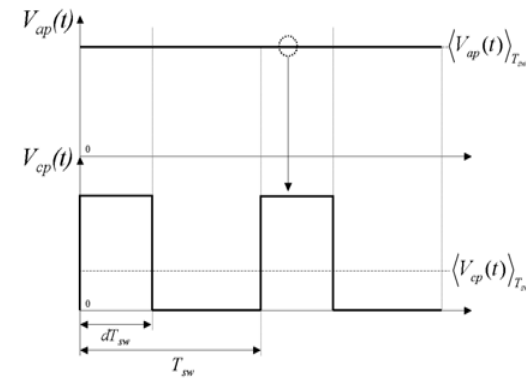
$$\langle I_a(t) \rangle_{T_{sw}} = I_a = \frac{1}{T_{sw}} \int_0^{T_{sw}} I_a(t) dt = d \langle I_c(t) \rangle_{T_{sw}} = d I_c$$




$$\langle V_{cp}(t) \rangle_{T_{sw}} = V_{cp} = \frac{1}{T_{sw}} \int_0^{T_{sw}} V_{cp}(t) dt = (1-d) \langle V_{ap}(t) \rangle_{T_{sw}} = (1-d) V_{ap}$$


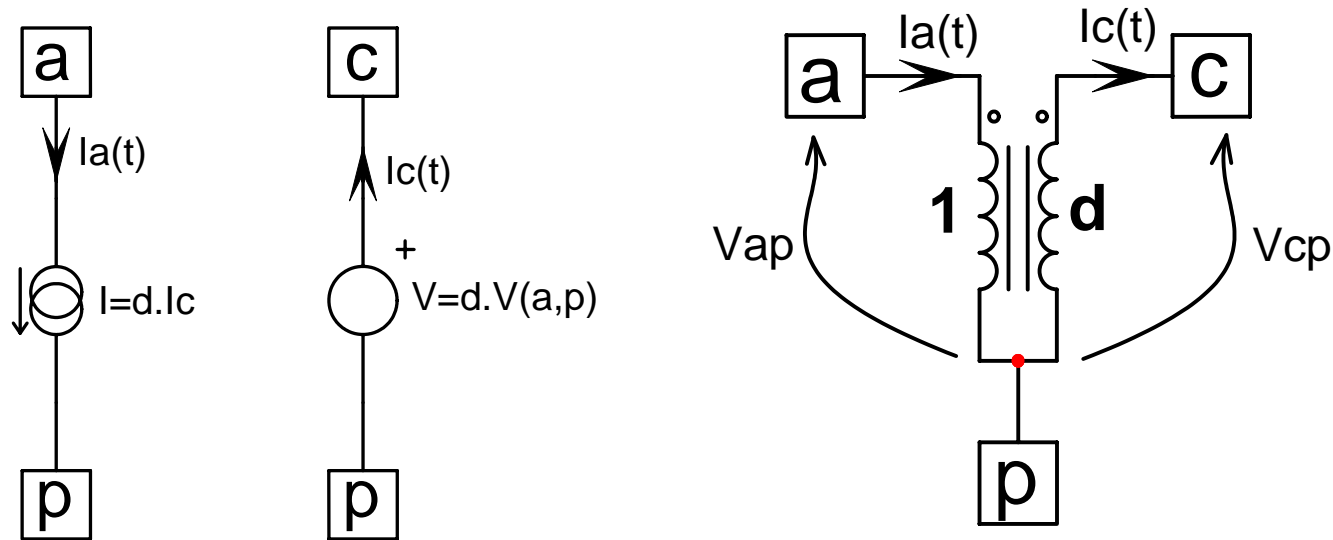
## The “PWM Switch” in mode transitioning SPICE models

PWM Switch model in CCM: a 1:D transformer!




Large-signal (non-linear) model



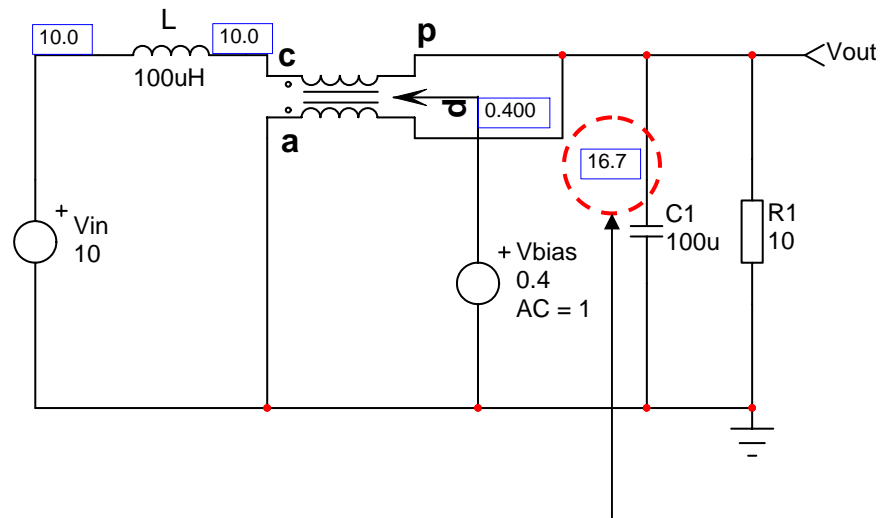
# The “PWM Switch” in mode transitioning SPICE models

Use it immediately, **SPICE** linearizes it for you!





Always verify the dc operating point!

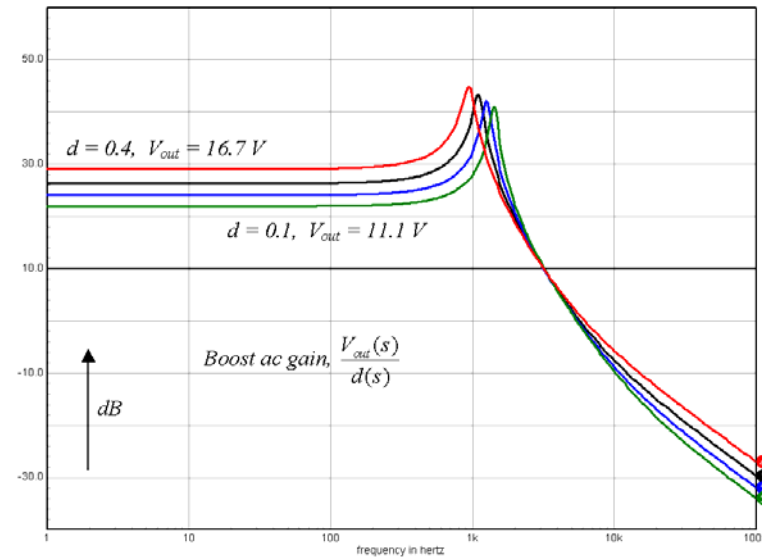

# The “PWM Switch” in mode transitioning SPICE models
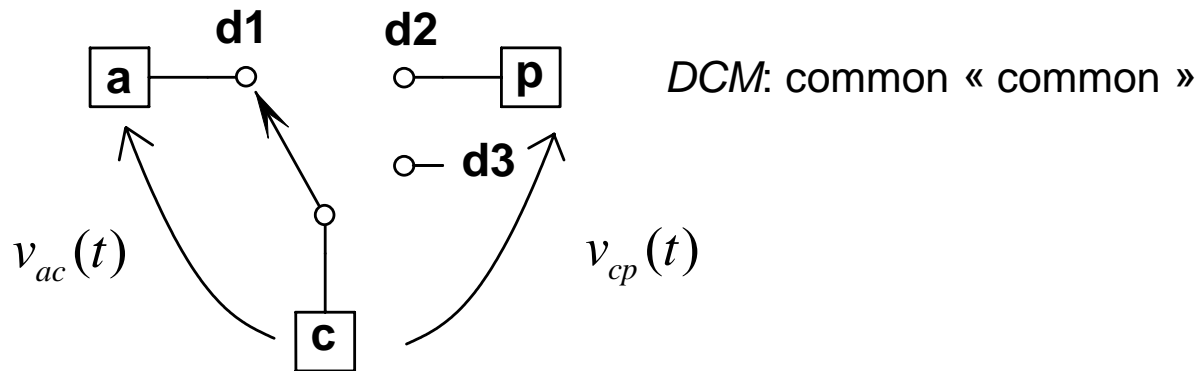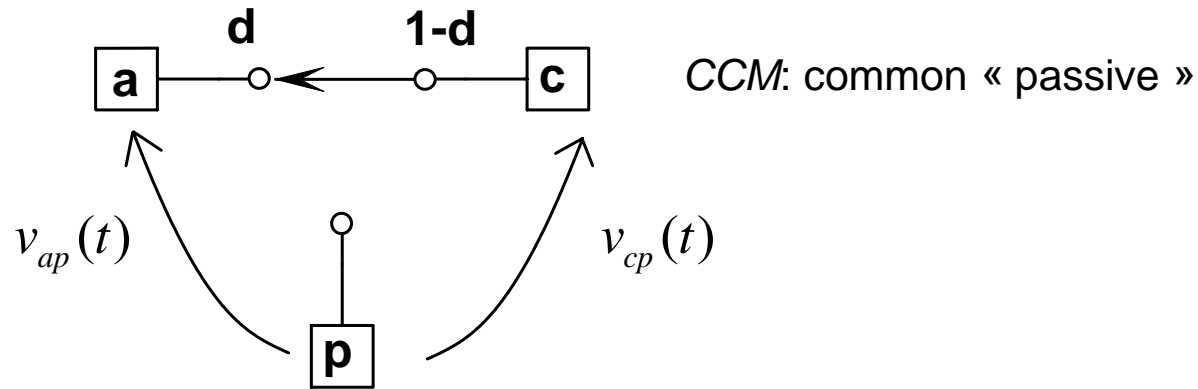
## The original CCM/DCM PWM Switch models




Looks like auto-toggling is impossible...



# The “PWM Switch” in mode transitioning SPICE models

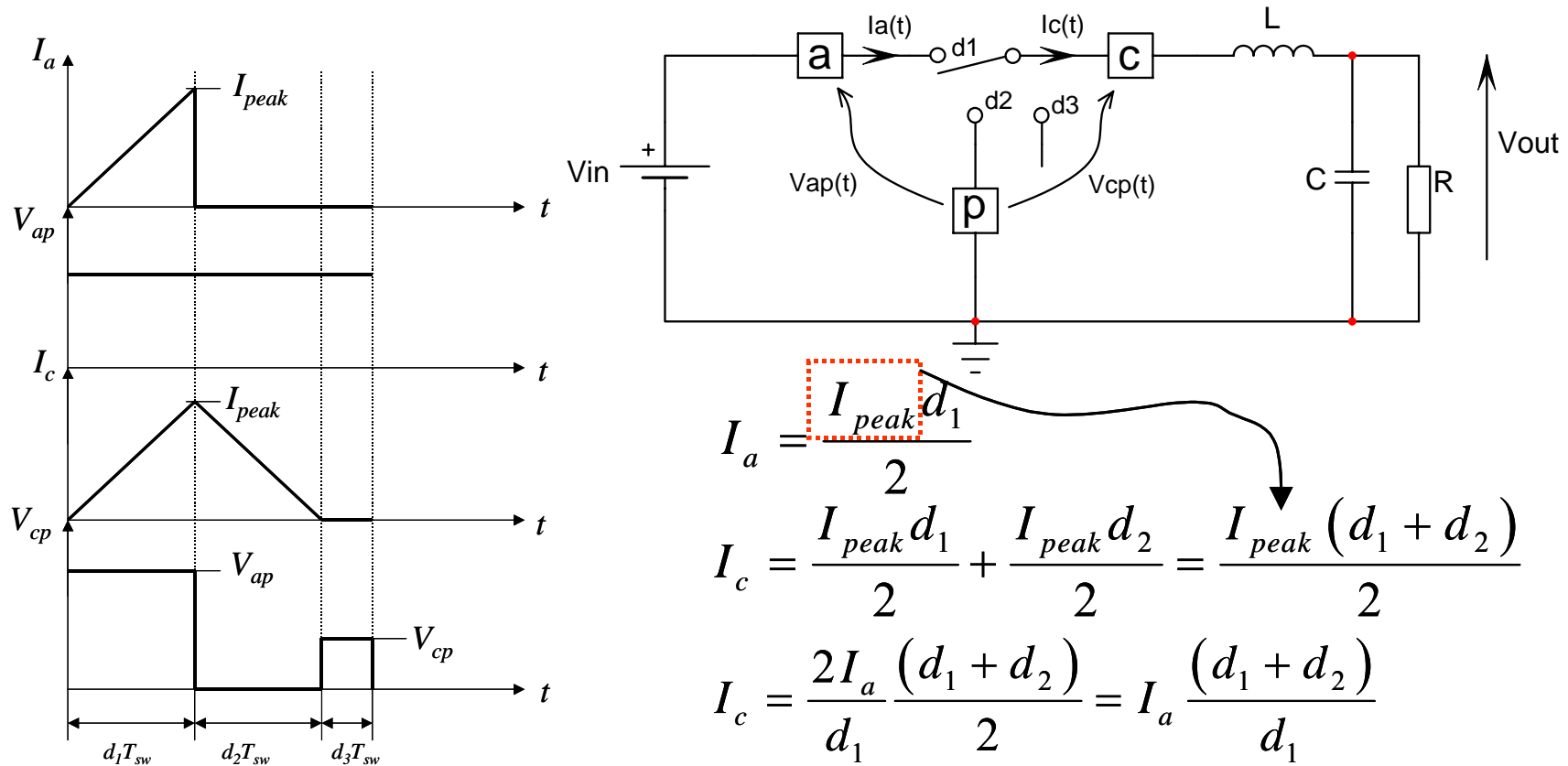
## Deriving the **DCM** PWM Switch in common « passive »




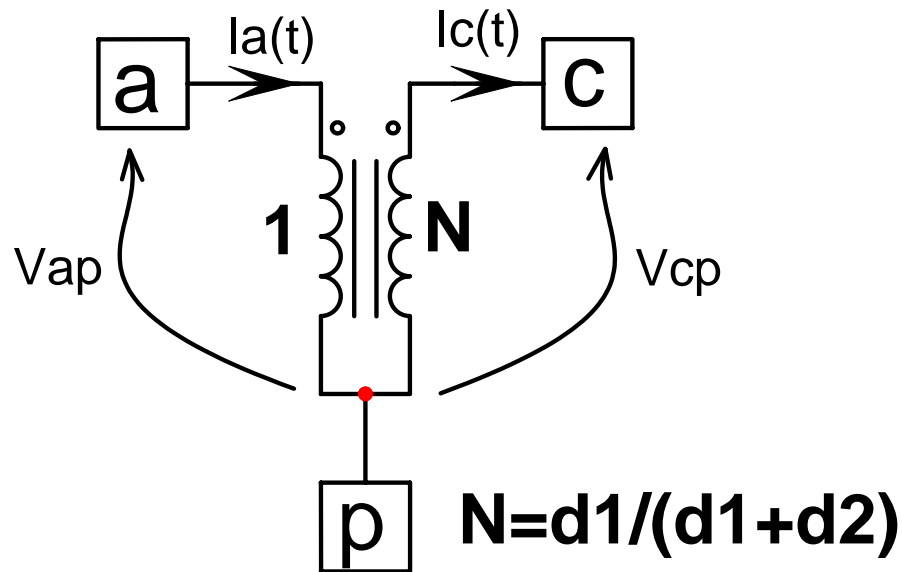
## The “PWM Switch” in mode transitioning SPICE models

An auto-toggling version: **clamp** the equation!



**Clamp**  $d_2$ :

$$d_2 \text{ CCM} = 1 - d_1$$

$$d_2 \text{ DCM} = 1 - d_1 - d_3$$

↓

$d_2 < d_2 \text{ CCM}$   
model is in DCM!


$$d_2 = \frac{2I_c L - V_{ac} d_1^2 T_{sw}}{V_{ac} d_1 T_{sw}} = \frac{2LF_{sw}}{d_1} \frac{I_c}{V_{ac}} \boxed{d_1}$$

← Model input


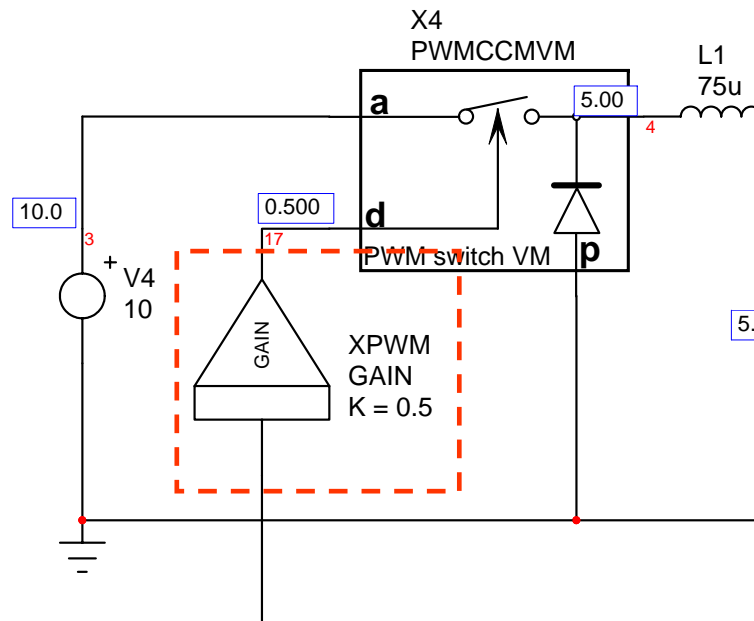
## The “PWM Switch” in mode transitioning SPICE models

In voltage mode, add the PWM *modulator* gain




$$K_{PWM} = \frac{1}{V_{peak}}$$




# The “PWM Switch” in mode transitioning SPICE models

## Testing the *auto-toggling* model

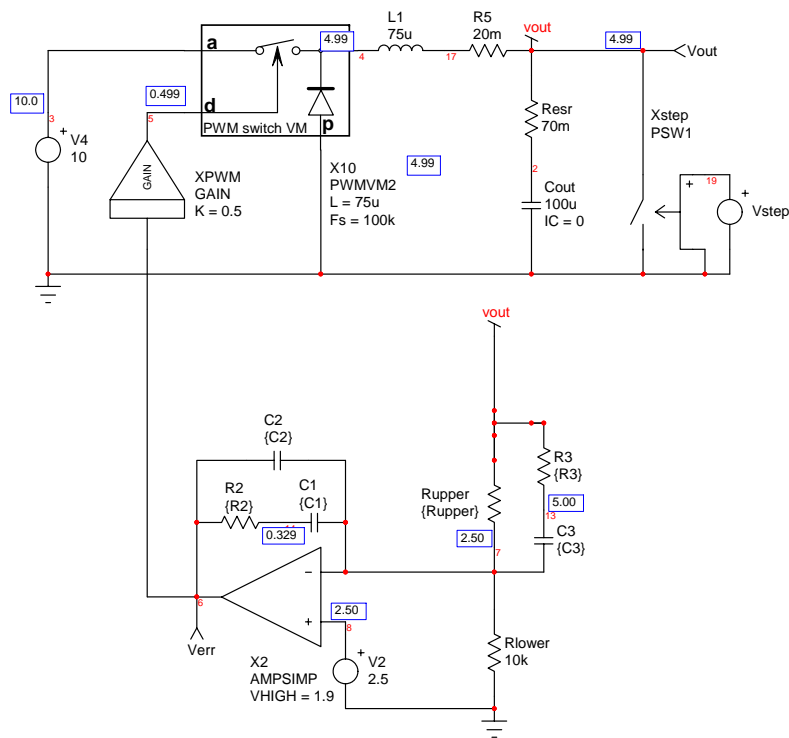

Averaged model


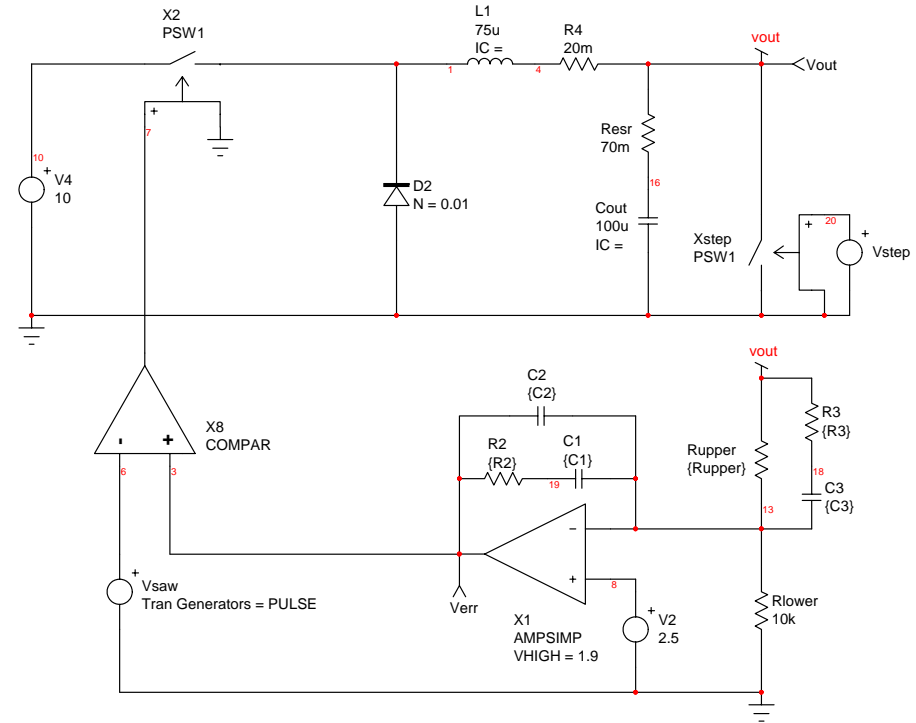


Cycle-by-cycle



# The “PWM Switch” in mode transitioning SPICE models
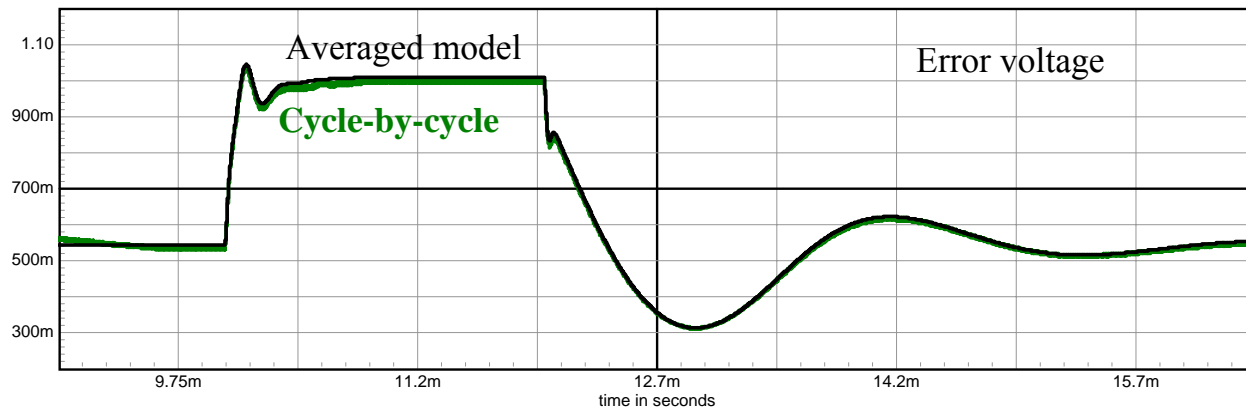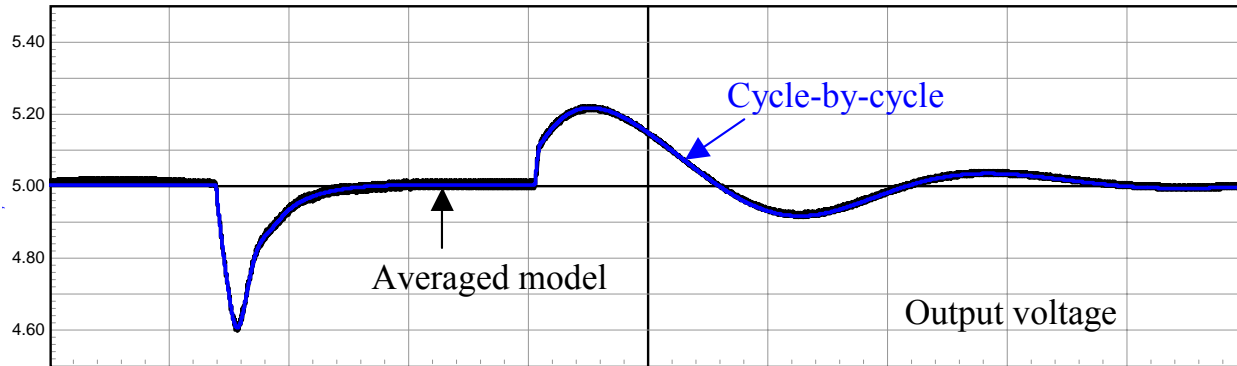
## Comparing *results* with a stepload...




I can't believe this result...



# The “PWM Switch” in mode transitioning SPICE models

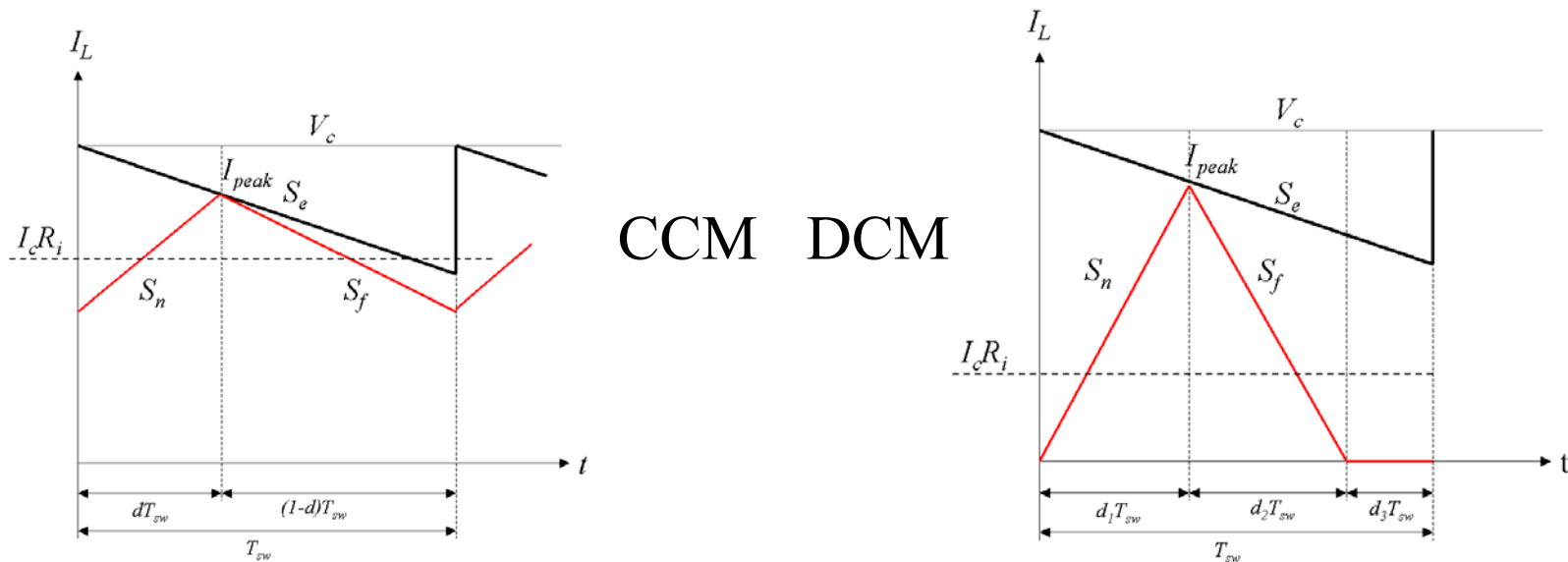
## Current-mode PWM switch

- Same approach as before:
  - ✓ observe and average waveforms
  - ✓ get the equivalent representation
  - ✓ perturb for small-signal analysis




# The “PWM Switch” in mode transitioning SPICE models

## CCM operation, current expression

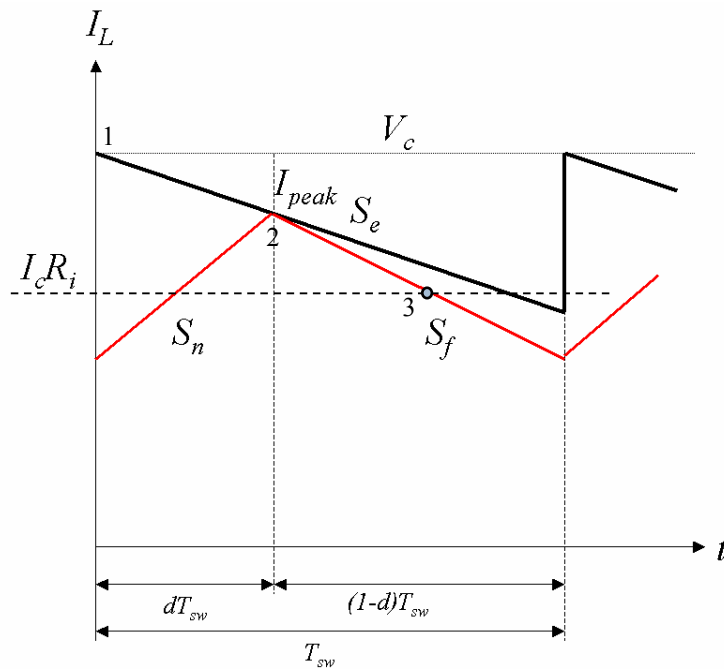


$$I_c(t)R_i = V_c(t) - d(t)T_{sw}S_e - \frac{S_f d'(t)T_{sw}^3}{2}$$
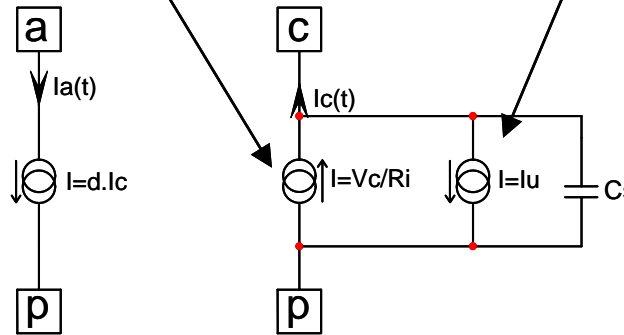
$$I_c = \frac{V_c}{R_i} \left[ d \frac{T_{sw}S_e}{R_i} - V_{cp}(1-d) \frac{T_{sw}}{2L} \right]$$



# The “PWM Switch” in mode transitioning SPICE models

## DCM operation, current expression

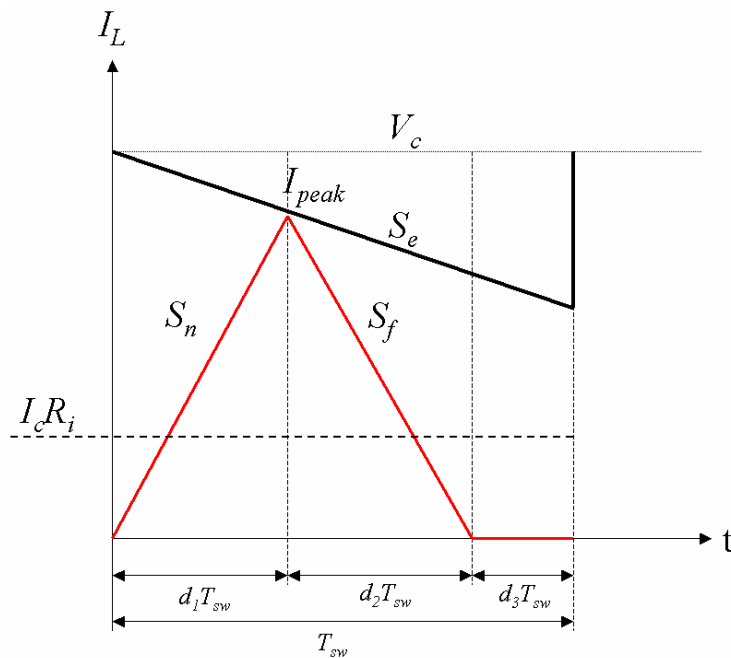


$$I_{peak} = \frac{V_c - d_1 T_{sw} \times S_e}{R_i}$$

$$I_c = \frac{V_c - d_1 T_{sw} S_e}{R_i} - \alpha d_2 T_{sw} S_f$$



$$I_c = \frac{I_{peak} d_1}{2} + \frac{I_{peak} d_2}{2} = \frac{I_{peak} (d_1 + d_2)}{2}$$
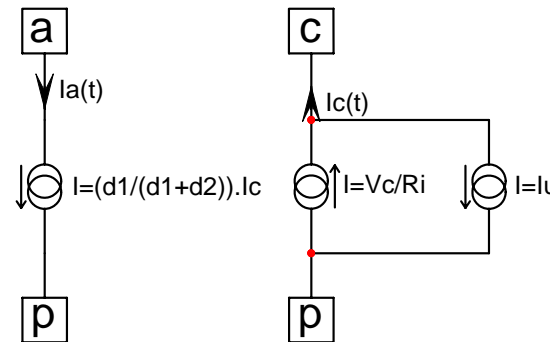
$$I \mu = \frac{d_1 \times T_{sw} \times S_e}{R_i} + d_2 \times T_{sw} \times \frac{V(c, p)}{L} \times \left(1 - \frac{d_1 + d_2}{2}\right)$$



# The “PWM Switch” in mode transitioning SPICE models
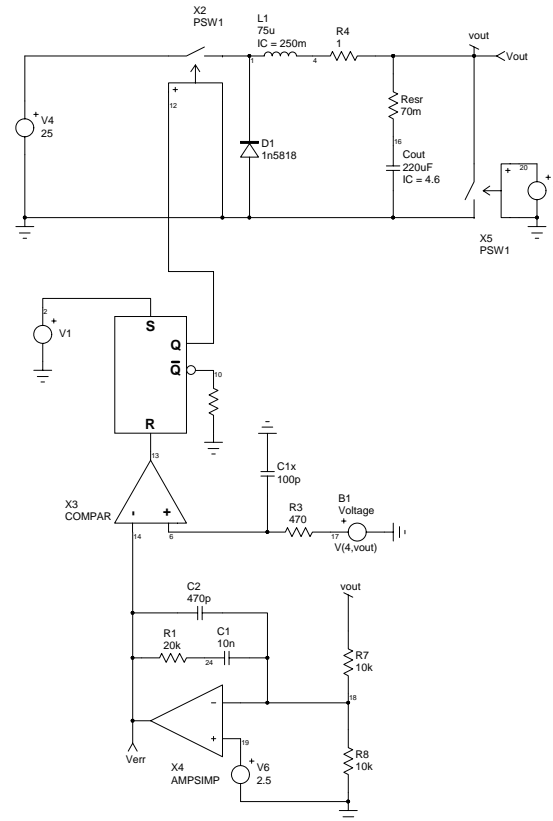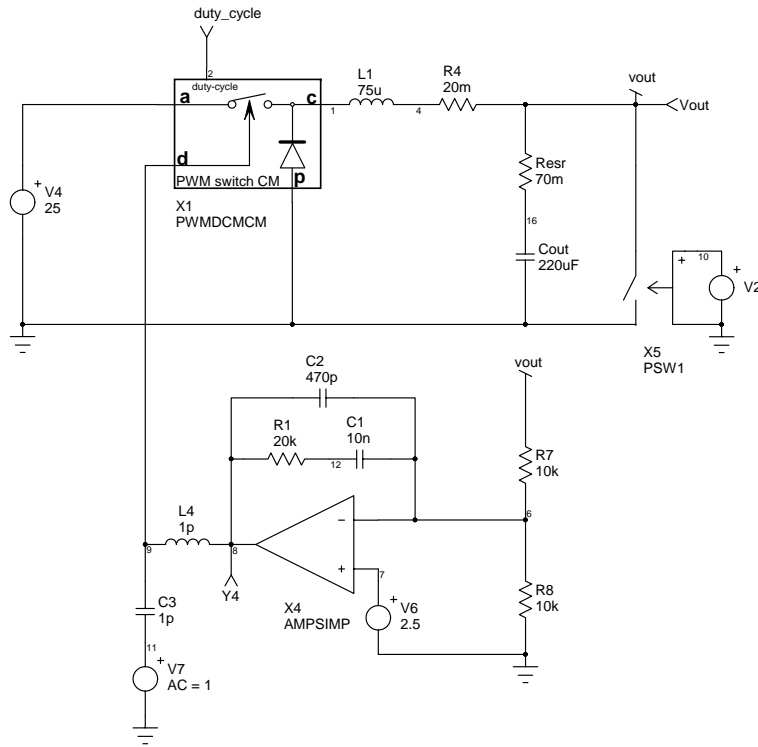
## The PWM Switch, the final encapsulation




A buck: averaged model vs cycle-by-cycle






# The “PWM Switch” in mode transitioning SPICE models

## Good matching between both models

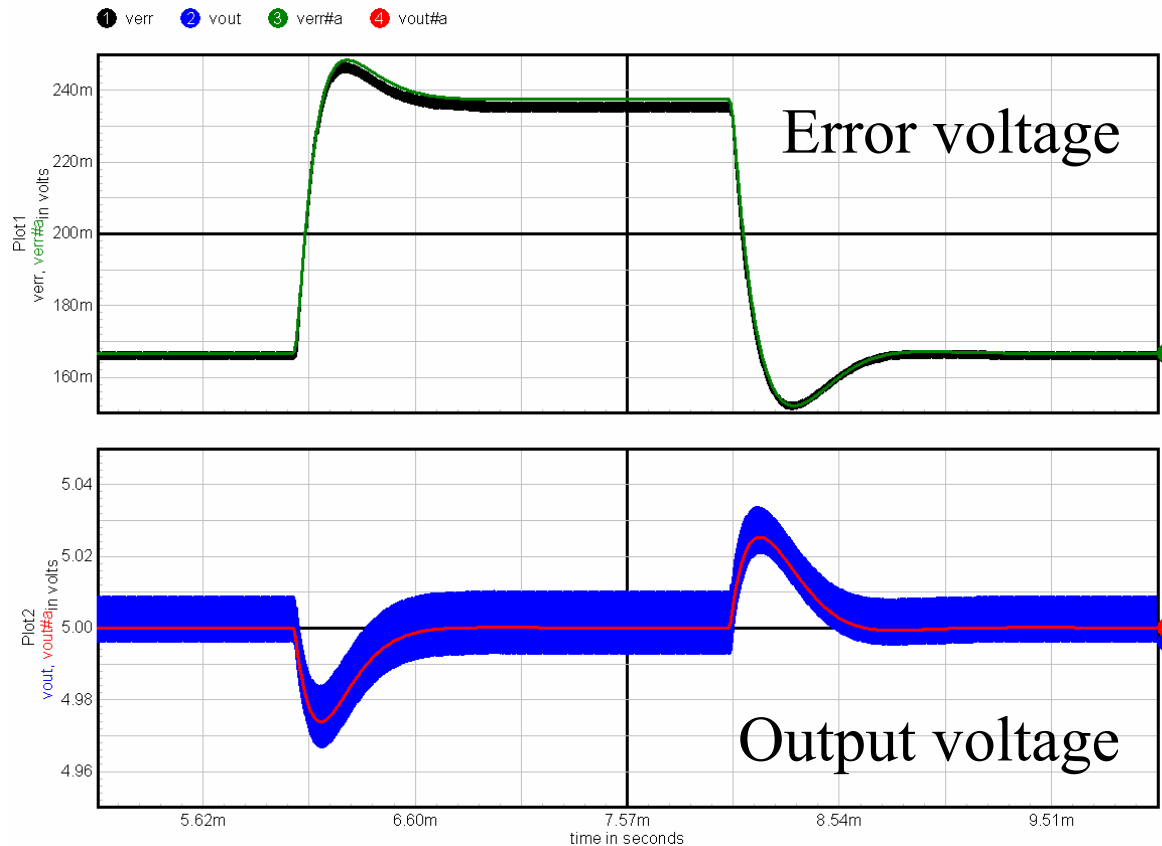

# The “PWM Switch” in mode transitioning SPICE models

## Testing the *ac* response

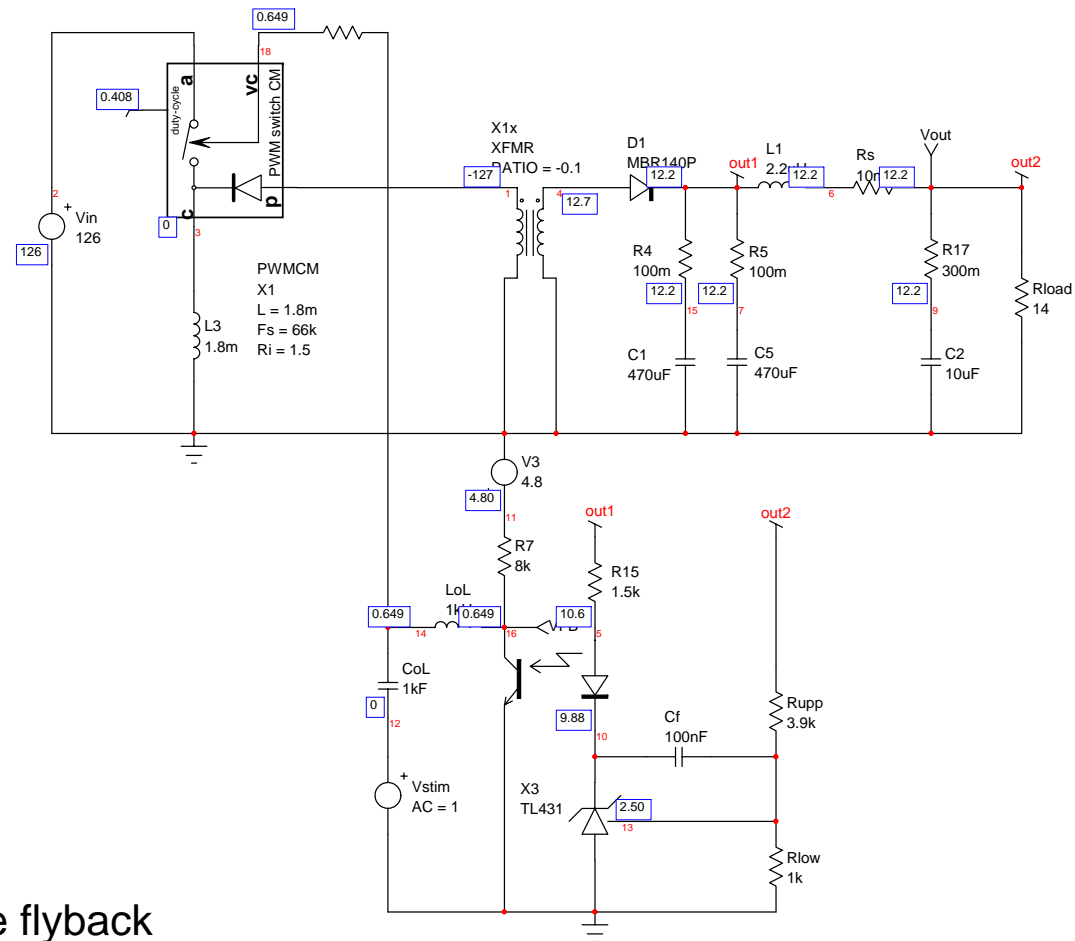


A dcm current-mode flyback




# The “PWM Switch” in mode transitioning SPICE models
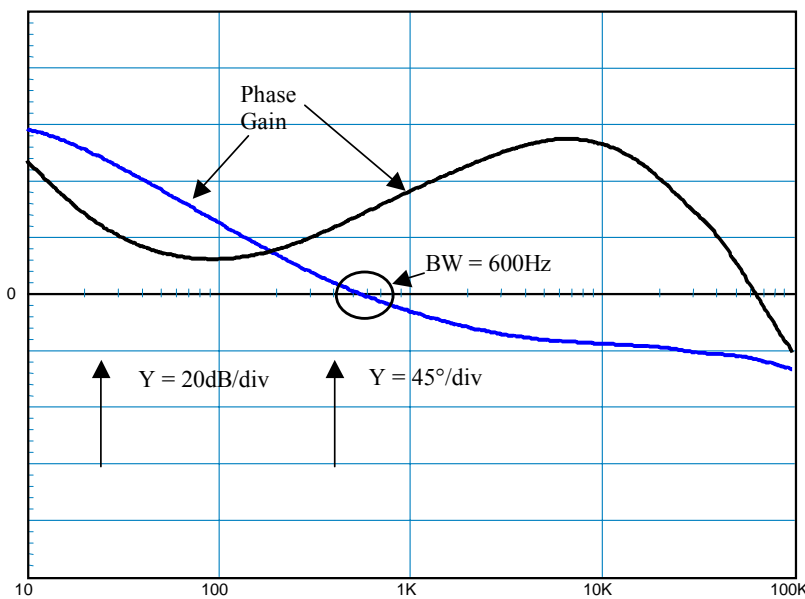
## Ac simulation results of the flyback converter



Simulation

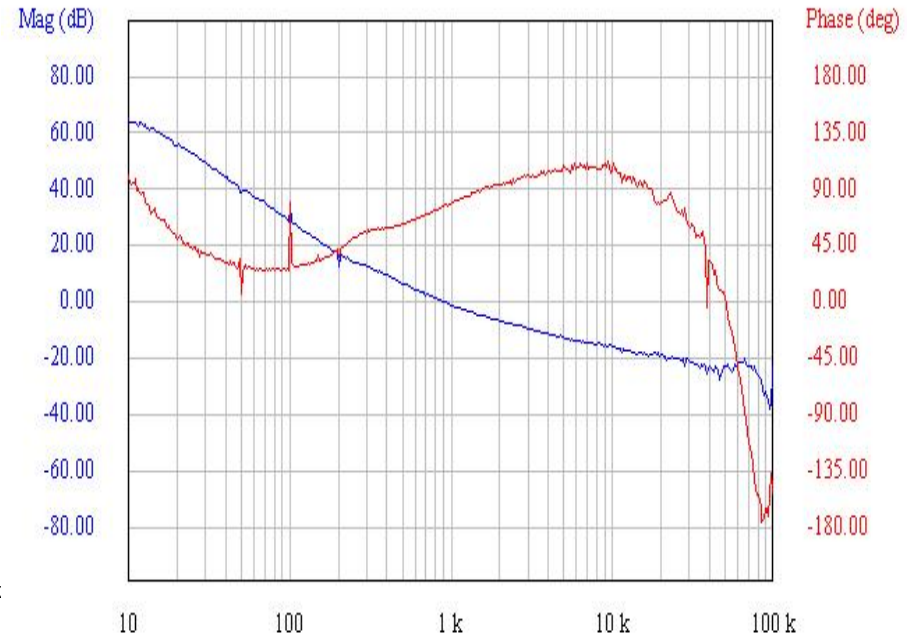


Measurement



# The “PWM Switch” in mode transitioning SPICE models


If the load increases...

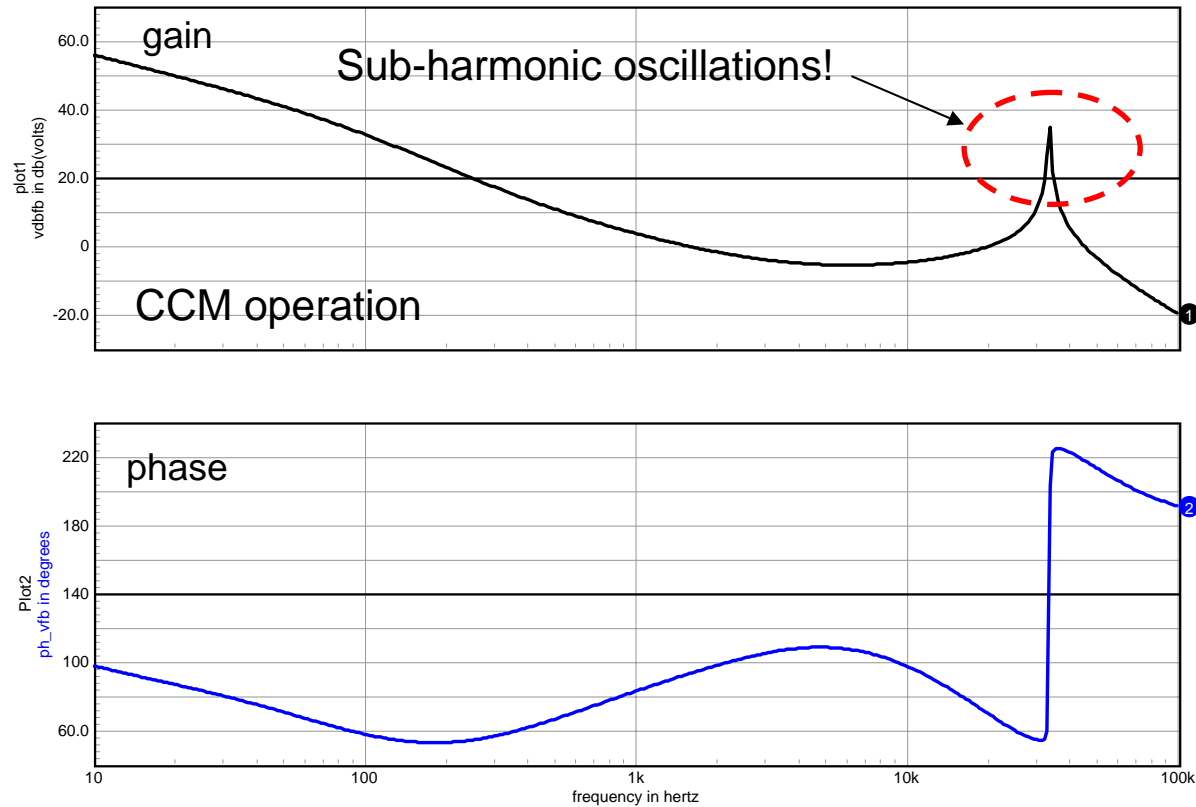



# The “PWM Switch” in mode transitioning SPICE models
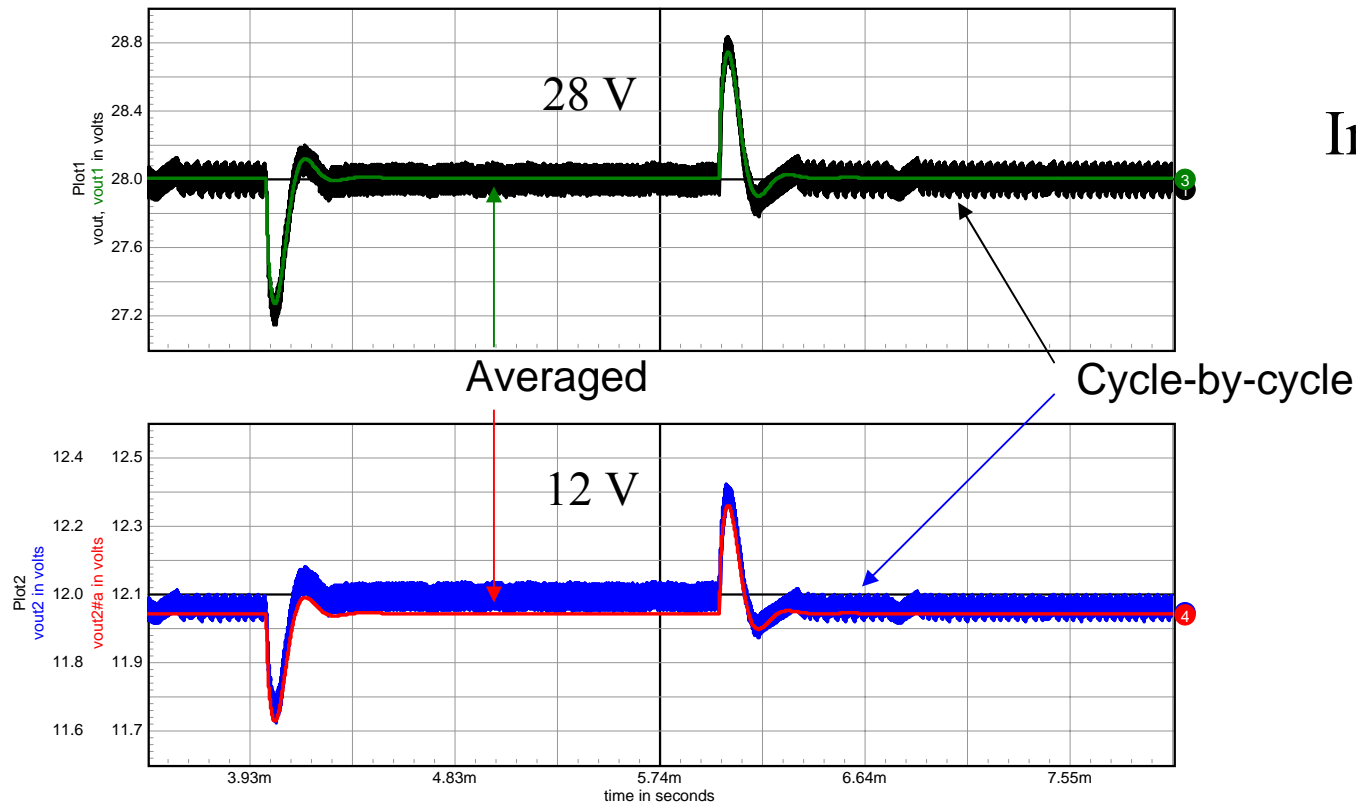
## Output voltage bang on the 28 V output...




Inductances are coupled...

A forward converter



# The “PWM Switch” in mode transitioning SPICE models
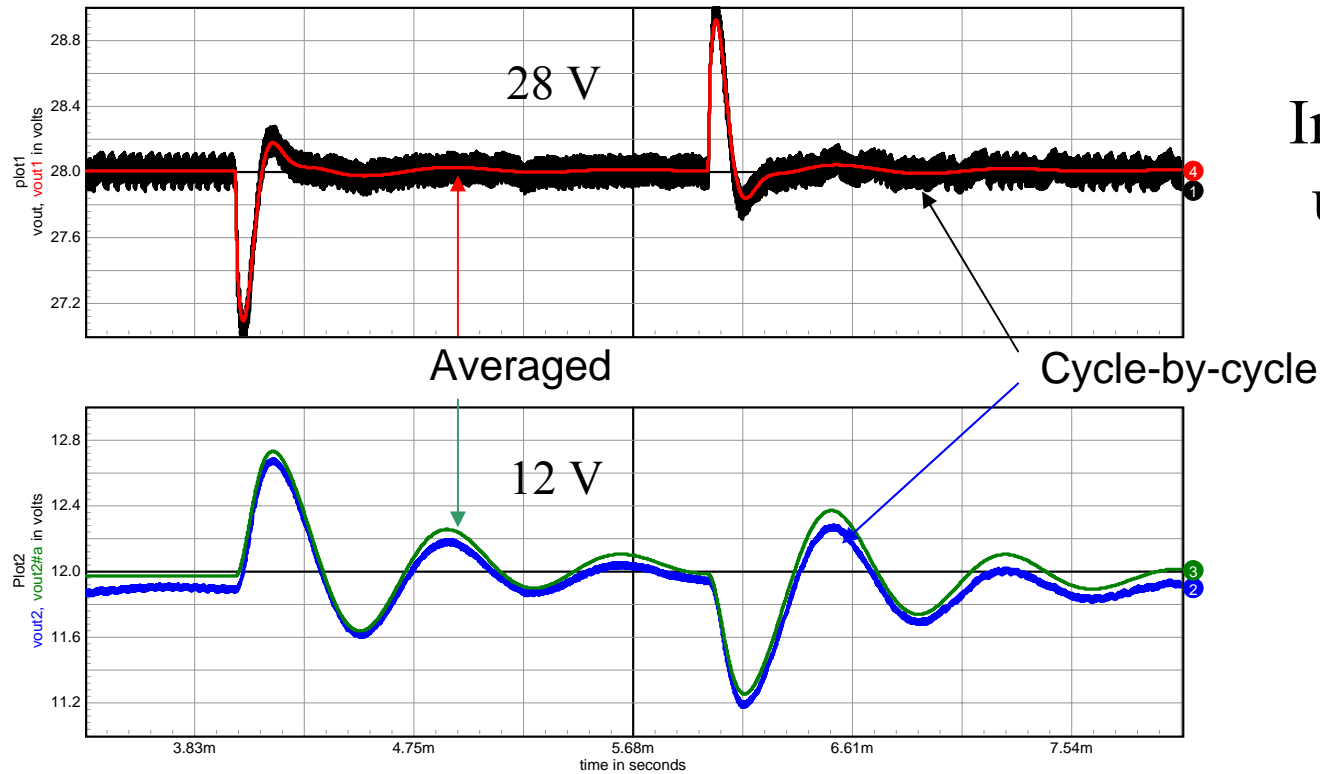
## Output voltage bang on the 28 V output...




Inductances are un-coupled...

A forward converter



# The “PWM Switch” in mode transitioning SPICE models
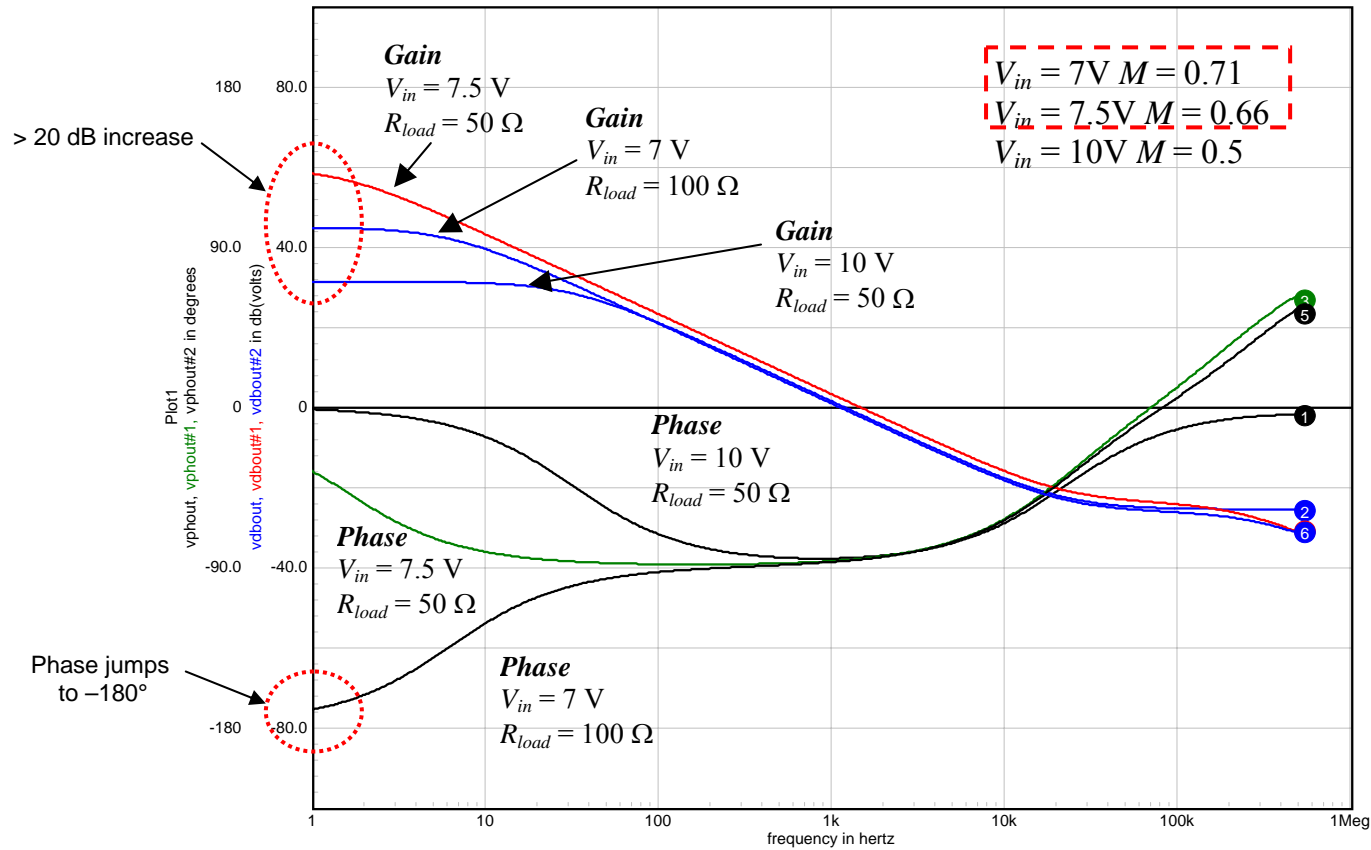
## Instability in the buck DCM current-mode




The DCM buck shows instability as  $M > 0.66$  without ramp





# The “PWM Switch” in mode transitioning SPICE models
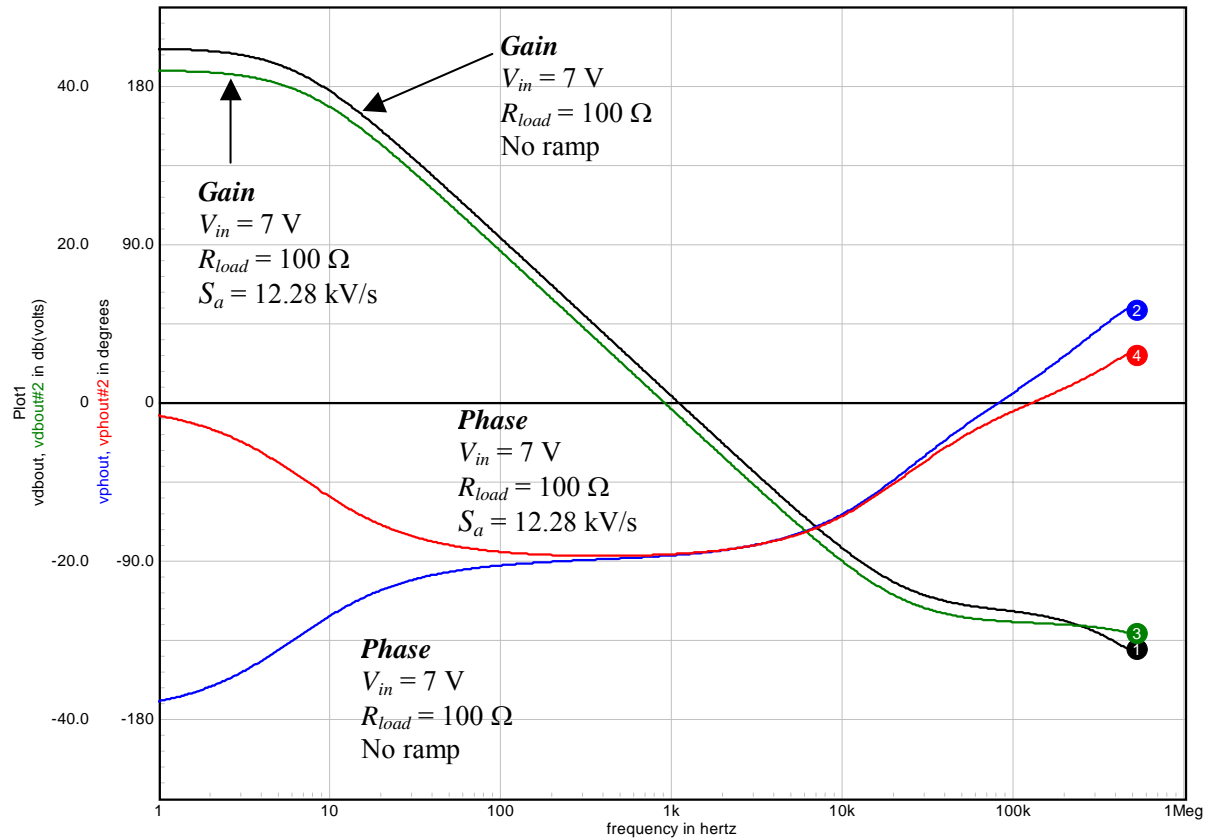
## Instability in the buck DCM current-mode



Adding  $0.086 \times S_{off}$   
cures the problem



### The conclusion

- The CM PWM Switch DCM was derived
- Two auto-toggling models developed
- Good matching of average vs reality
- Models also exist in BCM (PFC simulations)
- Exist in both IsSpice and PSpice

