

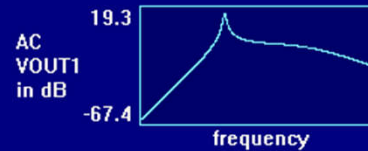
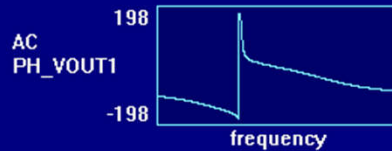
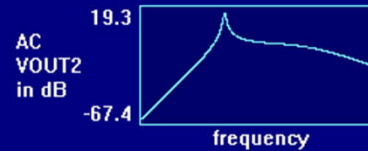
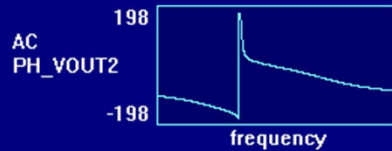
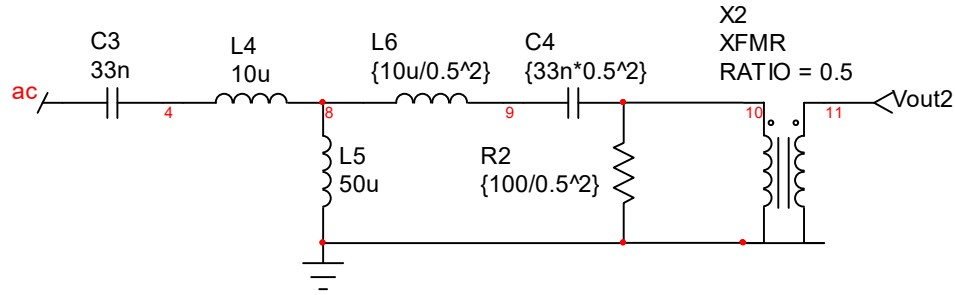
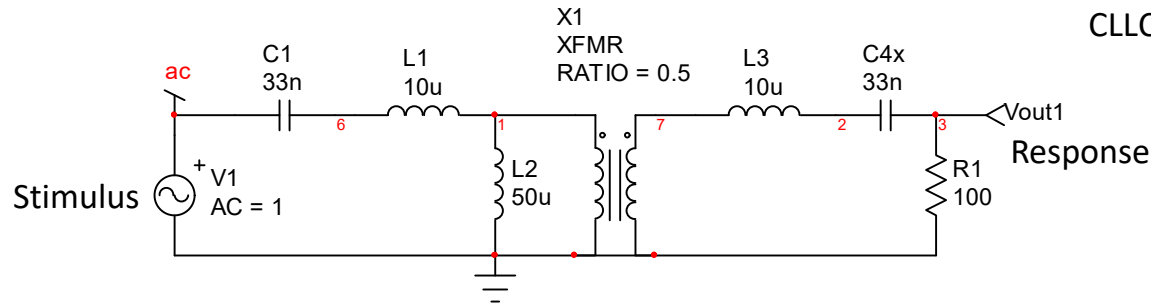



CLLC Transfer Function Determination

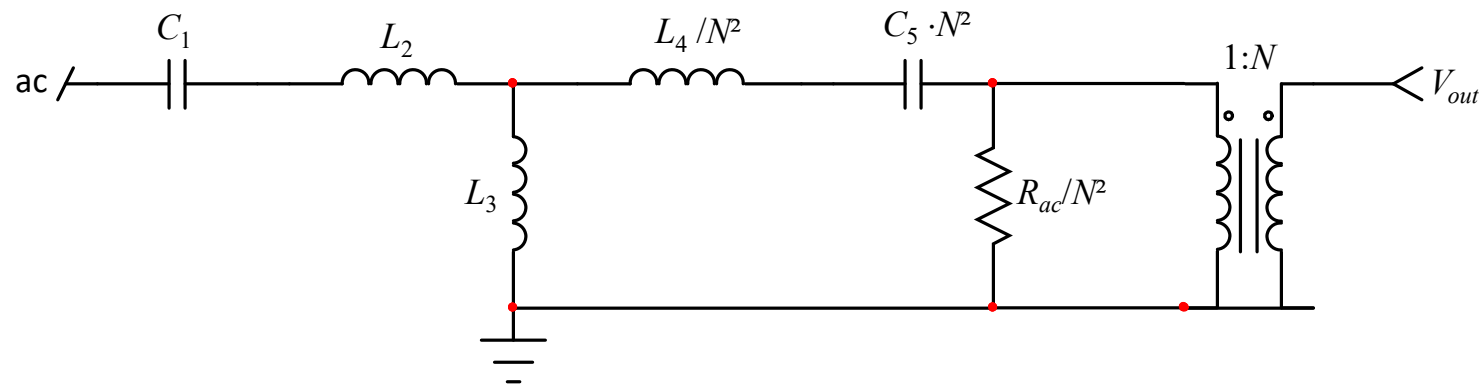

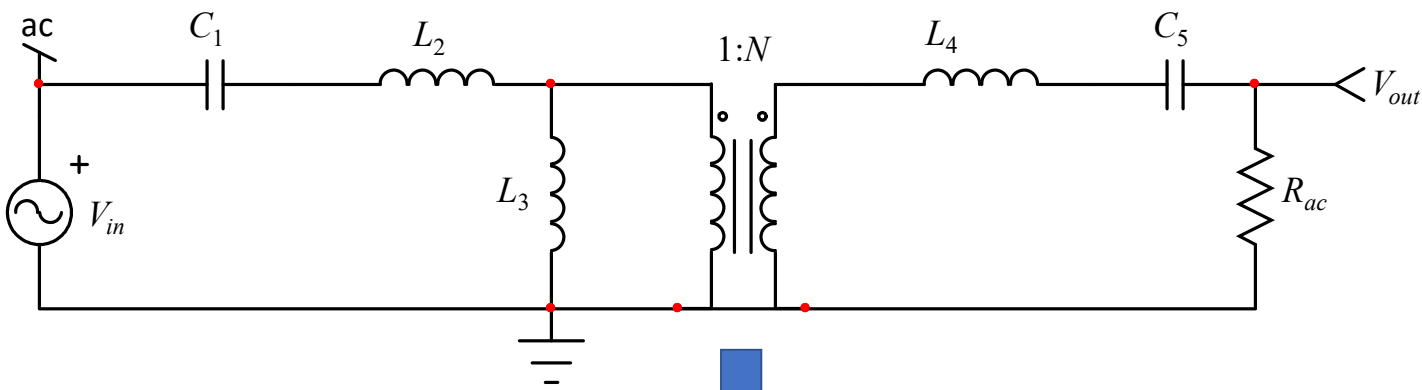


Set $s = 0$

Degenerate case

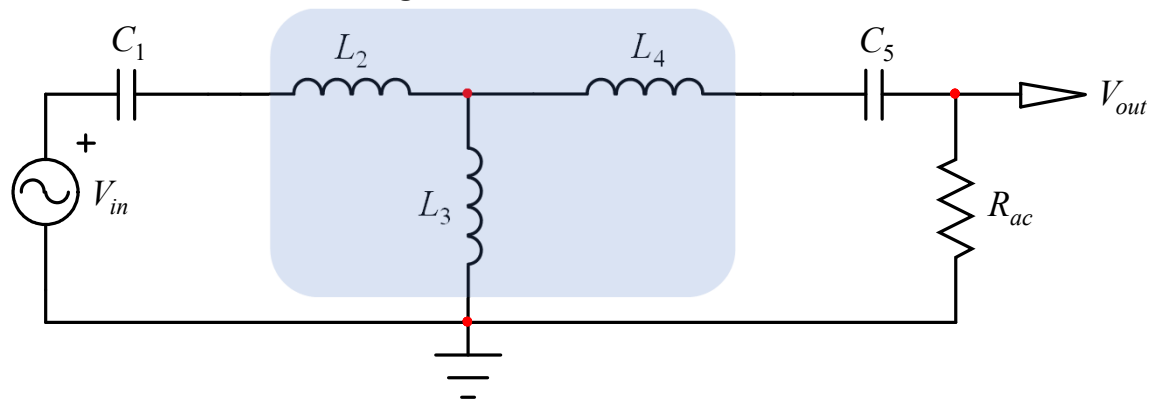


$\Rightarrow H_0 = 0$

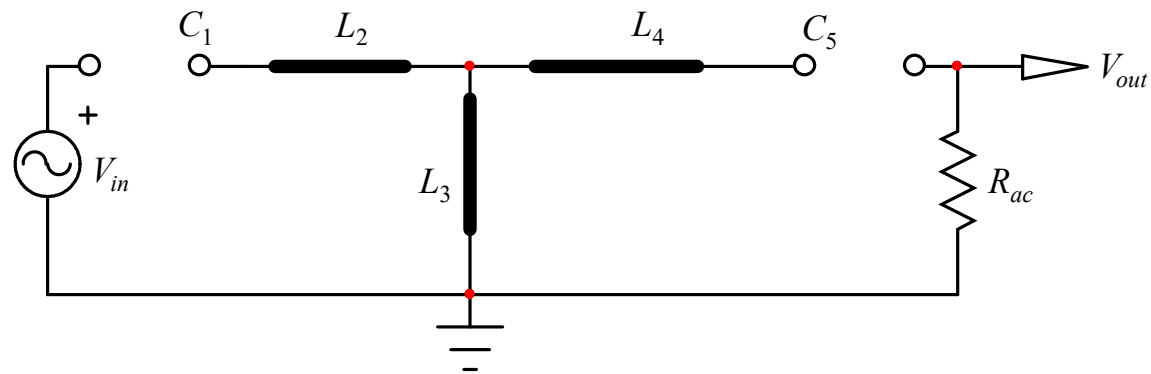


There are 5 energy-storing elements, this is a 4th-order TF because of the degenerate case (inductive node L_2 - L_3 - L_4)

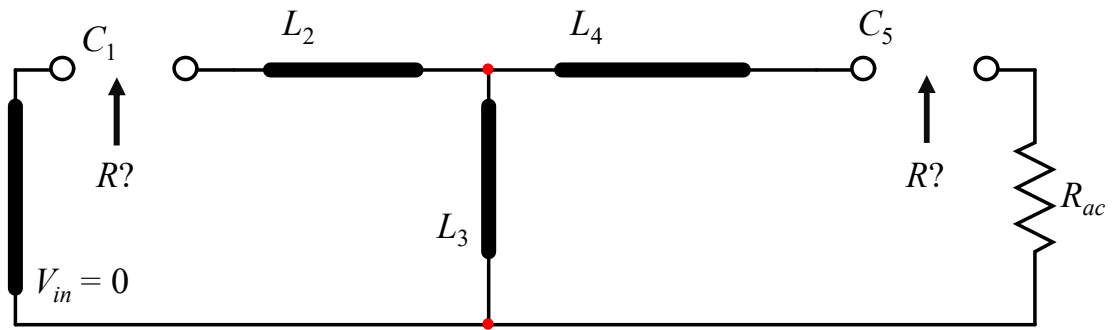Zero the excitation and determine time constants:




$$\tau_1 = R_s \cdot C_1$$


$$\tau_5 = R_{ac} \cdot C_5$$

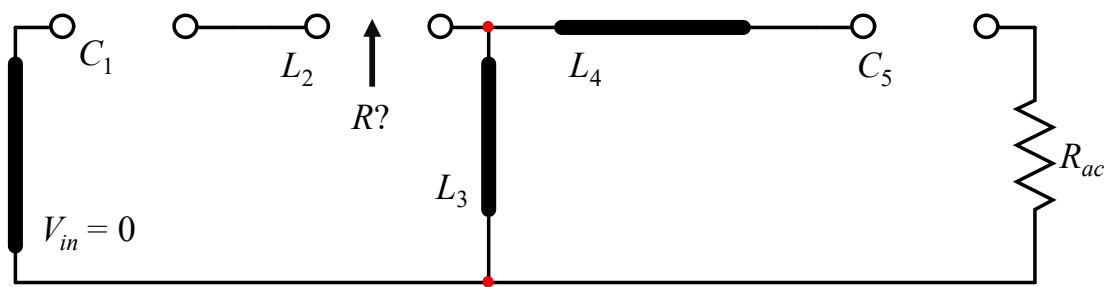

$$\tau_2 = \frac{L_2}{R_{inf}}$$

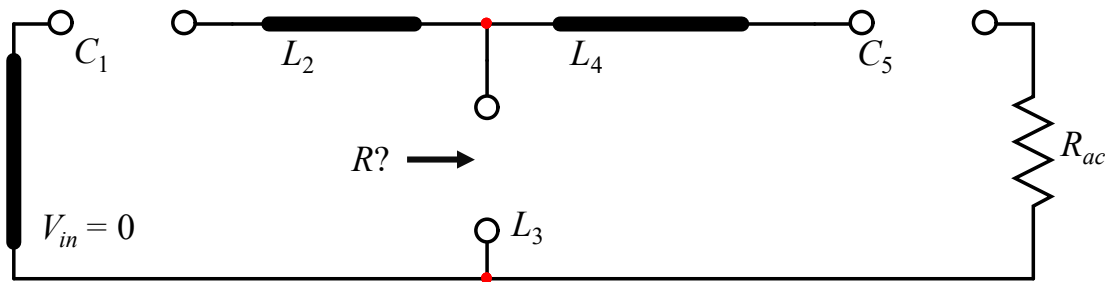

$$\tau_3 = \frac{L_3}{R_{inf}}$$

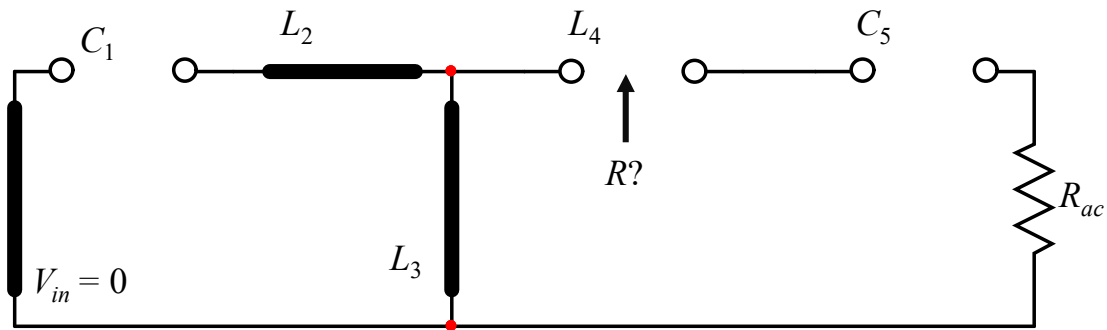


$$\tau_4 = \frac{L_4}{R_{inf}}$$

$$b_1 = \tau_1 + \tau_2 + \tau_3 + \tau_4 + \tau_5 = \underbrace{R_s C_1}_{=0} + R_{ac} C_5 + \underbrace{\frac{L_2}{R_{inf}}}_{=0} + \underbrace{\frac{L_3}{R_{inf}}}_{=0} + \underbrace{\frac{L_4}{R_{inf}}}_{=0}$$

How many terms for b_2 ?

order $\rightarrow \binom{n}{j} = \frac{n!}{j!(n-j)!} \rightarrow \binom{5}{2} = 10$

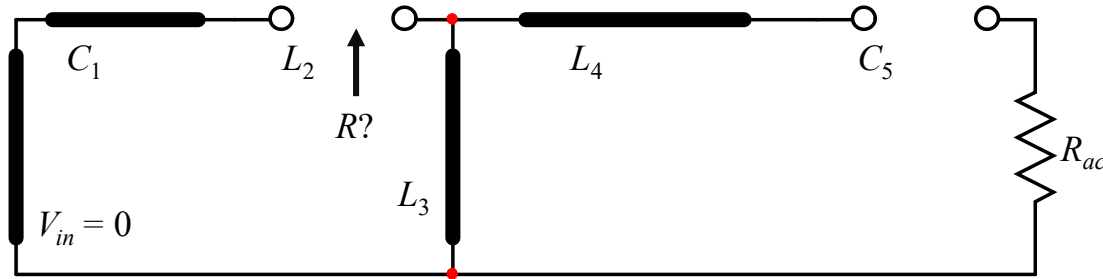
$$b_2 = \tau_1\tau_2^1 + \tau_1\tau_3^1 + \tau_1\tau_4^1 + \tau_1\tau_5^1 + \tau_2\tau_3^2 + \tau_2\tau_4^2 + \tau_2\tau_5^2 + \tau_3\tau_4^3 + \tau_3\tau_5^3 + \tau_4\tau_5^4$$




τ_2^1 ← Set in high frequency
A short circuit for a cap.

$R?$ ↑
The remaining elements
are left in their dc state
(all caps open)


$$\tau_2^1 = \frac{L_2}{R_s}$$

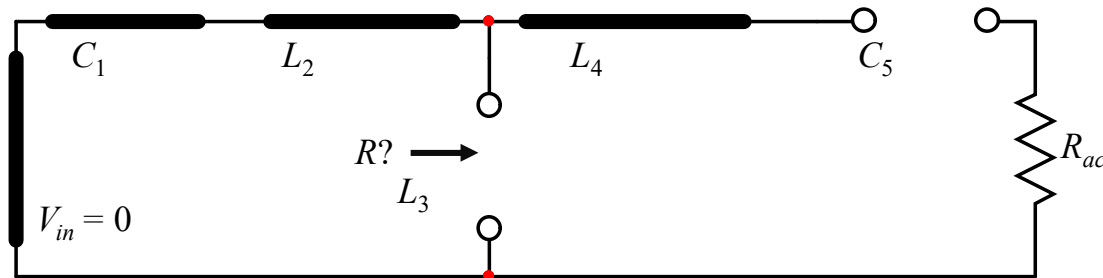


$$\tau_3^1 = \frac{L_3}{R_s}$$

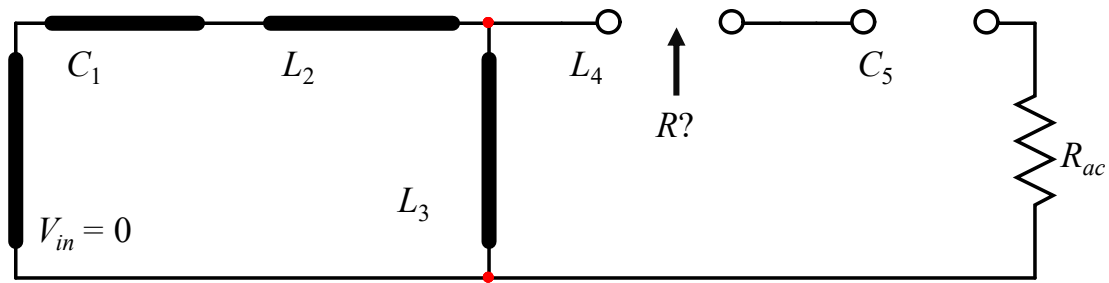


$$\tau_4^1 = \frac{L_4}{R_{inf}}$$

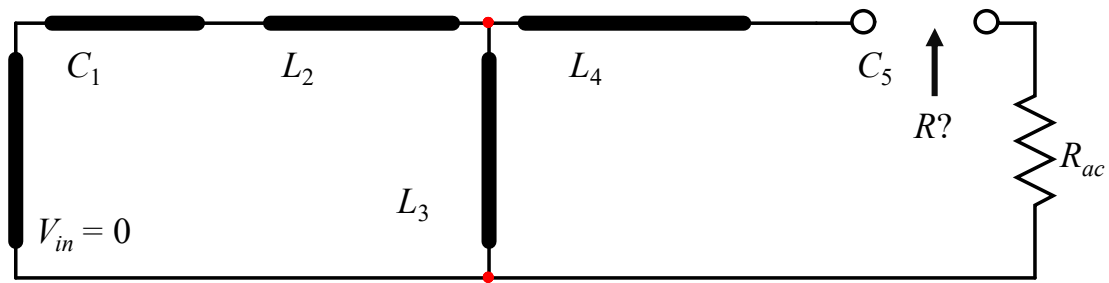


$$\tau_5^1 = C_5 R_{ac}$$

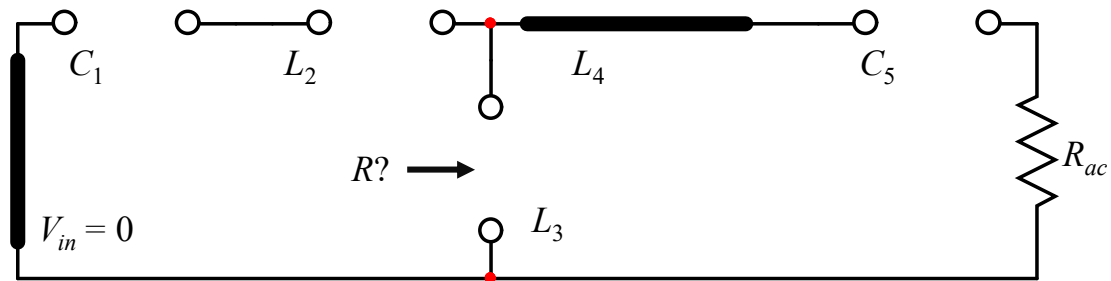

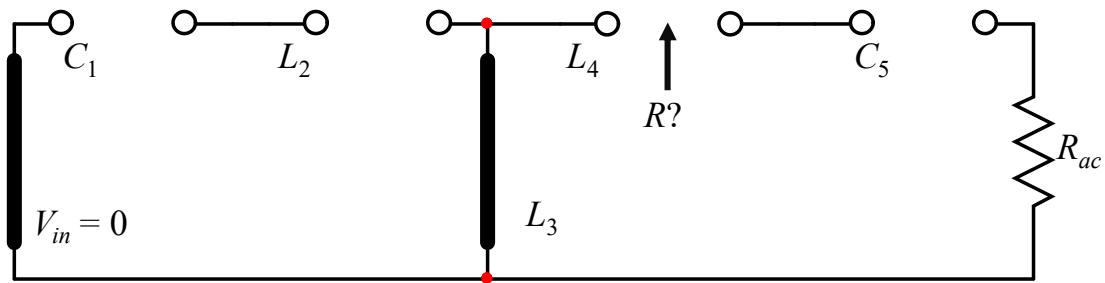
$$\tau_3^2 = \frac{L_3}{R_{\text{inf}}}$$



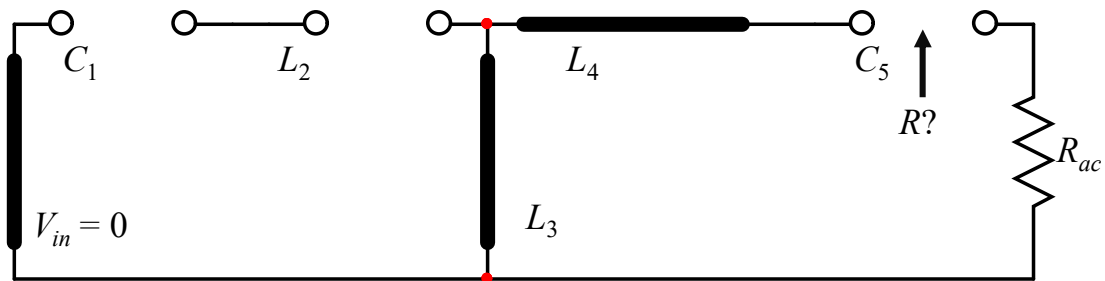
$$\tau_4^2 = \frac{L_4}{R_{\text{inf}}}$$




$$\tau_5^2 = C_5 R_{ac}$$

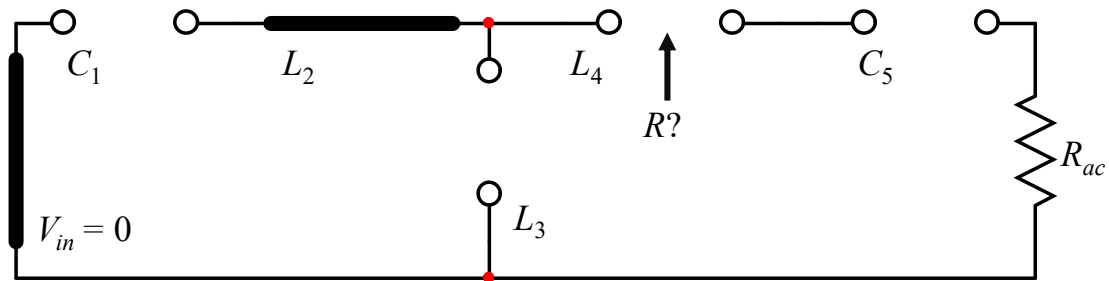
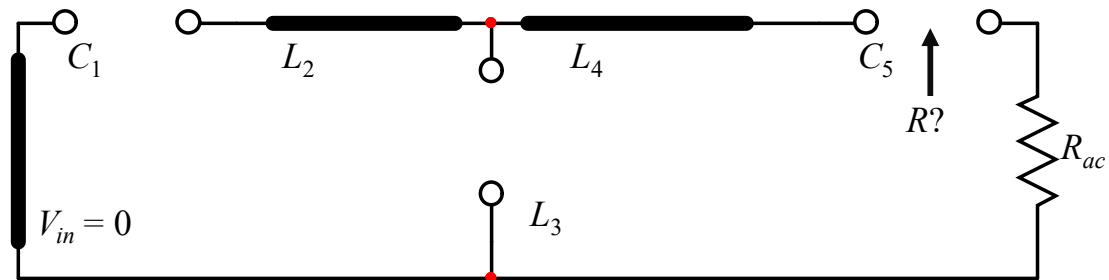
$$\tau_4^3 = \frac{L_4}{R_{\text{inf}}}$$



$$\tau_5^3 = C_5 R_{\text{inf}}$$

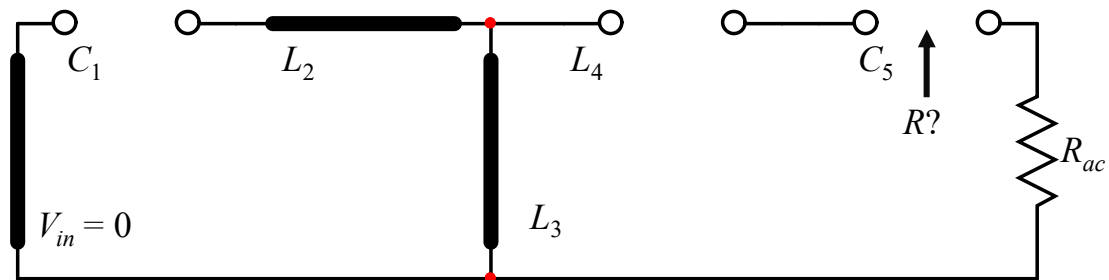

$$\tau_5^4 = C_5 R_{\text{inf}}$$

How many terms for b_3 ?

order \rightarrow $\binom{n}{j} = \frac{n!}{j!(n-j)!} \rightarrow \binom{5}{3} = 10$
 rank \rightarrow

$$b_3 = \tau_1 \tau_2^1 \tau_3^{12} + \tau_1 \tau_2^1 \tau_4^{12} + \tau_1 \tau_2^1 \tau_5^{12} + \tau_1 \tau_3^1 \tau_4^{13} + \tau_1 \tau_3^1 \tau_5^{13} + \tau_1 \tau_4^1 \tau_5^{14} + \tau_2 \tau_3^2 \tau_4^{23} + \tau_2 \tau_3^2 \tau_5^{23} + \tau_2 \tau_4^2 \tau_5^{24} + \tau_3 \tau_4^3 \tau_5^{34}$$


$$\tau_3^{12}$$

$$\uparrow$$


$$R?$$

Set in high frequency
A short circuit for a cap.

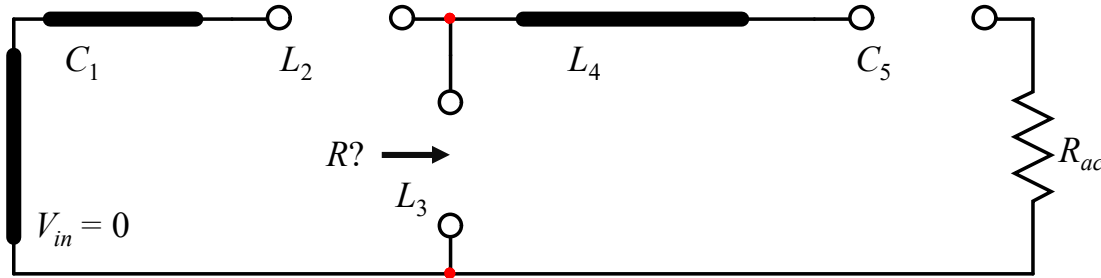
The remaining elements
are left in their dc state
(all caps open)



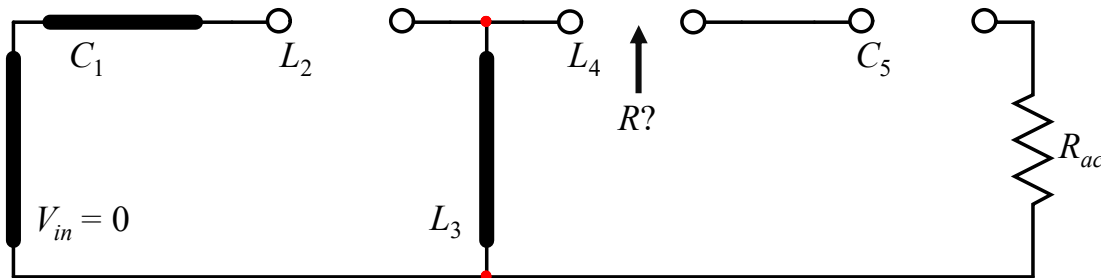
$$\tau_3^{12} = \frac{L_3}{R_{\text{inf}}}$$



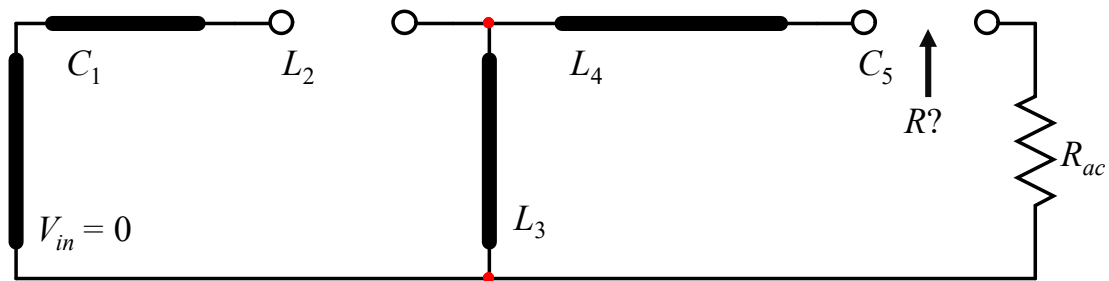
$$\tau_4^{12} = \frac{L_4}{R_{\text{inf}}}$$




$$\tau_5^{12} = C_5 R_{ac}$$

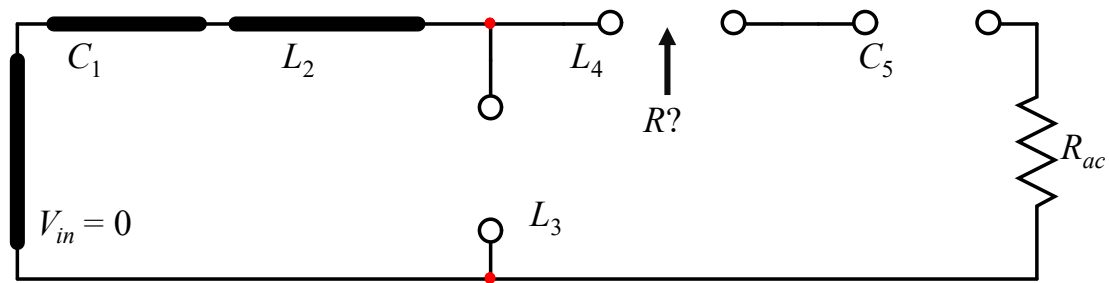


$$\tau_4^{13} = \frac{L_4}{R_{inf}}$$

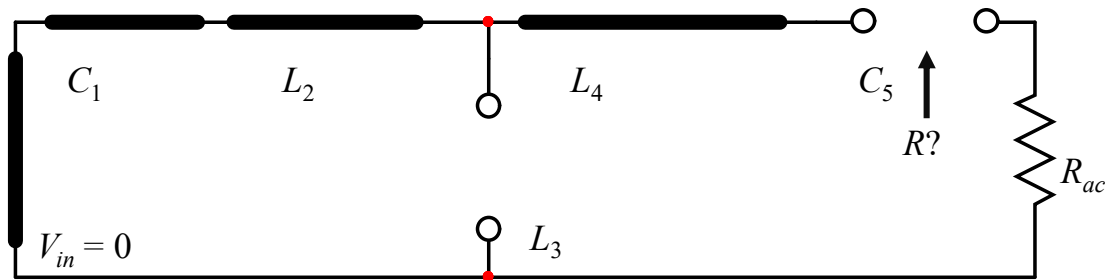


$$\tau_5^{13} = C_5 R_{ac}$$

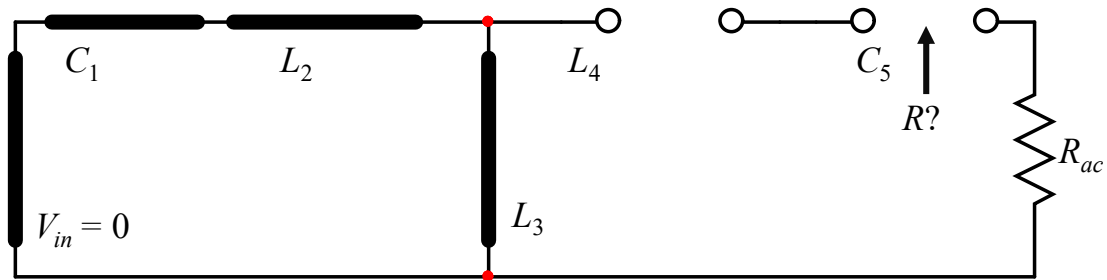



$$\tau_5^{14} = C_5 R_{\text{inf}}$$

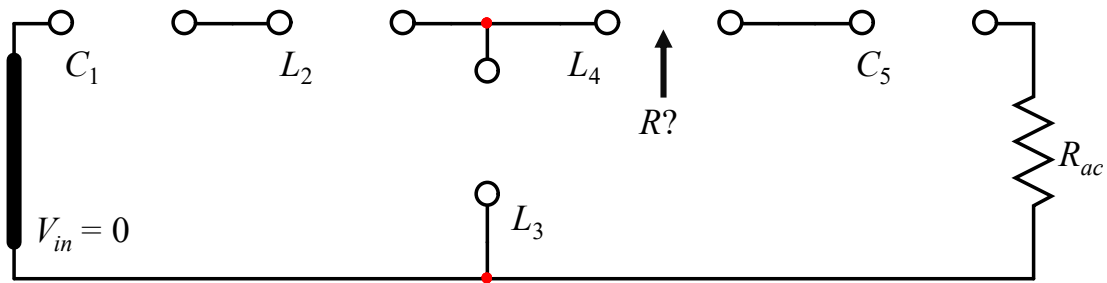
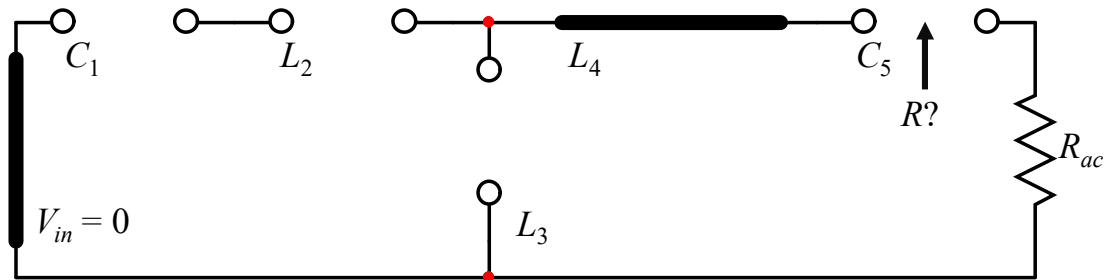
$$\tau_4^{23} = \frac{L_4}{R_{\text{inf}}}$$




$$\tau_5^{23} = C_5 R_{\text{inf}}$$

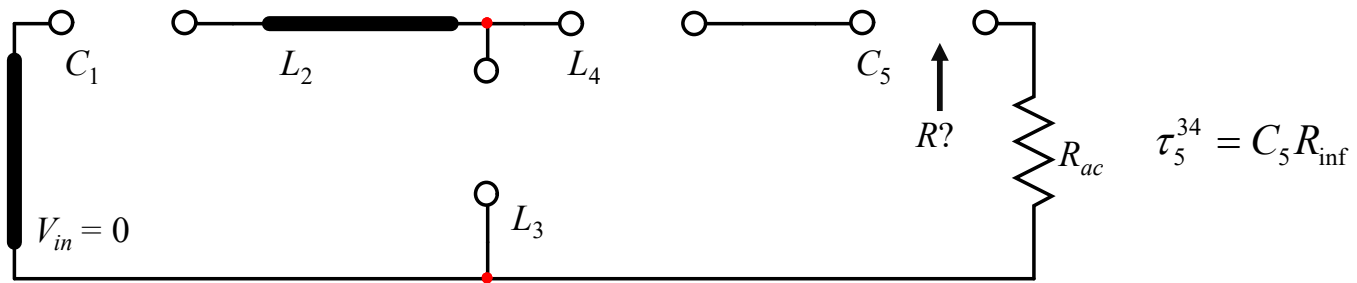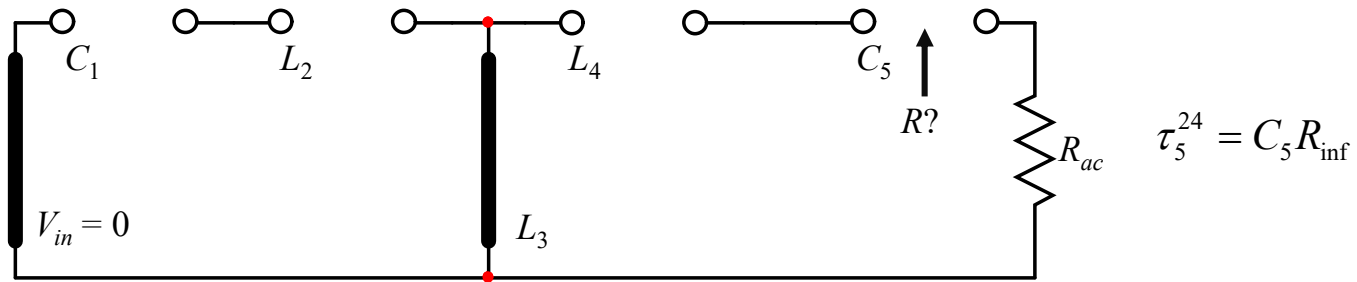


How many terms for b_4 ?

order \rightarrow $\binom{n}{j} = \frac{n!}{j!(n-j)!}$ \rightarrow $\binom{5}{4} = 5$
 rank \rightarrow
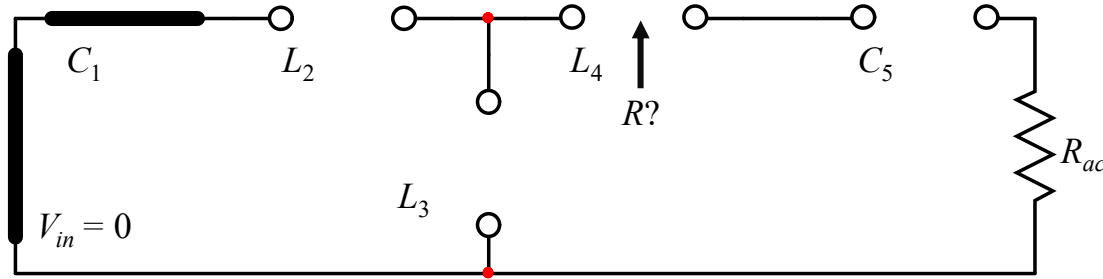
$$b_4 = \tau_1 \tau_2^1 \tau_3^{12} \tau_4^{123} + \tau_1 \tau_2^1 \tau_3^{12} \tau_5^{123} + \tau_1 \tau_2^1 \tau_4^{12} \tau_5^{124} + \tau_1 \tau_3^1 \tau_4^{13} \tau_5^{134} + \tau_2 \tau_3^2 \tau_4^{23} \tau_5^{234}$$


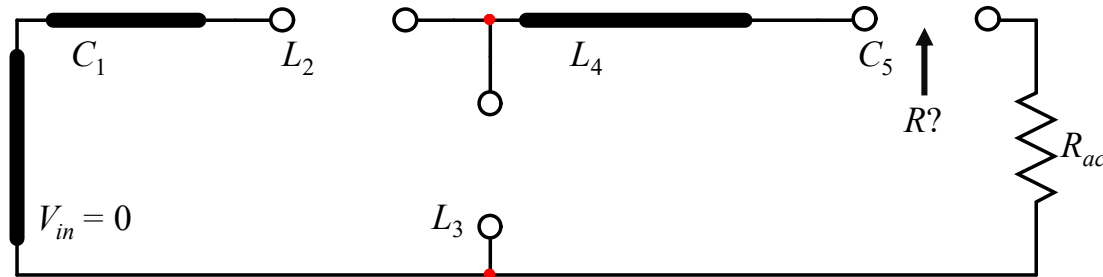
$$\tau_4^{123} = \frac{L_4}{R_{\text{inf}}}$$






$$\tau_5^{123} = C_5 R_{\text{inf}}$$

$$\tau_4^{123}$$


Set in high frequency
A short circuit for a cap.

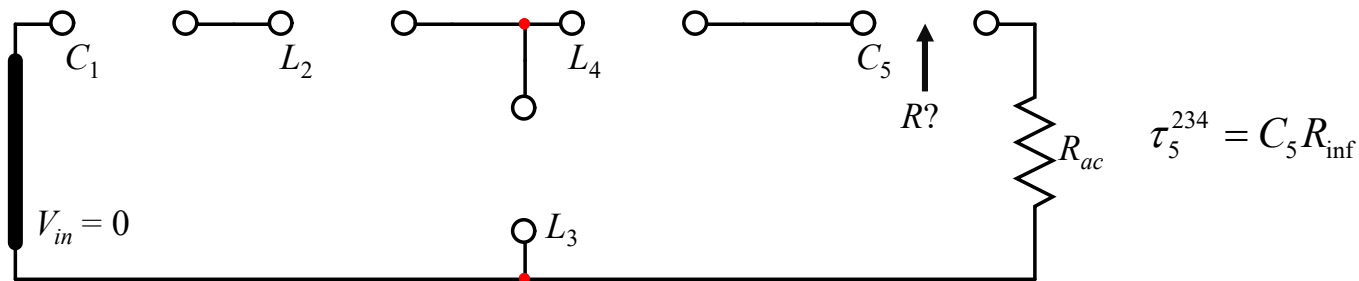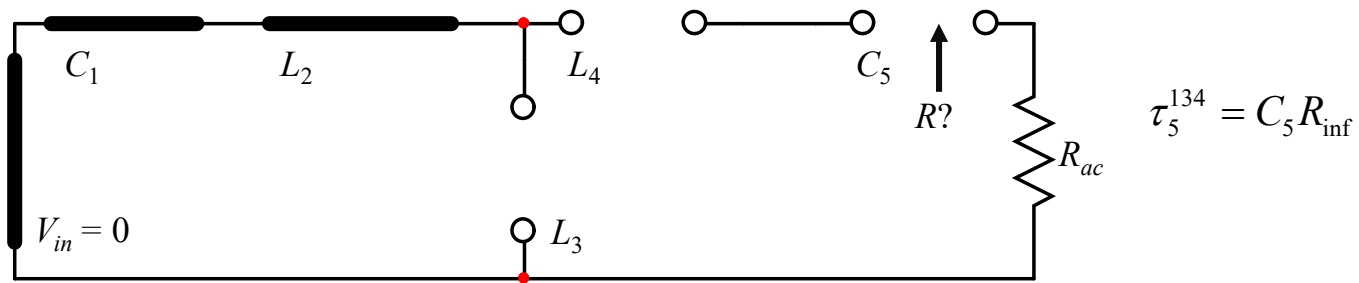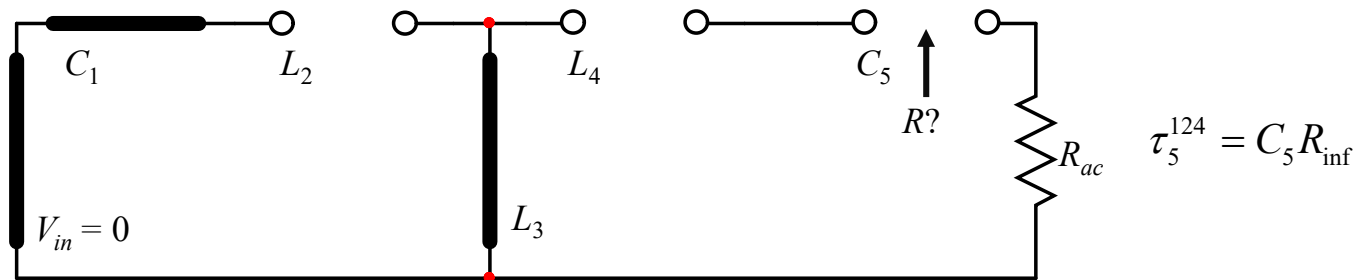The remaining elements
are left in their dc state
(all caps open)



How many terms for b_5 ?

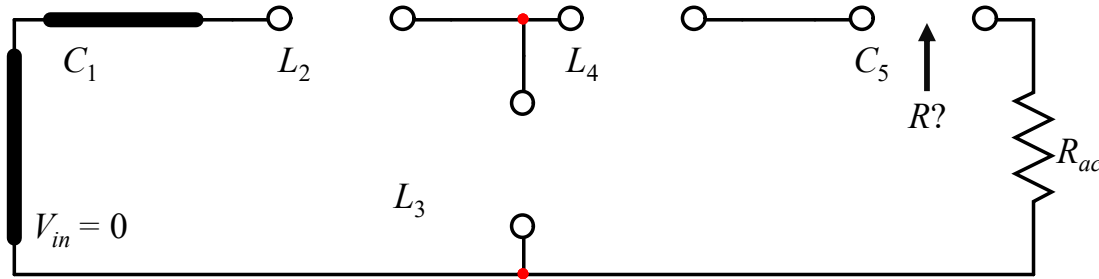order \rightarrow $\binom{n}{j} = \frac{n!}{j!(n-j)!}$ \rightarrow $\binom{5}{5} = 1$ $b_5 = \tau_1 \tau_2^1 \tau_3^{12} \tau_4^{123} \tau_5^{1234}$




τ_5^{1234}
 \uparrow
 $R?$

Set in high frequency
 A short circuit for a cap.
 An open circuit for L
 The remaining elements
 are left in their dc state
 (all caps open, all shorted)

$\tau_5^{1234} = C_5 R_{inf}$

Determining high-frequency gains

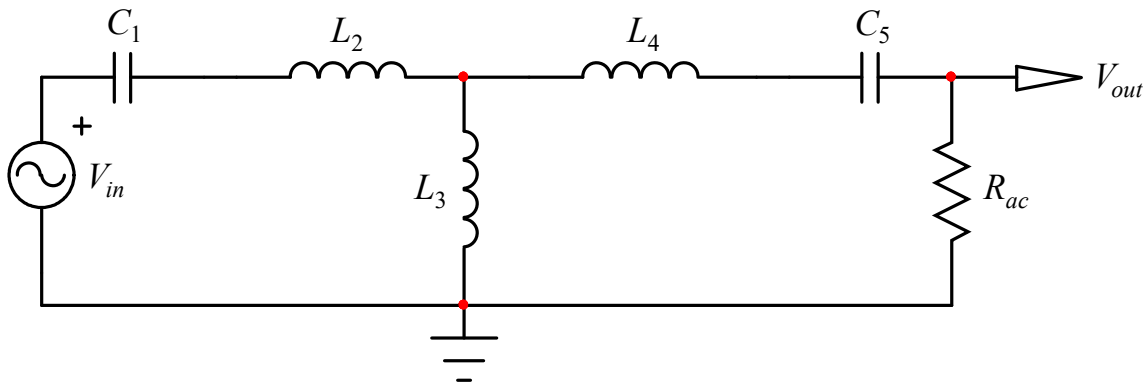

The only combination in which a gain exists is when C_1, L_3 and C_5 are in their high-frequency state: $H^{135} = 1$

$$H^1$$

Element 1 is in HF
The rest are in dc
What is the gain?

$$H^1 = 0$$

$$H^2 = 0$$

$$H^3 = 0$$

$$H^4 = 0$$

$$H^5 = 0$$

$$H^{12}$$

Element 12 are in HF
The rest are in dc
What is the gain?

$$H^{12} = 0 \quad H^{25} = 0$$

$$H^{13} = 0 \quad H^{34} = 0$$

$$H^{14} = 0 \quad H^{35} = 0$$

$$H^{15} = 0 \quad H^{45} = 0$$

$$H^{23} = 0$$

$$H^{24} = 0$$

$$H^{123}$$

Element 123 are in HF
The rest are in dc
What is the gain?

$$H^{123} = 0 \quad H^{234} = 0$$

$$H^{124} = 0 \quad H^{235} = 0$$

$$H^{125} = 0 \quad H^{245} = 0$$

$$H^{134} = 0 \quad H^{345} = 0$$

$$H^{135} = 1$$

$$H^{145} = 0$$

$$H^{1234}$$

Element 1234 are in HF
The rest are in dc
What is the gain?

$$H^{1234} = 0$$

$$H^{1235} = 0$$

$$H^{1245} = 0$$

$$H^{1345} = 0$$

$$H^{2345} = 0$$

$$H^{12345} = 0$$


$$H(s) = \frac{H_0 + s^3 H^{135} \tau_1 \tau_3^1 \tau_5^{13}}{D(s)} = \frac{s^3 \tau_1 \tau_3^1 \tau_5^{13}}{1 + s b_1 + s^2 b_2 + s^3 b_3 + s^4 b_4 + s^5 \underbrace{b_5}_{=0}}$$

Turns ratio, 1:N




$$H(s) = N \frac{s^3 R_{ac} L_3 C_5 C_1}{1 + s R_{ac} C_5 + s^2 [C_1 (L_2 + L_3) + C_5 (L_3 + L_4)] + s^3 C_1 C_5 R_{ac} (L_2 + L_3) + s^4 C_1 C_5 (L_2 L_3 + L_2 L_4 + L_3 L_4)}$$

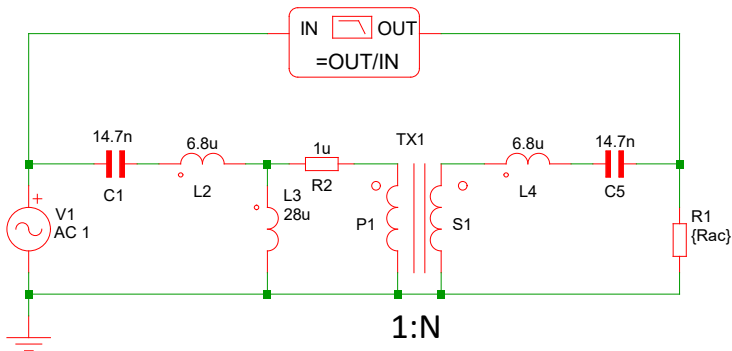
*
 .PARAM Pout=10k
 .PARAM Vout=500
 .PARAM RL={Vout^2/Pout}
 .PARAM Rac={8*RL/pi^2}
 *



$$20 \cdot \log \left(\left| N_1 \cdot H_1(i \cdot 2\pi \cdot f_k) \right| \right)$$

$\langle i \rangle$
 H_{SIM}

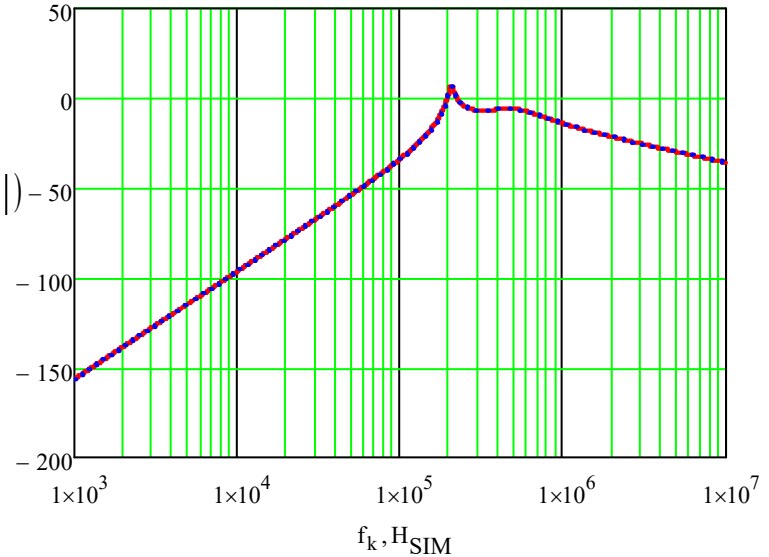

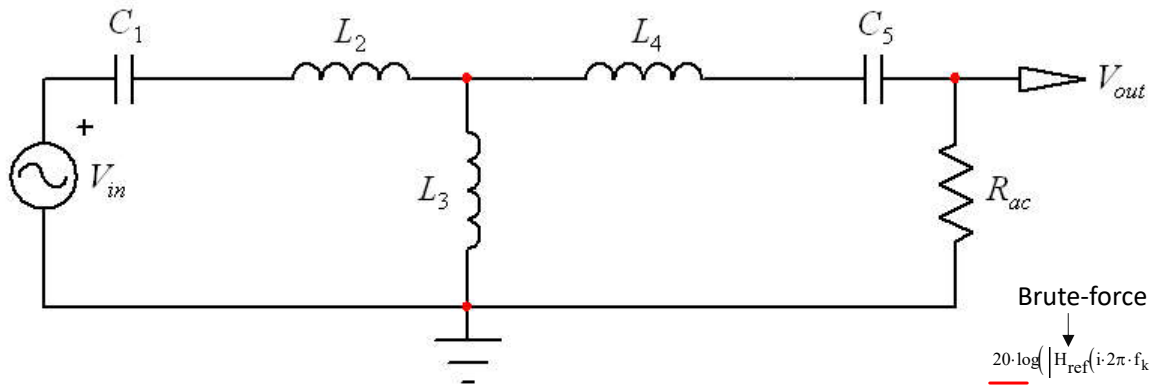


$$Z_1(s) := \frac{1}{s \cdot C_1} + s \cdot L_2$$

$$Z_4(s) := s \cdot L_4 + \frac{1}{s \cdot C_5}$$


$$H_{\text{ref}}(s) := \frac{s \cdot L_3}{s \cdot L_3 + Z_1(s)} \cdot \frac{R_{ac}}{Z_4(s) + R_{ac} + (s \cdot L_3 \parallel Z_1(s))}$$

Brute force transfer function

Magnitude difference


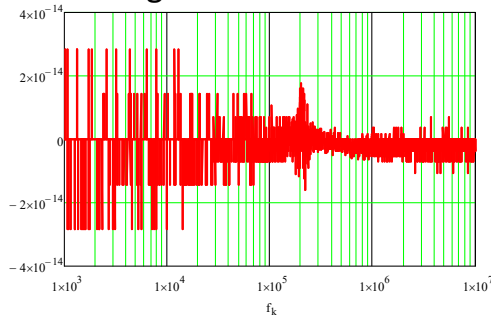



Phase difference

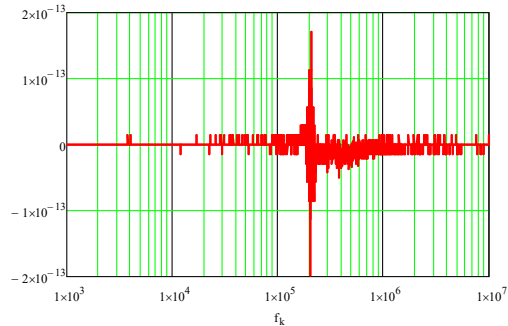

Brute-force

$$\begin{aligned} & \downarrow \\ & 20 \cdot \log(|H_{\text{ref}}(i \cdot 2\pi \cdot f_k)|) \\ & \text{---} \\ & 20 \cdot \log(|H_1(i \cdot 2\pi \cdot f_k)|) \\ & \dots \\ & \uparrow \\ & H(s) \end{aligned}$$

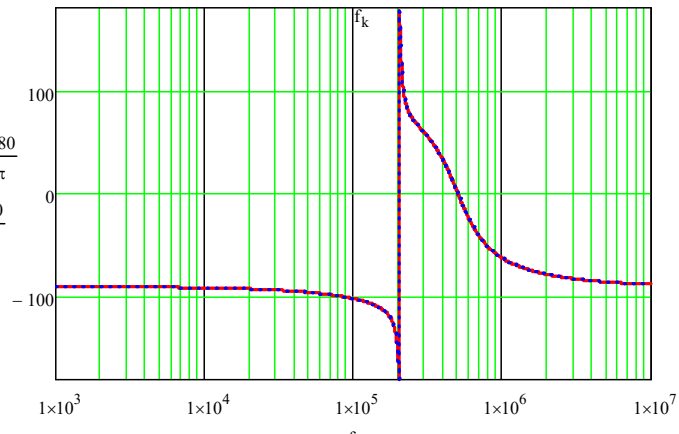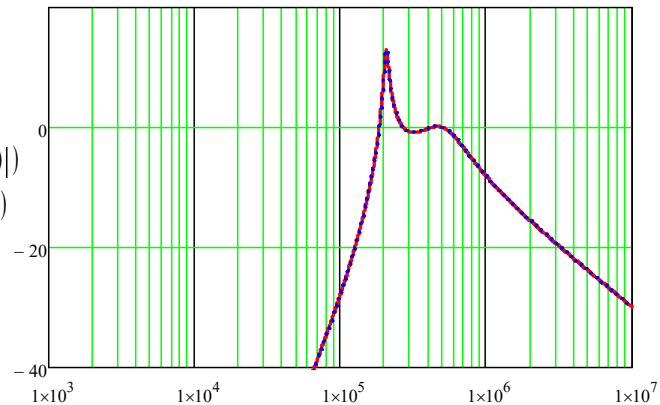

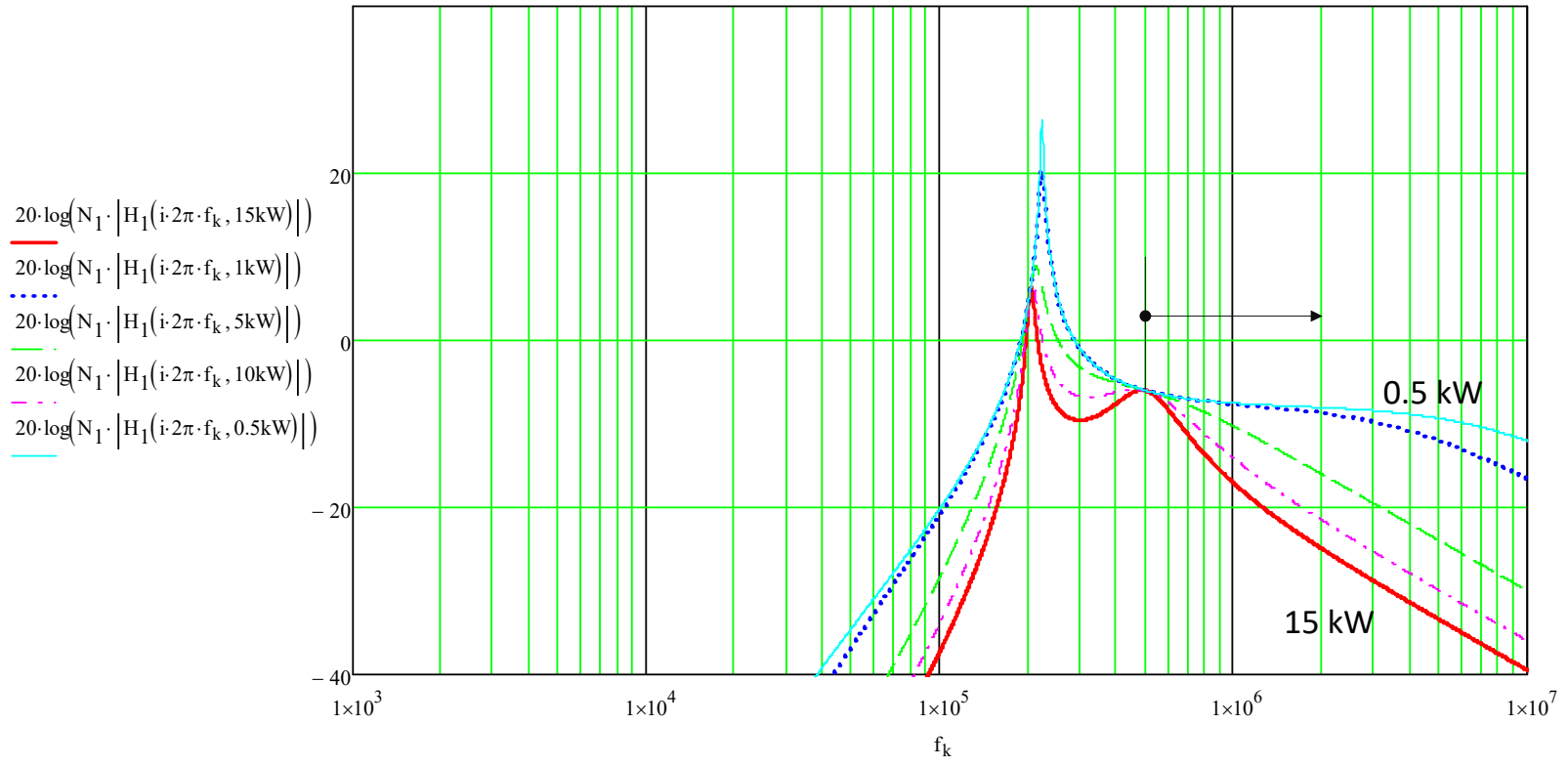

$$\|(x,y) := \frac{x \cdot y}{x + y}$$

CLLC converter transfer function

$$\text{bino}(n,j) := \frac{n!}{j! \cdot (n-j)!}$$

$$C_1 := 14.7\text{nF} \quad N_1 := 0.5 \quad L_2 := 6.8\mu\text{H} \quad L_3 := 28\mu\text{H}$$

turns ratio N1 is 1:n

$$P_{\text{out}} := 10\text{kW} \quad V_{\text{out}} := 500\text{V} \quad R_L := \frac{V_{\text{out}}^2}{P_{\text{out}}} = 25\Omega$$

$$R_{\text{ac}} := \frac{8}{\pi^2} \cdot \frac{R_L}{N_1^2} = 81.0569\Omega$$

$$C_5 := C_1 \cdot N_1^2 = 3.675\text{nF} \quad L_4 := \frac{L_2}{N_1^2} = 27.2\mu\text{H}$$

$$R_{\text{inf}} := 10^{-23}\Omega \quad R_s := 10^{-23}\Omega$$

$$H_0 := 0$$

$$\tau_1 := R_s \cdot C_1 = 0\mu\text{s} \quad \tau_2 := \frac{L_2}{R_{\text{inf}}} = 0\mu\text{s} \quad \tau_3 := \frac{L_3}{R_{\text{inf}}} = 0\mu\text{s}$$

$$\tau_4 := \frac{L_4}{R_{\text{inf}}} = 0\mu\text{s} \quad \tau_5 := R_{\text{ac}} \cdot C_5 = 2.9788 \times 10^{-7}\text{s}$$

$$b_1 := \tau_1 + \tau_2 + \tau_3 + \tau_4 + \tau_5 = 0.2979\mu\text{s}$$

How many terms in b2?

$$\text{bino}(5,2) = 10 \quad \text{5th order, term 2}$$

$$\tau_{12} := \frac{L_2}{R_s} = 6.8 \times 10^{17}\text{s} \quad \tau_{13} := \frac{L_3}{R_s} = 2.8 \times 10^{18}\text{s}$$

$$\tau_{14} := \frac{L_4}{R_{\text{inf}}} = 0\text{s} \quad \tau_{15} := R_{\text{ac}} \cdot C_5 = 2.9788 \times 10^{-7}\text{s}$$

$$\tau_{23} := \frac{L_3}{R_{\text{inf}}} = 0\text{s} \quad \tau_{24} := \frac{L_4}{R_{\text{inf}}}$$

$$\tau_{25} := R_{\text{ac}} \cdot C_5 = 2.9788 \times 10^{-7}\text{s} \quad \tau_{34} := \frac{L_4}{R_{\text{inf}}} = 0\text{s}$$

$$\tau_{35} := R_{\text{inf}} \cdot C_5 = 3.675 \times 10^{14}\text{s} \quad \tau_{45} := R_{\text{inf}} \cdot C_5 = 3.675 \times 10^{14}\text{s}$$

$$b_2 := \tau_1 \cdot \tau_{12} + \tau_1 \cdot \tau_{13} + \tau_1 \cdot \tau_{14} + \tau_1 \cdot \tau_{15} + \tau_2 \cdot \tau_{23} + \tau_2 \cdot \tau_{24} + \tau_2 \cdot \tau_{25} + \tau_3 \cdot \tau_{34} + \tau_3 \cdot \tau_{35} + \tau_4 \cdot \tau_{45} = 7.1442 \times 10^{-13}\text{s}^2$$

$$b_2 := R_s \cdot C_1 \cdot \frac{L_2}{R_s} + R_s \cdot C_1 \cdot \frac{L_3}{R_s} + R_s \cdot C_1 \cdot \frac{L_4}{R_{\text{inf}}} + R_s \cdot C_1 \cdot (R_{\text{ac}} \cdot C_5) + \frac{L_2}{R_{\text{inf}}} \cdot \frac{L_3}{R_{\text{inf}}} + \frac{L_2}{R_{\text{inf}}} \cdot \frac{L_4}{R_{\text{inf}}} + \frac{L_2}{R_{\text{inf}}} \cdot (R_{\text{ac}} \cdot C_5) + \frac{L_3}{R_{\text{inf}}} \cdot \frac{L_4}{R_{\text{inf}}} + \frac{L_3}{R_{\text{inf}}} \cdot (R_{\text{inf}} \cdot C_5) + \frac{L_4}{R_{\text{inf}}} \cdot (R_{\text{inf}} \cdot C_5) = 7.1442 \times 10^{-13}\text{s}^2$$

$$b_2 := C_1 \cdot L_2 + C_1 \cdot L_3 + 0 + 0 + 0 + 0 + 0 + 0 + 0 + L_3 \cdot C_5 + L_4 \cdot C_5 = 7.1442 \times 10^{-13}\text{s}^2$$

How many terms in b3?

$\text{bino}(5, 3) = 10$ 5th order, term 3

$$\tau_{123} := \frac{L_3}{R_{\text{inf}}} = 0 \text{ s} \quad \tau_{125} := R_{\text{ac}} \cdot C_5 = 2.9788 \times 10^{-7} \text{ s}$$

$$\tau_{124} := \frac{L_4}{R_{\text{inf}}} = 0 \text{ s} \quad \tau_{134} := \frac{L_4}{R_{\text{inf}}} = 0 \text{ s}$$

$$\tau_{135} := R_{\text{ac}} \cdot C_5 = 2.9788 \times 10^{-7} \text{ s} \quad \tau_{145} := R_{\text{inf}} \cdot C_5 = 3.675 \times 10^{14} \text{ s}$$

$$\tau_{234} := \frac{L_4}{R_{\text{inf}}} = 0 \text{ s} \quad \tau_{235} := R_{\text{inf}} \cdot C_5 = 3.675 \times 10^{14} \text{ s}$$

$$\tau_{245} := R_{\text{inf}} \cdot C_5 = 3.675 \times 10^{14} \text{ s} \quad \tau_{345} := R_{\text{inf}} \cdot C_5 = 3.675 \times 10^{14} \text{ s}$$

$$b_3 := \tau_1 \cdot \tau_{12} \cdot \tau_{123} + \tau_1 \cdot \tau_{12} \cdot \tau_{124} + \tau_1 \cdot \tau_{12} \cdot \tau_{125} + \tau_1 \cdot \tau_{13} \cdot \tau_{134} + \tau_1 \cdot \tau_{13} \cdot \tau_{135} + \tau_1 \cdot \tau_{14} \cdot \tau_{145} + \tau_2 \cdot \tau_{23} \cdot \tau_{234} + \tau_2 \cdot \tau_{23} \cdot \tau_{235} + \tau_2 \cdot \tau_{24} \cdot \tau_{245} + \tau_3 \cdot \tau_{34} \cdot \tau_{345} = 1.5239 \times 10^8 \cdot \text{ns}^3$$

$$b_3 := R_s \cdot C_1 \cdot \frac{L_2}{R_s} \cdot \frac{L_3}{R_{\text{inf}}} + R_s \cdot C_1 \cdot \frac{L_2}{R_s} \cdot \frac{L_4}{R_{\text{inf}}} + R_s \cdot C_1 \cdot \frac{L_2}{R_s} \cdot (R_{\text{ac}} \cdot C_5) + R_s \cdot C_1 \cdot \frac{L_3}{R_s} \cdot \frac{L_4}{R_{\text{inf}}} + R_s \cdot C_1 \cdot \frac{L_3}{R_s} \cdot (R_{\text{ac}} \cdot C_5) + R_s \cdot C_1 \cdot \frac{L_4}{R_{\text{inf}}} \cdot (R_{\text{inf}} \cdot C_5) + \frac{L_2}{R_{\text{inf}}} \cdot \frac{L_3}{R_{\text{inf}}} \cdot \frac{L_4}{R_{\text{inf}}} + \frac{L_2}{R_{\text{inf}}} \cdot \frac{L_3}{R_{\text{inf}}} \cdot (R_{\text{inf}} \cdot C_5) + \frac{L_2}{R_{\text{inf}}} \cdot \frac{L_4}{R_{\text{inf}}} \cdot (R_{\text{inf}} \cdot C_5) + \frac{L_3}{R_{\text{inf}}} \cdot \frac{L_4}{R_{\text{inf}}} \cdot (R_{\text{inf}} \cdot C_5) = 1.5239 \times 10^8 \cdot \text{ns}^3$$

$$b_3 := 0 + 0 + C_1 \cdot L_2 \cdot C_5 \cdot R_{\text{ac}} + 0 + C_1 \cdot L_3 \cdot R_{\text{ac}} \cdot C_5 + 0 + 0 + 0 + 0 + 0 = 1.5239 \times 10^8 \cdot \text{ns}^3$$

How many terms in b4?

$\text{bino}(5, 4) = 5$ 5th order, term 4

$$\tau_{1234} := \frac{L_4}{R_{\text{inf}}} = 0 \text{ s}$$

$$\tau_{1245} := C_5 \cdot R_{\text{inf}} = 3.675 \times 10^{14} \text{ s}$$

$$\tau_{1235} := C_5 \cdot R_{\text{inf}} = 3.675 \times 10^{14} \text{ s}$$

$$\tau_{1345} := C_5 \cdot R_{\text{inf}} = 3.675 \times 10^{14} \text{ s}$$

$$\tau_{2345} := C_5 \cdot R_{\text{inf}} = 3.675 \times 10^{14} \text{ s}$$

$$b_4 := \tau_1 \cdot \tau_{12} \cdot \tau_{123} \cdot \tau_{1234} + \tau_1 \cdot \tau_{12} \cdot \tau_{123} \cdot \tau_{1235} + (\tau_1 \cdot \tau_{12} \cdot \tau_{124} \cdot \tau_{1245} + \tau_1 \cdot \tau_{13} \cdot \tau_{134} \cdot \tau_{1345} + \tau_2 \cdot \tau_{23} \cdot \tau_{234} \cdot \tau_{2345}) = 6.1421 \times 10^{10} \cdot \text{ns}^4$$

$$b_4 := R_s \cdot C_1 \cdot \frac{L_2}{R_s} \cdot \frac{L_3}{R_{\text{inf}}} \cdot \frac{L_4}{R_{\text{inf}}} + R_s \cdot C_1 \cdot \frac{L_2}{R_s} \cdot \frac{L_3}{R_{\text{inf}}} \cdot (C_5 \cdot R_{\text{inf}}) + \left[R_s \cdot C_1 \cdot \frac{L_2}{R_s} \cdot \frac{L_4}{R_{\text{inf}}} \cdot (C_5 \cdot R_{\text{inf}}) + R_s \cdot C_1 \cdot \frac{L_3}{R_s} \cdot \frac{L_4}{R_{\text{inf}}} \cdot (C_5 \cdot R_{\text{inf}}) + \frac{L_2}{R_{\text{inf}}} \cdot \frac{L_3}{R_{\text{inf}}} \cdot \frac{L_4}{R_{\text{inf}}} \cdot (C_5 \cdot R_{\text{inf}}) \right] = 6.1421 \times 10^{10} \cdot \text{ns}^4$$

$$b_4 := 0 + C_1 \cdot C_5 \cdot L_2 \cdot L_3 + (C_1 \cdot C_5 \cdot L_2 \cdot L_4 + C_1 \cdot L_3 \cdot L_4 \cdot C_5 + 0) = 6.1421 \times 10^{10} \cdot \text{ns}^4$$

How many terms in b5?

$$\text{bino}(5,5) = 1 \quad \text{5th order, term 5}$$

$$\tau_{12345} := C_5 \cdot R_{\text{inf}} = 3.675 \times 10^{14} \text{ s}$$

$$b_5 := \tau_1 \cdot \tau_{12} \cdot \tau_{123} \cdot \tau_{1234} \cdot \tau_{12345} = 2.7978 \times 10^{-9} \cdot \text{ns}^5$$

$$b_5 := 1 \cdot C_1 \cdot \frac{L_2}{1} \cdot \frac{L_3}{1} \cdot \frac{L_4}{R_{\text{inf}}} \cdot (C_5 \cdot 1) = 2.7978 \times 10^{-9} \cdot \text{ns}^5$$

b5 is actually zero because of the degenerate case

$$H_1(s) := \frac{s^3 \cdot \tau_1 \cdot \tau_{13} \cdot \tau_{135}}{1 + b_1 \cdot s + b_2 \cdot s^2 + b_3 \cdot s^3 + b_4 \cdot s^4 + 0 \cdot s^5}$$

$$H_1(s) := \frac{s^3 \cdot (R_{\text{ac}} \cdot L_3 \cdot C_5 \cdot C_1)}{1 + R_{\text{ac}} \cdot C_5 \cdot s + [C_1 \cdot (L_2 + L_3) + C_5 \cdot (L_3 + L_4)] \cdot s^2 + [C_1 \cdot C_5 \cdot R_{\text{ac}} \cdot (L_2 + L_3)] \cdot s^3 + [C_1 \cdot C_5 \cdot (L_2 \cdot L_3 + L_2 \cdot L_4 + L_3 \cdot L_4)] \cdot s^4}$$

Time constants studies:

$$b_1 = 297.8843 \text{ ns} \quad \frac{b_2}{b_1} = 2.3983 \mu\text{s} \quad \frac{b_3}{b_2} = 213.2999 \text{ ns} \quad \frac{b_4}{b_3} = 403.0656 \text{ ns}$$

$$\omega_{01} := \frac{1}{\sqrt{b_2}}$$

$$f_{01} := \frac{\omega_{01}}{2 \cdot \pi} = 188.297 \text{ kHz}$$

$$\omega_{02} := \frac{1}{\omega_{01} \cdot \sqrt{b_4}} = 3.4105 \times 10^6 \frac{1}{\text{s}}$$

$$f_{02} := \frac{\omega_{02}}{2 \cdot \pi} = 542.7963 \text{ kHz}$$

$$Q_1 := \frac{1}{b_1 \cdot \omega_{01}} = 2.8375$$

$$Q_2 := \frac{\omega_{02}}{\frac{b_3}{b_4} - \frac{\omega_{01}}{Q_1}} = 1.6523$$

$$H_2(s) := \frac{\left[s^3 \cdot (R_{\text{ac}} \cdot L_3 \cdot C_5 \cdot C_1) \right]}{\left[1 + \frac{s}{\omega_{01} \cdot Q_1} + \left(\frac{s}{\omega_{01}} \right)^2 \right] \cdot \left[1 + \frac{s}{\omega_{02} \cdot Q_2} + \left(\frac{s}{\omega_{02}} \right)^2 \right]}$$

H_{SIM} := READPRN("ATF.txt")